

SKEE1223: Digital Electronics

10 – Medium Scale Integrated (MSI) Circuits



Dr Michael Tan Loong Peng
PhD (Cambridge)
Senior Lecturer
Faculty of Electrical Engineering
Universiti Teknologi Malaysia

MSI Circuits

- Multiplexers (Mux)
 - 2x1, 4x1, and 8x1 muxes
 - 74x151, 74x153, 74x157 devices
- Demultiplexers (Demux), Decoders, and Encoders
 - 74x138 and 74x139 decoders
 - Encoder, priority encoder and the 75x147 devices
 - BCD to 7-segment decoder and the 74x247 devices
 - Logic functions using muxes and decoders
- Adders and Comparators
 - Half, full and ripple carry adders
 - The 74x83 devices
 - Comparator and the 74x85 devices

Half-Adder

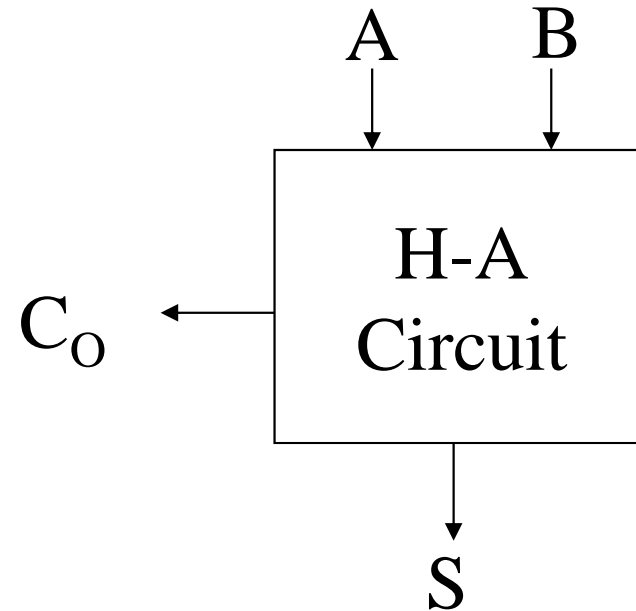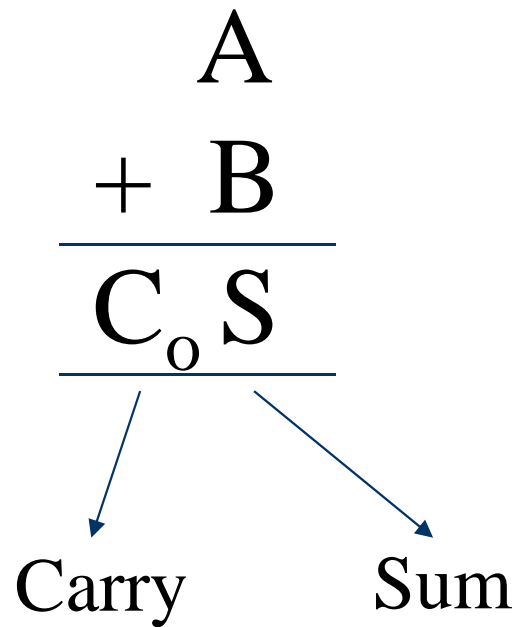- ◆ Half-Adder is a circuit that add two binary numbers without input carry




Half-Adder

- ◆ Truth table for 1-bit Half-Adder

A	B	C _{Out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$C_{out} = A \cdot B$$

$$S = A \oplus B$$

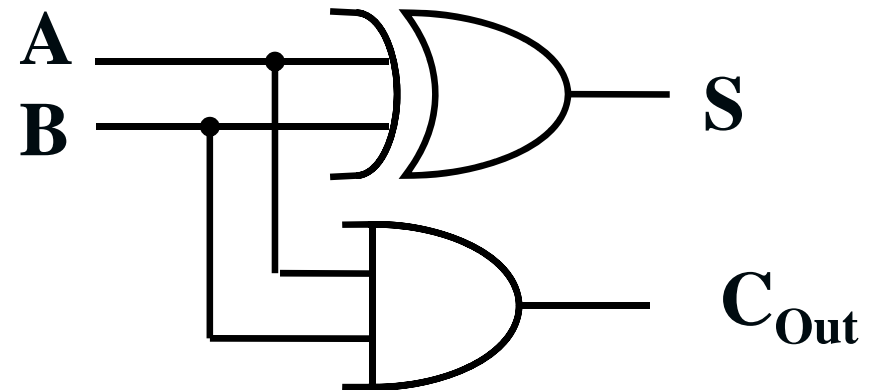


Full-Adder

- ◆ Full-Adder is a circuit that add two binary numbers with the existence of input carry

$$\begin{array}{r} C_{in} \\ A \\ + B \\ \hline C_o S \\ \hline \end{array}$$

Carry Sum

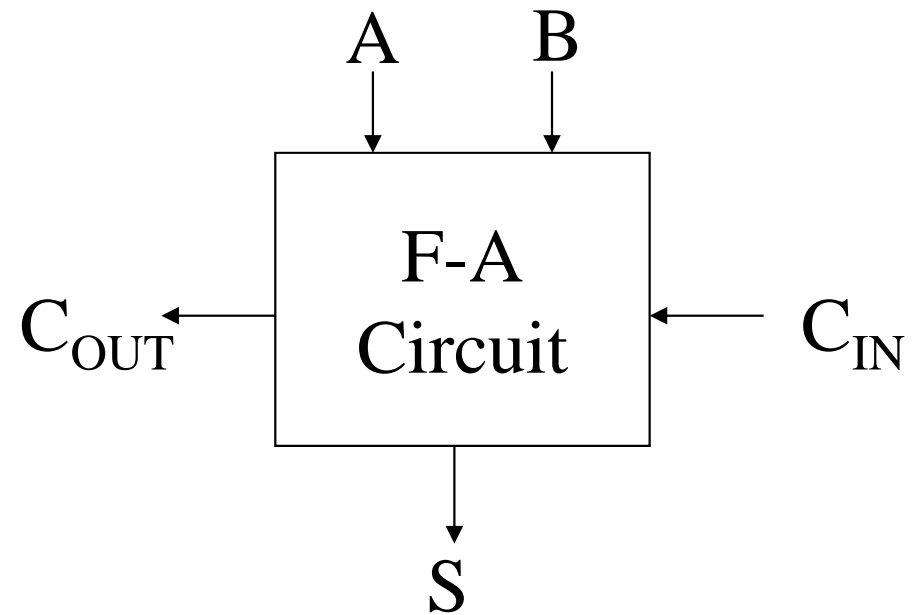

Full-Adder

- ◆ Truth Table for 1-bit Full-Adder

A	B	C_{IN}	C_{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder (cont.)

◆ Design of Full Addder

C_{out}

$C_{in} \backslash AB$	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$C_{in}B$ $C_{in}A$

AB

$$C_{out} = C_{in}B + C_{in}A + AB$$

Sum

$C_{in} \backslash AB$	00	01	11	10
0	0	1	0	1
1	1	0	1	0


$$\begin{aligned}
 S &= C_{in} \overline{A} \overline{B} + C_{in} A B + \overline{C_{in}} \overline{A} B + \overline{C_{in}} A \overline{B} \\
 &= C_{in} (\overline{A} \overline{B} + A B) + \overline{C_{in}} (\overline{A} B + A \overline{B}) \\
 &= C_{in} (\overline{A} \overline{B} + A B) + \overline{C_{in}} (\overline{A} B + A \overline{B}) \\
 &= C_{in} \oplus A \oplus B
 \end{aligned}$$

Full-Adder

- ◆ Boolean expression for C_{OUT} and Sum, S .


$$C_{OUT} = AC_{IN} + BC_{IN} + AB$$

$$S = A \oplus B \oplus C_{IN}$$

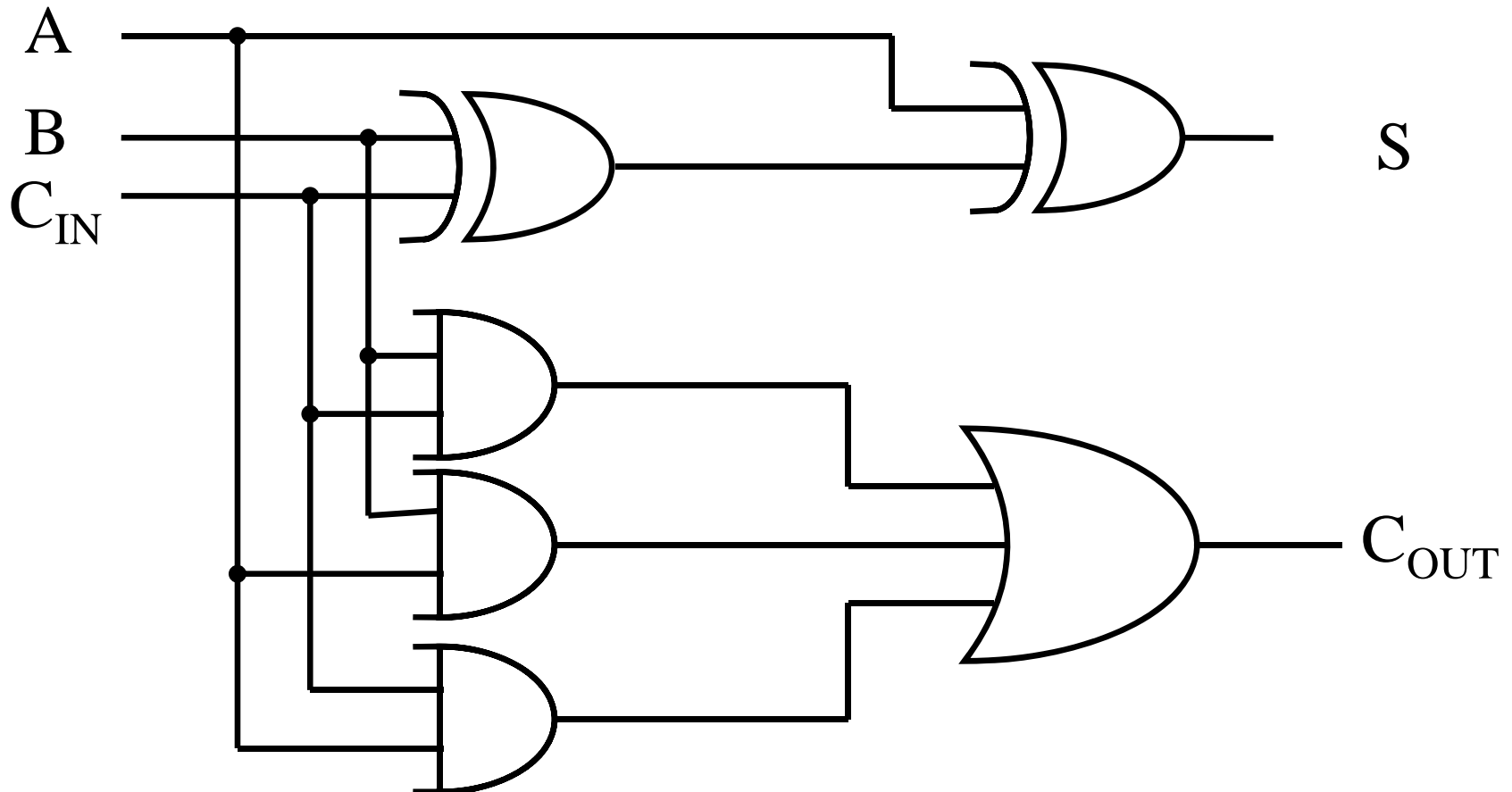


Full-Adder from Half Adders

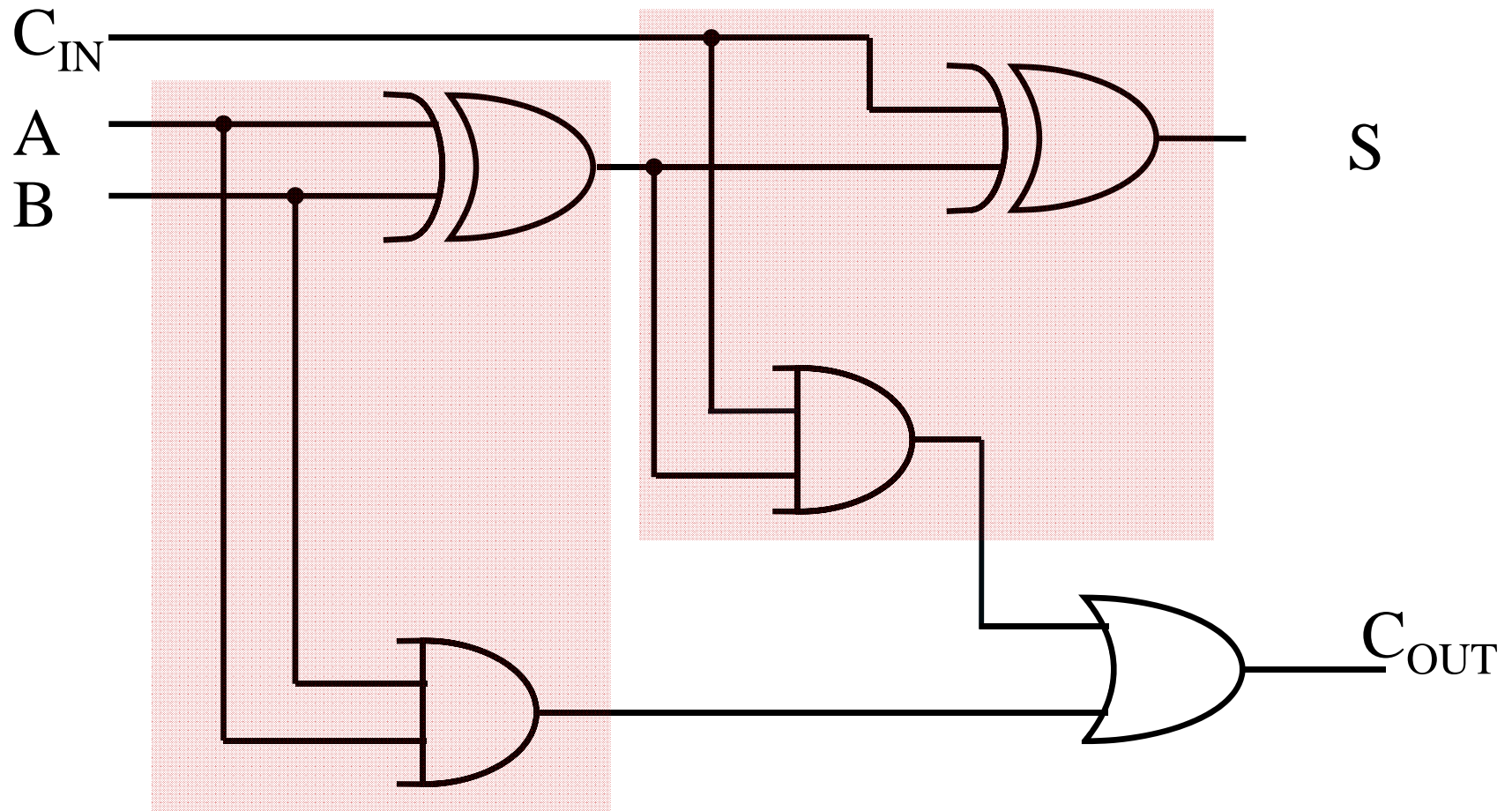- ◆ Logic circuit of Full Adder from two half adders:



Full-Adder

- ◆ Block diagram

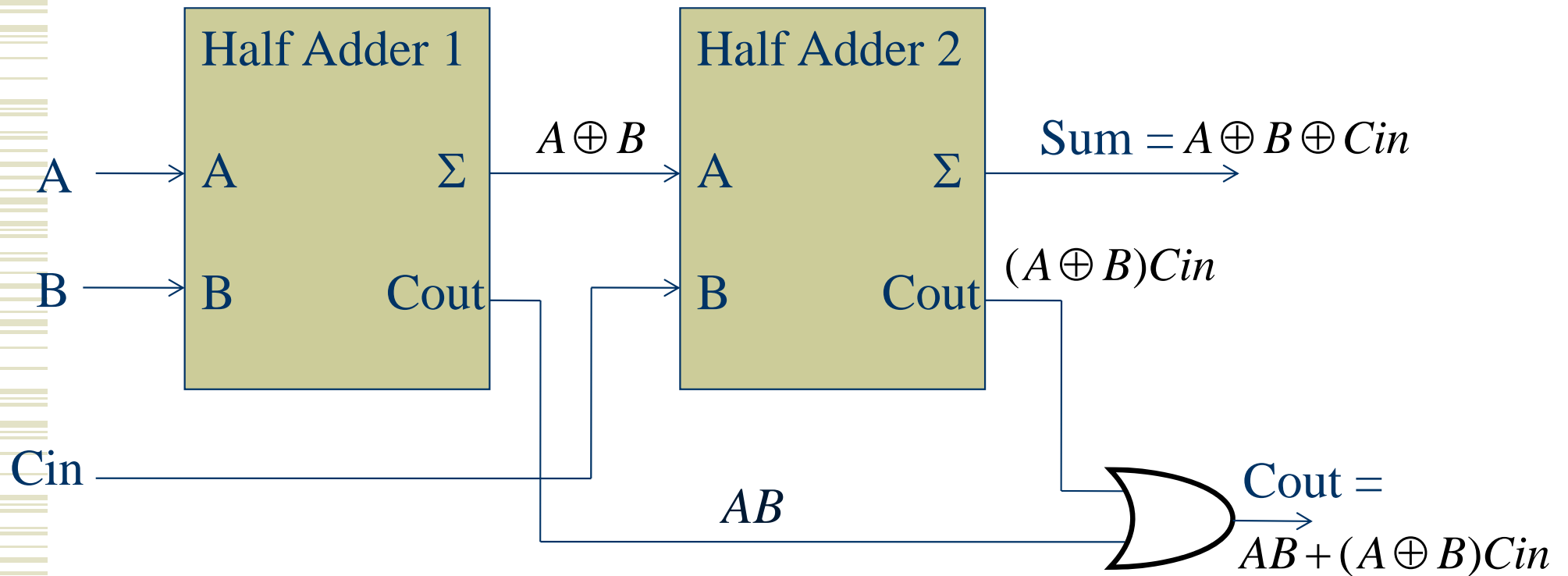

Ripple Carry Adder/Parallel Adder


- Ripple carry adder is used to add multiple bit binary numbers, for example:

$$\begin{array}{rcccccl} 0 & 0 & 0 & 1 & 0 & \leftarrow C_4, C_3, C_2, C_1, C_0 \\ & & & 1 & 0 & 0 & 1 & \leftarrow A_3, A_2, A_1, A_0 \\ + & & & 0 & 1 & 0 & 1 & \leftarrow B_3, B_2, B_1, B_0 \\ \hline & & & 1 & 1 & 1 & 0 & \leftarrow S_3, S_2, S_1, S_0 \end{array}$$

To implement the above, we use the 4-bit ripple carry adder, which adds two four bit numbers $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$ and generates the sum $S_3S_2S_1S_0$ with carries $C_4C_3C_2C_1C_0$


Ripple Carry Adder (cont.)

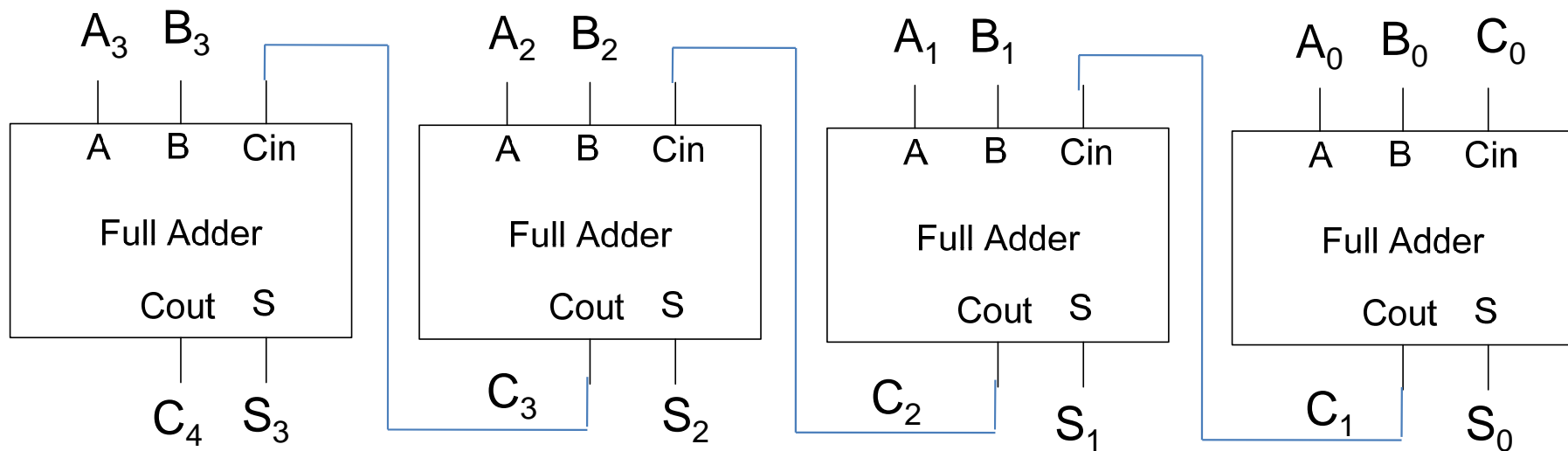- How to design 4-bit ripple carry adder using four full adders?
 - Inputs $A_3A_2A_1A_0$, $B_3B_2B_1B_0$, and C_0 (first carry)
 - Outputs $S_3S_2S_1S_0$ and C_4 (final carry)




Ripple Carry Adder (cont.)

- 7483 Single 4-bit Fast Adder

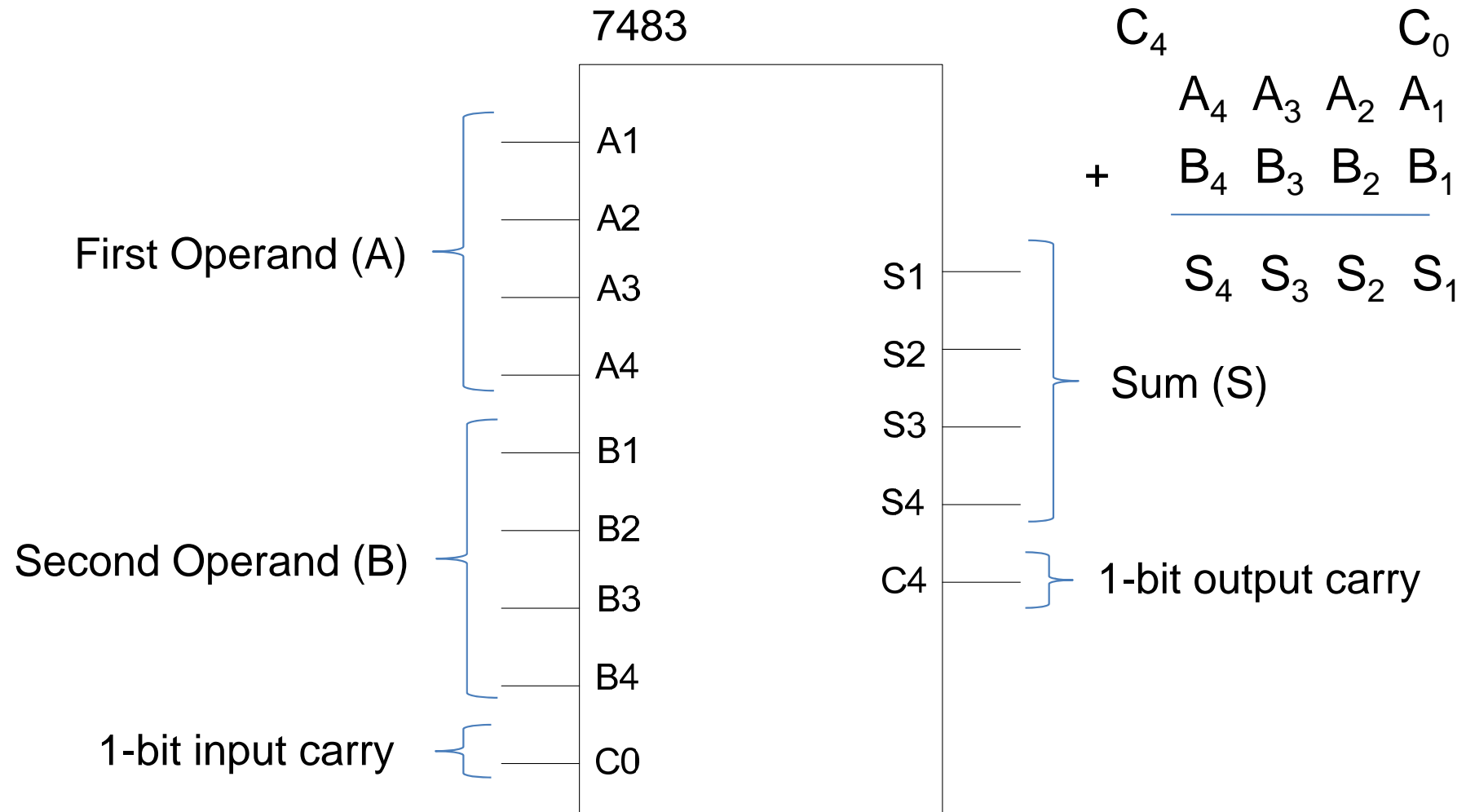


Ripple Full-Adder

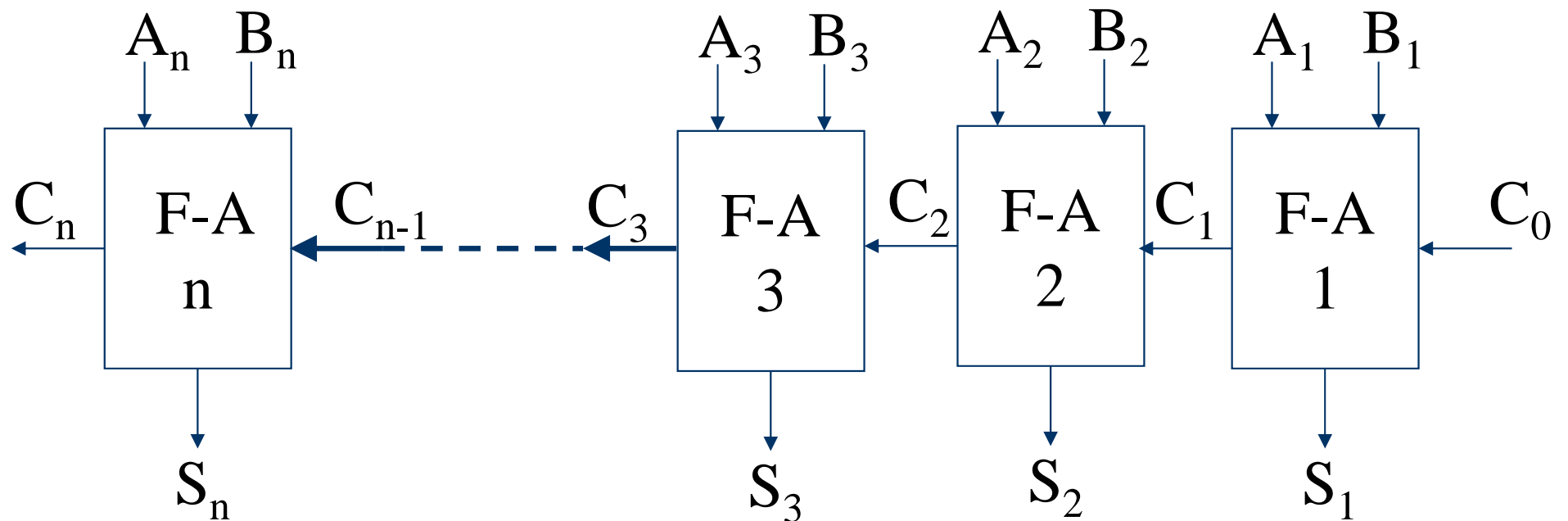- ◆ Adding two numbers for bit greater than 1 (N-bit number)




Full-Adder

- ◆ 7483 4-bit Full-Adder

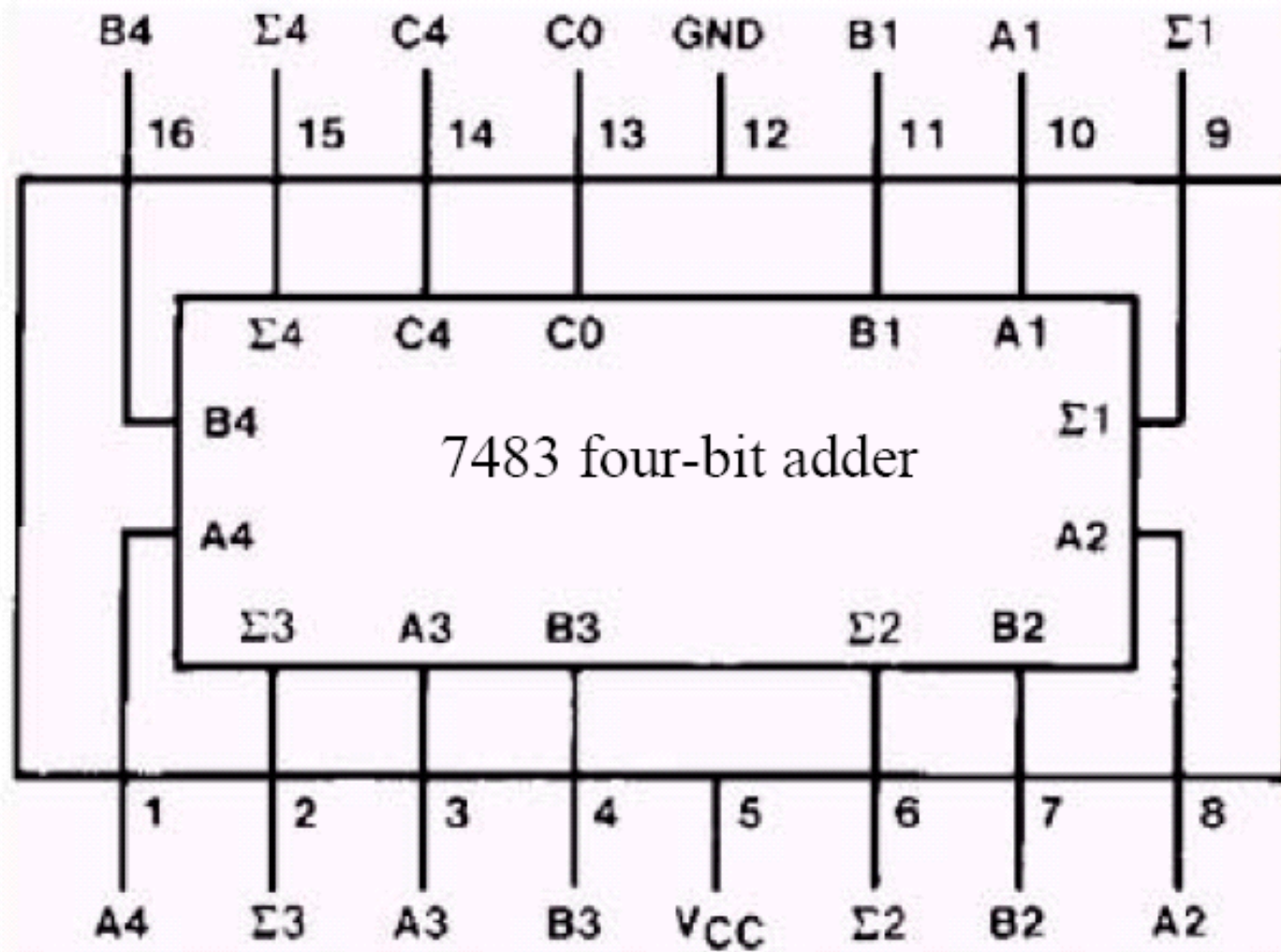

Parallel Adders

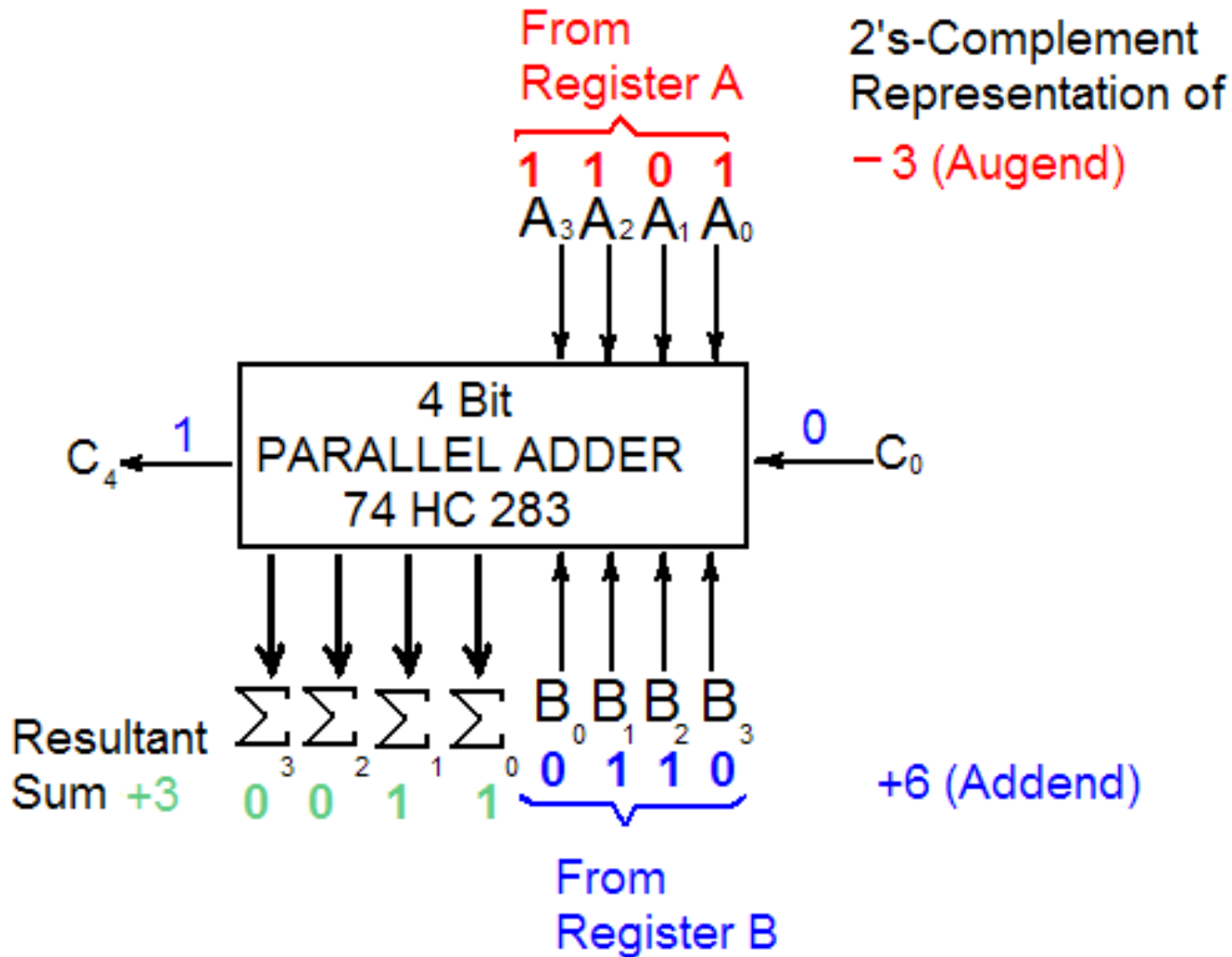

Comparator

- ◆ Comparator is a device that compares two digital numbers or more. Comparison is made in terms of :
 - Equal to ‘=’
 - Less than ‘<’
 - Greater than ‘>’
 - Less or equal than ‘≤’
 - Greater or equal than ‘≥’

Comparator

- ◆ Basically, comparison is made between two 1-bit numbers! It can then be extended to any number with greater bit.
- ◆ Comparison between two 1-bit number are as follows:
(hint: obtain the expression using truth table and K-map)

A > B

The Boolean expression is $Y = A \bullet \bar{B}$

A < B

The Boolean expression is $Y = \bar{A} \bullet B$

Comparator

A=B

The Boolean expression is $Y = \overline{A \oplus B}$

A ≤ B

The Boolean expression is $Y = \overline{A \bullet \overline{B}}$

A ≥ B

The Boolean expression is $Y = \overline{\overline{A} \bullet B}$

Comparator

- ◆ Comparison between two 2-bit numbers, ($\mathbf{A_1A_0}$ and $\mathbf{B_1B_0}$)
- ◆ For example, design a circuit that compares two 2-bit numbers such that the output $\mathbf{X = A_1A_0 > B_1B_0}$
 - Thus, the Boolean expression are:-

1) $\mathbf{A_1 > B_1}$	$\rightarrow \mathbf{A_1 \cdot \bar{B_1}}$
2) $\mathbf{A_1 = B_1}$ dan $\mathbf{A_0 > B_0}$	$\rightarrow \overline{(\mathbf{A_1 \oplus B_1})} \cdot (\mathbf{A_0 \bar{B_0}})$


$$\mathbf{X = A_1 \cdot \bar{B_1} + \overline{(A_1 \oplus B_1)} \cdot (A_0 \bar{B_0})}$$

Comparator

- ◆ Design a circuit that compares two 3-bit numbers **A** and **B** ($\mathbf{A=A_2A_1A_0}$ and $\mathbf{B=B_2B_1B_0}$) such that the output are as follows:-
 - $\mathbf{X = 1}$, if $\mathbf{A=B}$ ($\mathbf{A_2A_1A_0 = B_2B_1B_0}$)
 - $\mathbf{Y = 1}$, if $\mathbf{A>B}$ ($\mathbf{A_2A_1A_0 > B_2B_1B_0}$)
 - $\mathbf{Z = 1}$, if $\mathbf{A<B}$ ($\mathbf{A_2A_1A_0 < B_2B_1B_0}$)

Solution Comparator


- ◆ Use 74HC85 Comparator chip

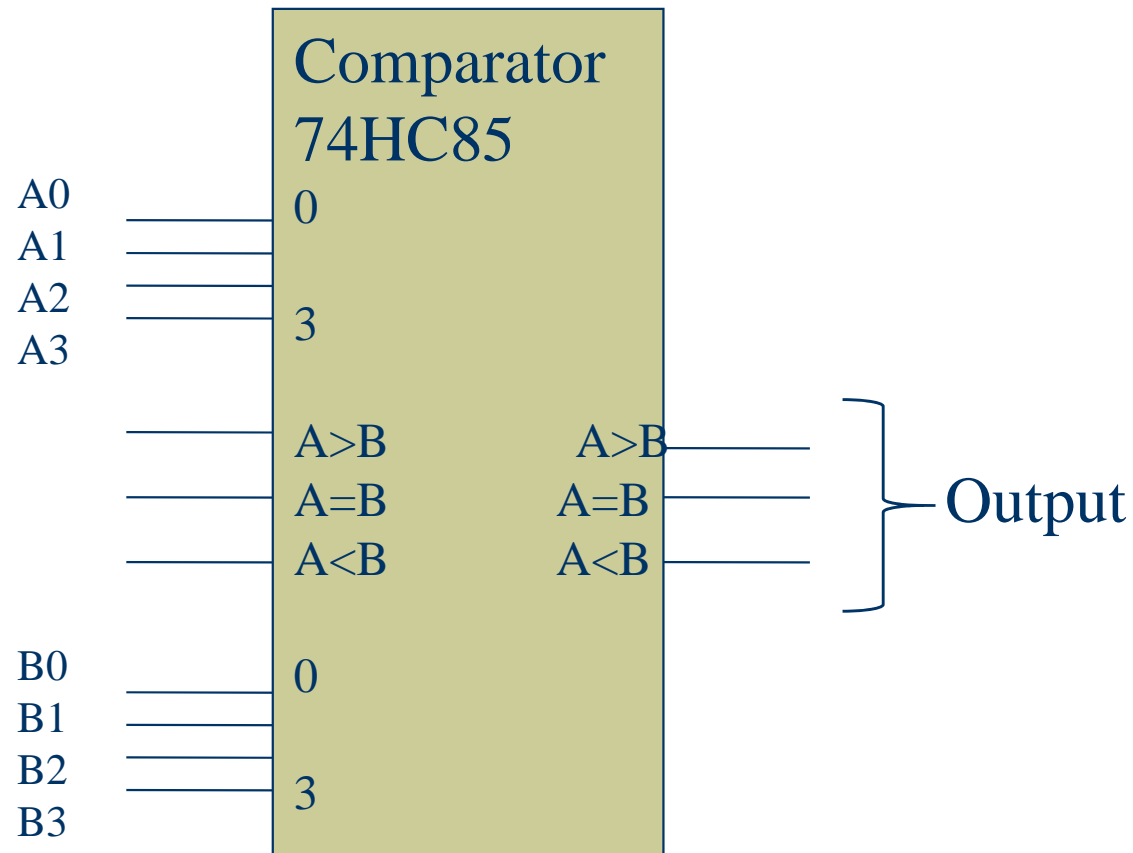

Comparators

- Function is to compare the magnitudes of two binary quantities
- 1-bit comparator:

$A = B$ $A > B$ $A < B$



A B	F_1	F_2	F_3
0 0	1	0	0
0 1	0	0	1
1 0	0	1	0
1 1	1	0	0

$F_1 = 1$ when $A = B$
 $F_2 = 1$ when $A > B$
 $F_3 = 1$ when $A < B$

What are the logic expressions?

$$F_1 = \overline{A \oplus B}$$

$$F_2 = A \cdot \overline{B}$$

$$F_3 = \overline{A} \cdot B$$

Comparators (cont.)

- 2-bit comparator A (A1,A0) and B (B1, B0)

A ₁	A ₀	B ₁	B ₀	A = B (F ₁)	A > B (F ₂)	A < B (F ₃)
0	0	0	0	1	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1

A ₁	A ₀	B ₁	B ₀	A = B (F ₁)	A > B (F ₂)	A < B (F ₃)
1	0	0	0	0	1	0
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	0	1	1	0	0	1
1	1	0	0	0	1	0
1	1	0	1	0	1	0
1	1	1	0	0	1	0
1	1	1	1	1	0	0

$F_1 = 1$ when $A = B$

$F_2 = 1$ when $A > B$

$F_3 = 1$ when $A < B$

Can you get the logic expression?

Comparators (cont.)

- 2-bit comparator (cont.)

By doing K-Maps for F1, F2, and F3,

For $A = B$,

$$F_1 = \overline{A_1} \cdot \overline{A_0} \cdot \overline{B_1} \cdot \overline{B_0} + \overline{A_1} \cdot A_0 \cdot \overline{B_1} \cdot B_0 + A_1 \cdot \overline{A_0} \cdot B_1 \cdot \overline{B_0} + A_1 \cdot A_0 \cdot B_1 \cdot B_0$$

For $A > B$,

$$F_2 = A_1 \cdot \overline{B_1} + A_0 \cdot \overline{B_1} \cdot \overline{B_0} + A_1 \cdot A_0 \cdot \overline{B_0}$$

For $A < B$,

$$F_3 = \overline{A_1} \cdot B_1 + \overline{A_0} \cdot B_1 \cdot B_0 + \overline{A_1} \cdot \overline{A_0} \cdot B_0$$

Comparators (cont.)

- 7485 Single 4-bit comparator

