


SKEE1223: Digital Electronics

11 – Latches and Flip-Flops

Dr Michael Tan Loong Peng
PhD (Cambridge)
Senior Lecturer
Faculty of Electrical Engineering
Universiti Teknologi Malaysia

Introduction


- ◆ A **combinational circuit** is a circuit whose **outputs** depends only upon its **current inputs**.
 - Do not have memory
 - Cannot store state
- ◆ A **sequential circuit** is a circuit whose **outputs** depends on the **current inputs** and the system's **current state** (past behavior).
 - Require use of storage elements.
 - Contents of storage elements is called state.
 - Circuit goes through sequence of states as a result of changes in inputs.

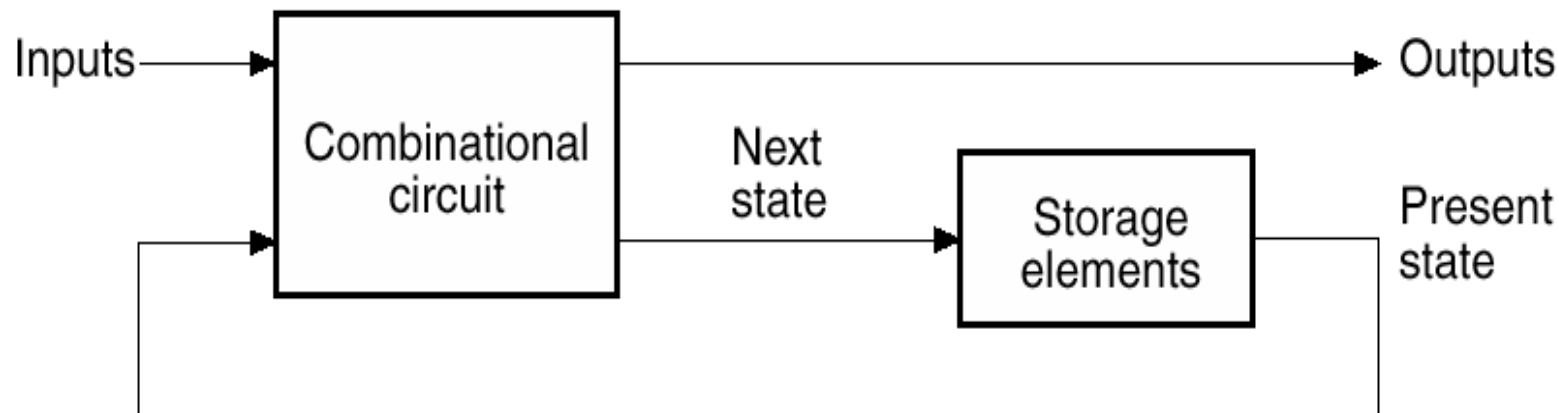

Storage or Memory Element


- ◆ Two types of memory element :-
- ◆ **LATCH**: temporary storage device that has two stable states (bi-stable). Output is executed upon changes in the input.
- ◆ **FLIP-FLOP**: synchronous bi-stable device. Synchronous means that the output changes state only at a specified point on the triggering input called the clock (CLK). Output changes are synchronize with the changes of the clock state.

Memory Element

 


SR Latch (NOR version)

 - ◆ Set-Reset latch
- ◆ Q_n is initial state, Q_{n+1} is next state.





Function Table			
S	R	Q_{n+1}	Function
0	0	Q_n	Hold
0	1	0	Reset
1	0	1	Set
1	1	?	Not allowed

 

Graphical symbol


- ◆ If S & R both 1 at same time, illegal inputs because it will cause $Q = Q' = 0$

SR Latch Operation

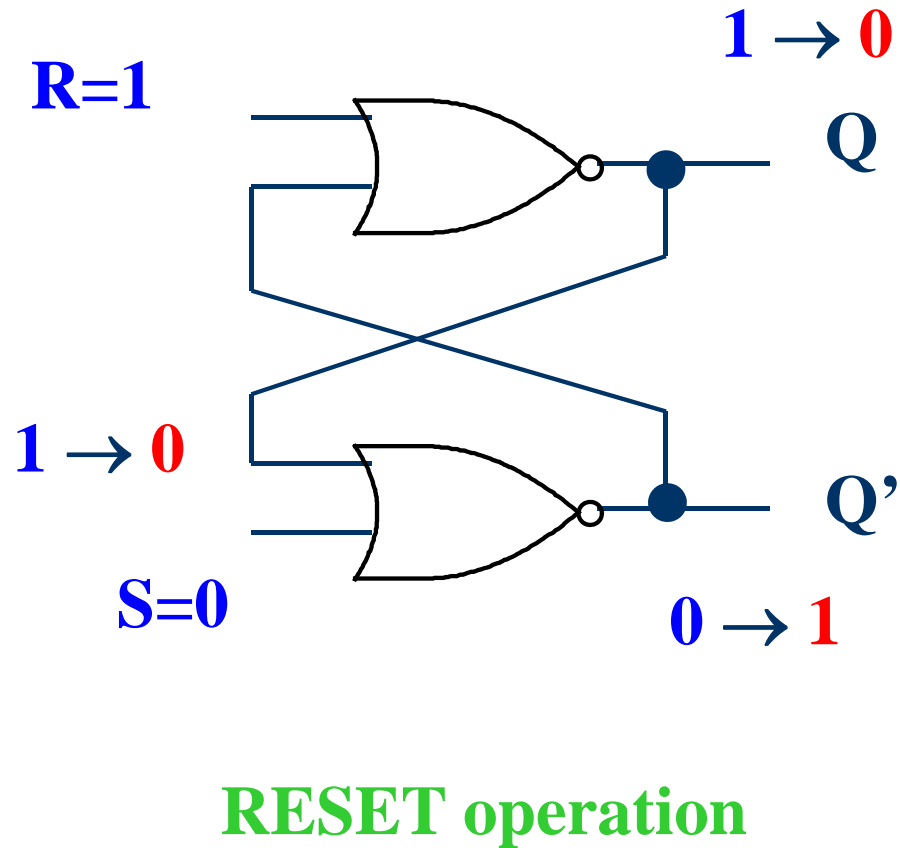 


SR Latch Operation

SET operation

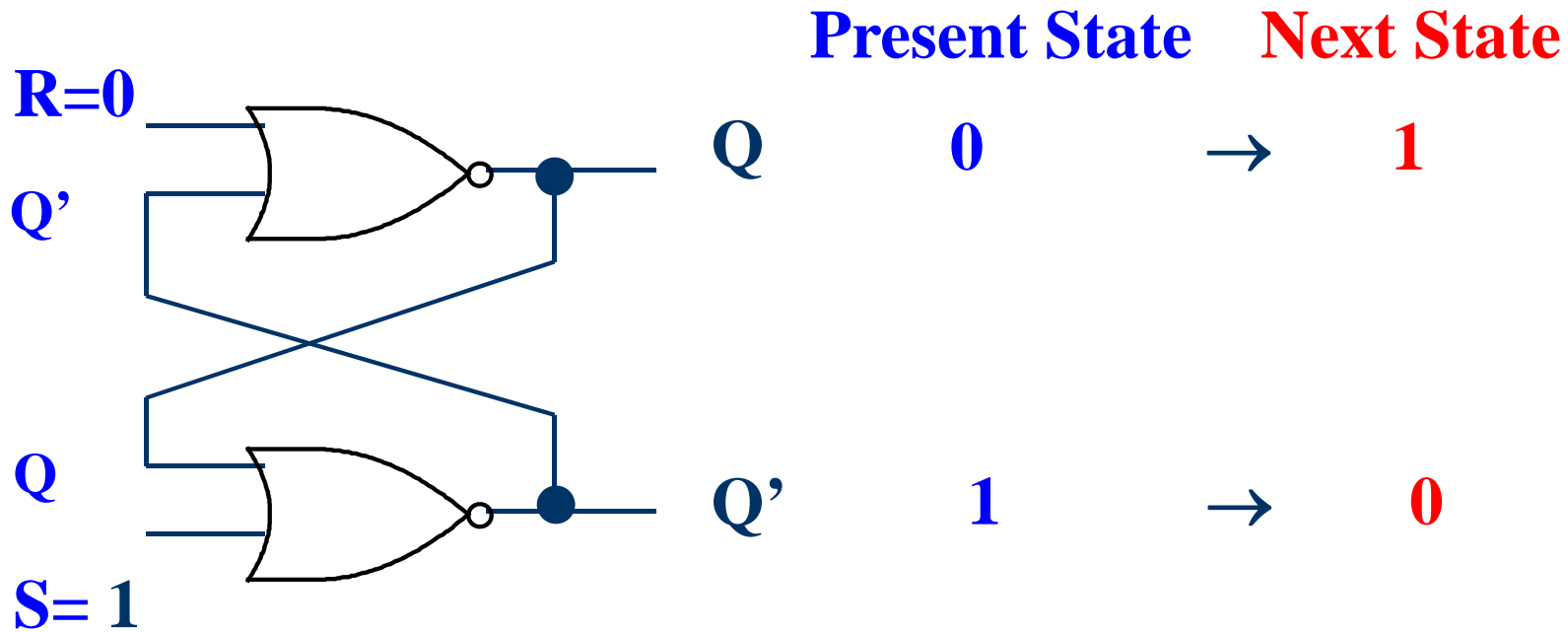


SR Latch Operation

SET operation

 


 Locate NOR with a high “1” input then find the corresponding Q




SR Latch Operation

SET operation

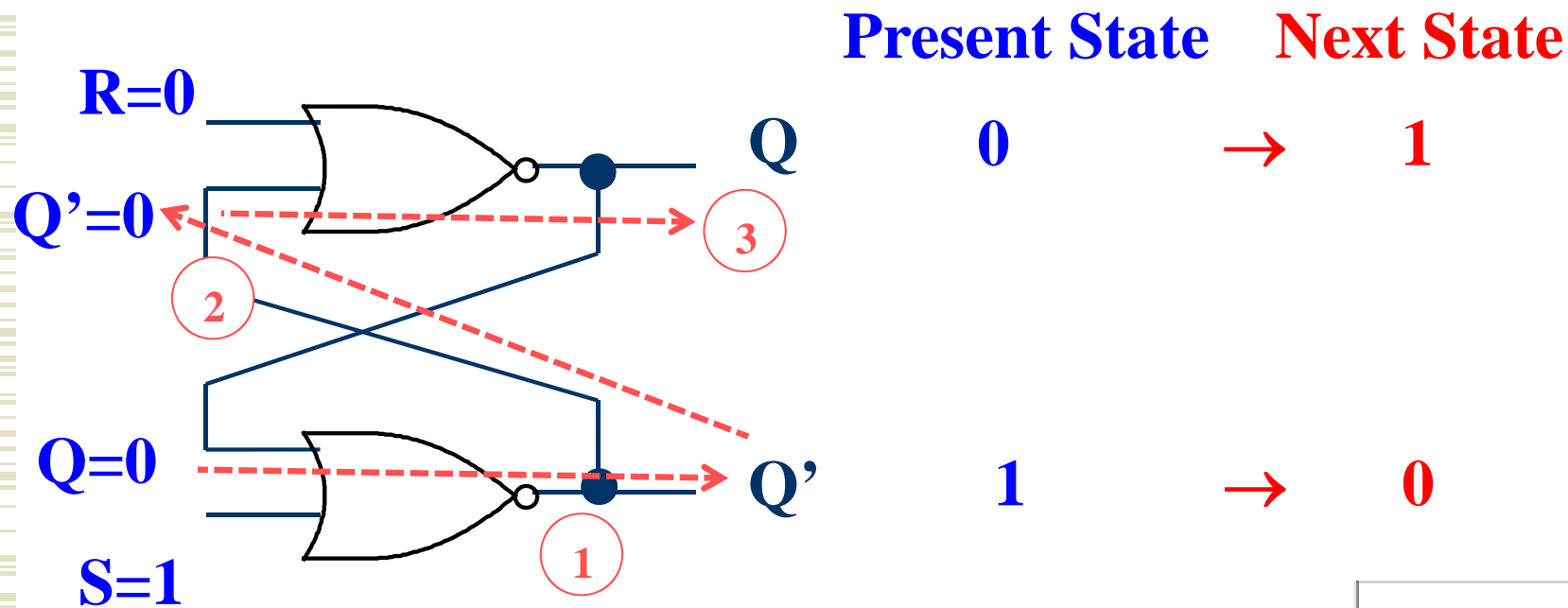

Locate NOR with a high “1” input then find the corresponding Q

NOR Gate




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Boolean Expression

$Y = (A + B)'$


SR Latch Operation

RESET operation

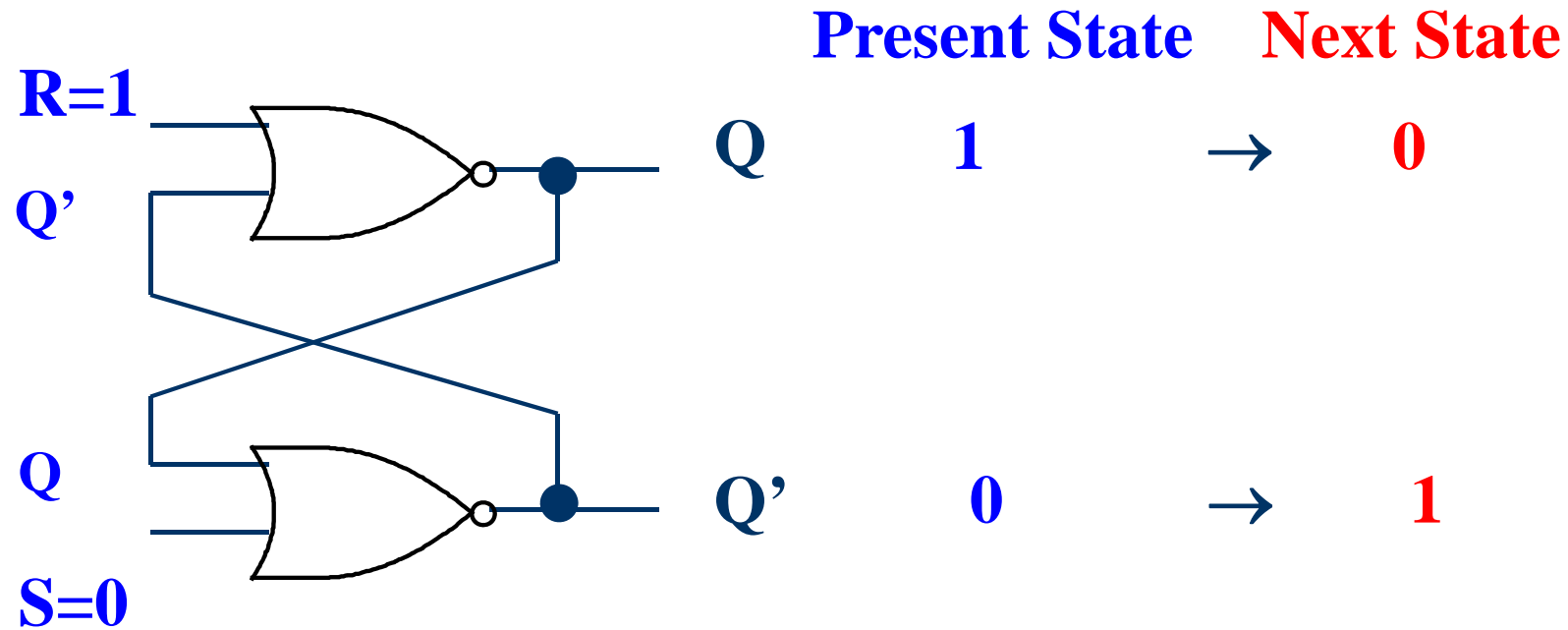


SR Latch Operation

RESET operation

 

Locate NOR with a high “1” input then find the corresponding Q

NOR Gate




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Boolean Expression
 $Y = (A + B)'$


SR Latch Operation

RESET operation

 

Locate NOR with a high “1” input then find the corresponding Q

NOR Gate




Boolean Expression

$$Y = (A + B)'$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


SR Latch Operation (cont)

 

Stable when

$$S = R = 0,$$

$$Q = 1, Q' = 0$$

 


Stable when

$$S = R = 0,$$

$$Q = 0, Q' = 1$$

SR Latch Operation (cont)

 


What about $S=R=1$? (Set, Reset both true?)

Assume that S, R both transition to **1** simultaneously. Q becomes '0', but Q' remains '0'! Outputs are **no longer** complements of each other.


This is an **INVALID STATE**.

S-R LATCH

 - ◆ S-R using **NOR** gates (ACTIVE-HIGH INPUT)



S-R Latch Logic Circuit

 

S-R Latch Logic Symbol

**S-R Latch
Truth Table**

S (Set)	R (Reset)	Output
0	0	No Change
1	0	Q = 1
0	1	Q = 0
1	1	Invalid

S-R LATCH

- ◆ S-R using **NOR** gates (ACTIVE-HIGH INPUT)

S	R	Q_N	Q_{N+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X


$\begin{matrix} R \\ Q_N \end{matrix}$	00	01	11	10
S				
0	0	1	0	0
1	1	1	X	X

Characteristic equation


$$Q_{N+1} = S + \bar{R}Q_N$$

S-R Latch (NAND)

 - ◆ \bar{S} - \bar{R} Latch using **NAND** gates (ACTIVE-LOW INPUT)



\bar{S} - \bar{R} Latch Logic Circuit

 

\bar{S} - \bar{R} Latch Logic Symbol

\bar{S} - \bar{R} Latch Truth Table

This is the S'-R' table. If S-R table, it will be the same as S-R NOR.

\bar{S} (Set)	\bar{R} (Reset)	Q (Output)
0	0	Invalid
0	1	Q = 1
1	0	Q = 0
1	1	No change

S-R Latch (NAND)

- ◆ \bar{S} - \bar{R} Latch using **NAND** gates (**ACTIVE-LOW INPUT**)

\bar{S}	\bar{R}	Q_N	Q_{N+1}
0	0	0	X
0	0	1	X
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


\bar{S} \ $\bar{R}Q_N$	00	01	11	10
0	X	X	1	1
1	0	0	1	0

Characteristic equation

$$Q_{N+1} = S + \bar{R}Q_N$$

 
Exercise

- ◆ Complete the truth table for this latch



 Exercise

- ◆ Complete the truth table for this latch



Condition when $S=1$ and $R=0$

NAND Gate


Boolean Expression

$$Y = (A \cdot B)' = A' + B'$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 
Exercise

- ◆ Complete the truth table for this latch




Locate NAND with a low “0” input then find the corresponding Q

Condition when $S=1$ and $R=0$

NAND Gate			
	A	B	Y
	0	0	1
	0	1	1
Boolean Expression	1	0	1
$Y = (A \cdot B)' = A' + B'$	1	1	0

 Exercise


- ◆ Complete the truth table for this latch



Locate NAND with a low “0” input then find the corresponding Q

Condition when $S=1$ and $R=0$

NAND Gate




A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Boolean Expression

$$Y = (A \cdot B)' = A' + B'$$

 
Exercise

- ◆ Complete the truth table for this latch



Condition when $S=0$ and $R=1$

NAND Gate




A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Boolean Expression

$Y = (A \cdot B)' = A' + B'$

 Exercise


- ◆ Complete the truth table for this latch



Locate NAND with a low “0” input then find the corresponding Q

Condition when $S=0$ and $R=1$

NAND Gate




A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Boolean Expression

$$Y = (A \cdot B)' = A' + B'$$

 Exercise


- Complete the truth table for this latch



Locate NAND with a low “0” input then find the corresponding Q

Condition when $S=0$ and $R=1$

NAND Gate




A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Boolean Expression
 $Y = (A \cdot B)' = A' + B'$

 
Exercise

- ◆ Complete the truth table for this latch



Solution Exercise

 - ◆ S-R latch (**NAND**) with **active high** inputs.



S	R	Q_{n+1}
0	0	Illegal inputs
0	1	1
1	0	0
1	1	Q_n

Please correct this table in your printed slide

S-R Latch Summary


- ◆ S-R Latch in any configuration will
 - SET when $S = 1$ and $R = 0$ (or when $S' = 0$ and $R' = 1$)
 - SET means output Q_{n+1} is 1.
 - RESET when $R = 1$, $S = 0$ (or when $R' = 0$ and $S' = 1$)
 - RESET means output Q_{n+1} is 0.

Gated S-R Latch

- ◆ S-R latch with trigger input, E
- ◆ High – level triggering (active high)
 - E=1: latch is enabled and output(future state) depends on present state and the inputs
 - E=0 : latch is disabled and no change to outputs
- ◆ Low-level triggering (active low)
 - E=1: latch is disabled and no change to outputs
 - E=0 : latch is enabled and output(future state) depends on present state and the inputs


Gated S-R Latch

NAND Gate




A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Boolean Expression
 
$$Y = (A \cdot B)' = A' + B'$$

 
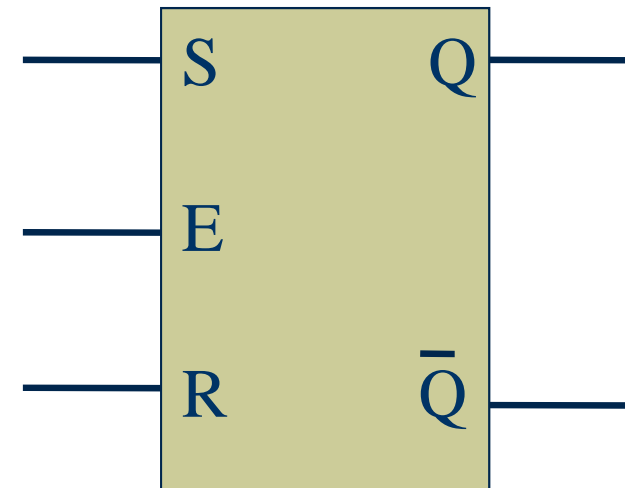
(a) HIGH level triggering input



(b) Example of timing diagram

E	R	S	Q_{N+1}
0	X	X	Q_N
1	0	0	Q_N
1	0	1	1
1	1	0	0
1	1	1	Illegal inputs


(c) Truth-table



 (d) Logic symbol


Gated J-K LATCH

- ◆ Solve the problem of illegal inputs in SR latch.




J-K Latch Logic Circuit

Gated J-K LATCH

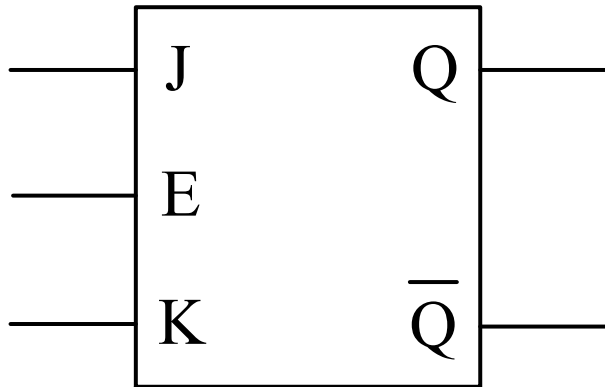

E	J	K	Q_{n+1}
0	X	X	Q_n (no change)
1	0	0	Q_n (no change)
1	0	1	0 (reset)
1	1	0	1 (set)
1	1	1	$\overline{Q_n}$ (toggle)


Gated J-K LATCH

 


Weakness of level triggering : If the duration of triggering is long, the output may toggle a few times when $J = K = 1$.

D LATCH

 - ◆ D Latch using S-R **NAND** implementation!



D Latch Logic Circuit

 


D Latch Logic Symbol

**D Latch
Truth Table**


E	D	Q	Q _{n+1}
0	x	0	0
0	x	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Flip-Flop


- ◆ To synchronize a circuit, LATCH cannot be used. Thus, an EDGE-TRIGGERED FLIP-FLOP is used to synchronize the changes at the output state either at the positive edge or negative edge of the CLOCK (CLK).
- ◆ As mentioned before, CLK is a control input signal used such that the output is executed at a specified time/point.
- ◆ Figure below shows the positive (rising edge) and negative edge (falling edge) of the CLK signal.

 

Flip-Flop

 


(a) Clock

 

(b) Edge triggering symbol

◆ Positive edge triggering circuit


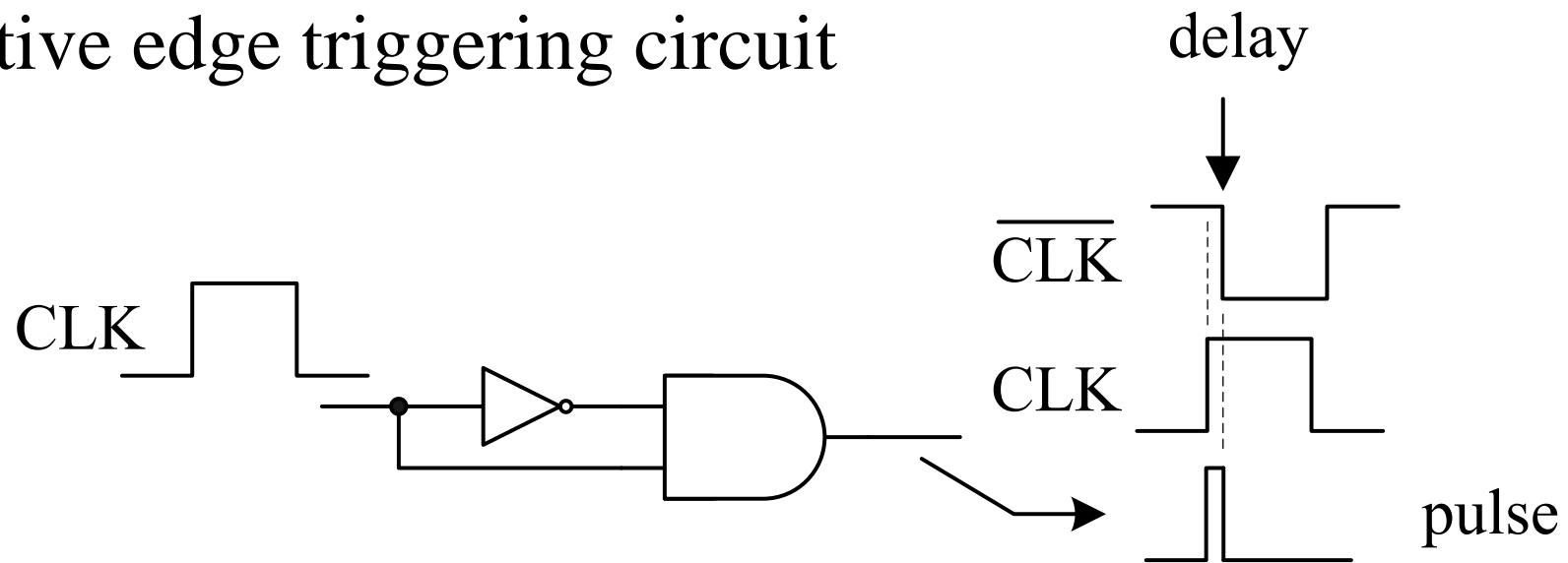


Exercise


- ◆ Design a negative edge triggering circuit
- ◆ Ans : Change AND gate to NAND gate

S-R FLIP-FLOP

- ◆ S-R Flip-Flop

  

S-R FF (+ve Edge-triggered)

 

S-R FF (-ve Edge-triggered)

S-R FLIP-FLOP


- ◆ Truth-table and Transition-table for S-R FF

S	R	Q_N	Q_{N+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	Invalid
1	1	1	Invalid


OUTPUT TRANSITION			FF INPUT	
Q_N		Q_{N+1}	S	R
0	→	0	0	X
0	→	1	1	0
1	→	0	0	1
1	→	1	X	0

$$Q_{N+1} = S + \bar{R}Q_N$$

Exercise S-R FF


 


Exercise S-R FF

 


J-K FLIP-FLOP

- ◆ J-K Flip-flop

  

J-K FF (+ve Edge-triggered)

 

J-K FF (-ve Edge-triggered)

J-K FLIP-FLOP

- ◆ Truth table and Characteristic equation for J-K FF

J	K	Q_N	Q_{N+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

		KQ_N			
		00	01	11	10
J	0	0	1	0	0
	1	1	1	0	1

Characteristic equation

$$Q_{N+1} = J\bar{Q}_N + \bar{K}Q_N$$


J-K FF improve the 'Invalid' condition in S-R FF

J-K FLIP-FLOP

- ◆ J-K FF Transition Table



OUTPUT TRANSITION		FF INPUT	
Q_N	Q_{N+1}	J	K
0	→ 0	0	X
0	→ 1	1	X
1	→ 0	X	1
1	→ 1	X	0

J-K FLIP-FLOP

 


D FLIP-FLOP

◆ D Flip-flop

 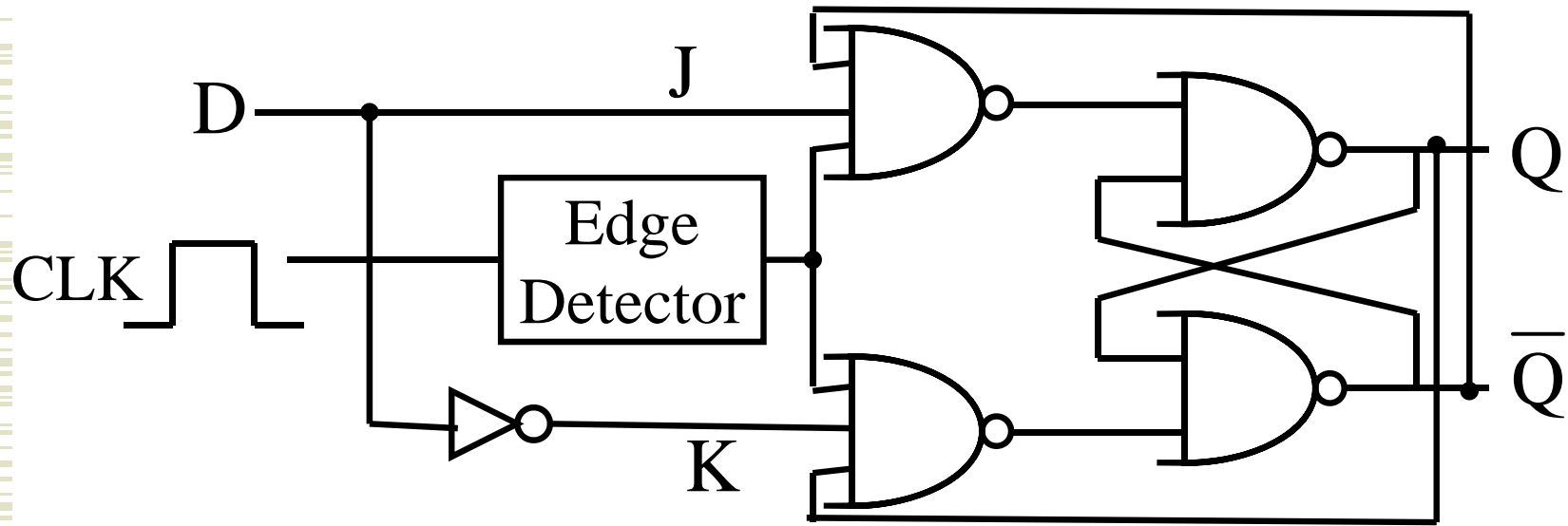

D FF (+ve Edge-triggered)

 

D FF (-ve Edge-triggered)

D FLIP-FLOP

- ◆ Truth table and Characteristic equation for D FF

D	Q_N	Q_{N+1}
0	0	0
0	1	0
1	0	1
1	1	1

Q_N	0	1
D	0	0
1	1	1

Characteristic equation


$$Q_{N+1} = D$$

D FLIP-FLOP

- ◆ D FF Transition Table!


OUTPUT TRANSITION		FF INPUT
Q_N	Q_{N+1}	D
0	→ 0	0
0	→ 1	1
1	→ 0	0
1	→ 1	1

D FLIP-FLOP

 


T FLIP-FLOP

- ◆ Flip-flop T (Toggle)!

 

T FF (+ve Edge-triggered)

 

T FF (-ve Edge-triggered)

T FLIP-FLOP

- ◆ Truth table and Characteristic equation for T FF!

T	Q_N	Q_{N+1}
0	0	0
0	1	1
1	0	1
1	1	0

} Q

		Q_N	
		0	1
T	0	0	1
	1	1	0

Characteristic equation


$$Q_{N+1} = T\overline{Q_N} + \overline{T}Q_N$$

T FLIP-FLOP

- ◆ T FF Transition Table!


OUTPUT TRANSITION		FF INPUT
Q_N	Q_{N+1}	T
0	→ 0	0
0	→ 1	1
1	→ 0	1
1	→ 1	0

T FLIP-FLOP

 

J-K FLIP-FLOP with $\overline{\text{PRE}}$ and $\overline{\text{CLR}}$

 - ◆ J-K Flip-flop with $\overline{\text{PRE}}$ and $\overline{\text{CLR}}$ inputs.




Asynchronous PRESET and CLEAR Inputs

- ◆ Inputs for SR, JK and D flip-flops are called *synchronous inputs* because this input will only be considered by the flip-flops during the triggering edge of the CLK.
- ◆ Most flip-flops also have *asynchronous inputs*. These inputs are used to change the output value immediately without considering the edge-triggered of the flip-flops.
- ◆ These inputs are labeled as PRESET (PRE) and CLEAR (CLR), or *direct set* (S_D) and *direct reset* (R_D).
- ◆ An active level of PRE will set the output (Q) of the flip-flop to logic '1'
- ◆ An active level of CLR will set the output (Q) of the flip-flop to logic '0'



J-K FLIP-FLOP with $\overline{\text{PRE}}$ and $\overline{\text{CLR}}$

- ◆ Truth table for JK Flip-flop with PRESET (PRE) and CLEAR (CLR) inputs!
- ◆ Async input must be kept HIGH for synchronous operation.

$\overline{\text{CLR}}$	$\overline{\text{PRE}}$	FF Operation
0	0	Not allowed
0	1	$Q = 0$
1	0	$Q = 1$
1	1	Usual flip flop operation

 


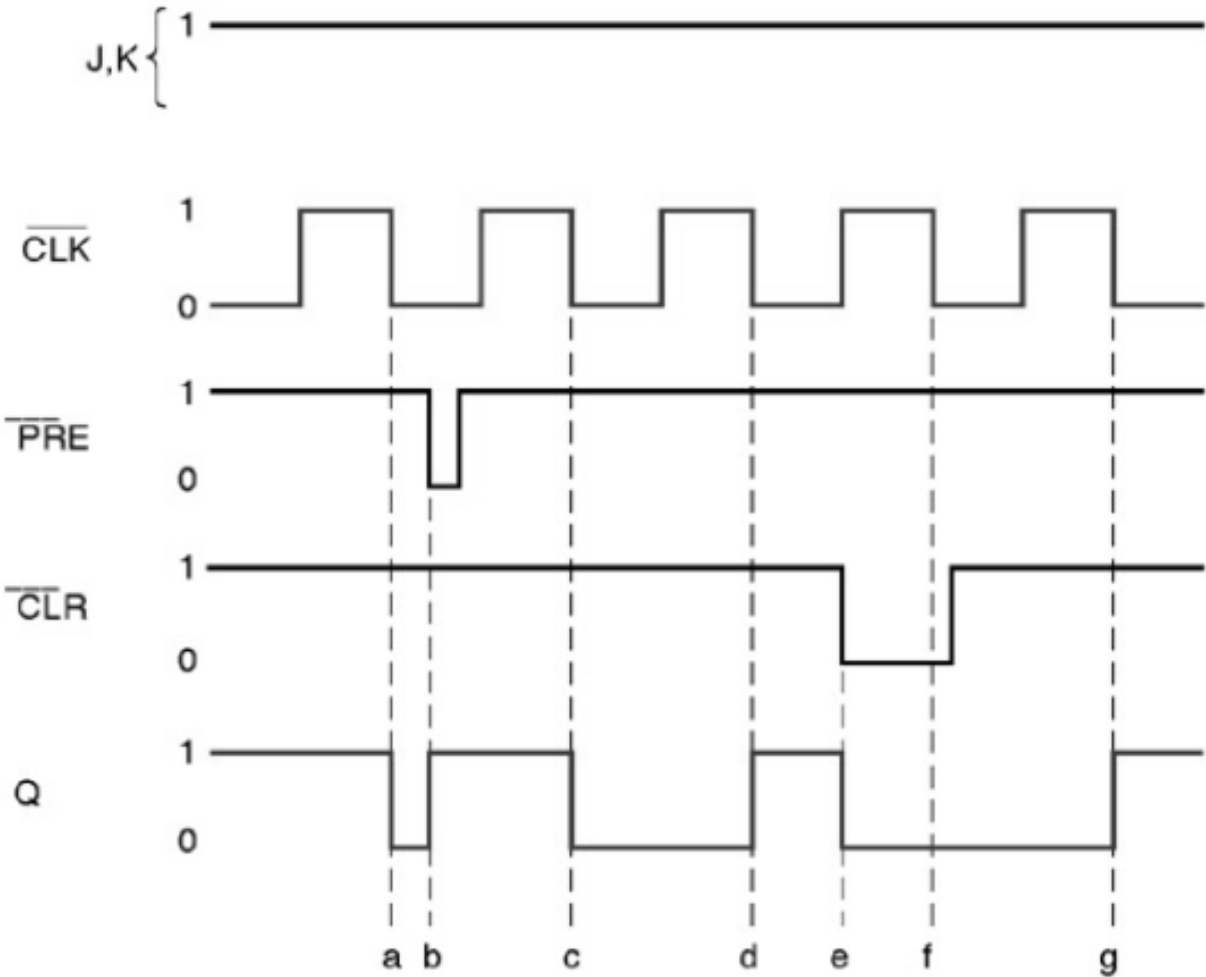 Exercise J-K FF with $\overline{\text{PRE}}$, $\overline{\text{CLR}}$, $\overline{\text{CLK}}$




(a)

 Exercise J-K FF with $\overline{\text{PRE}}$, $\overline{\text{CLR}}$, $\overline{\text{CLK}}$





 Exercise J-K FF with $\overline{\text{PRE}}$, $\overline{\text{CLR}}$, $\overline{\text{CLK}}$



  Exercise

Sketch the output waveform for the circuit.




Exercise

Sketch the output waveform for the circuit. Q is initially 0.



Q

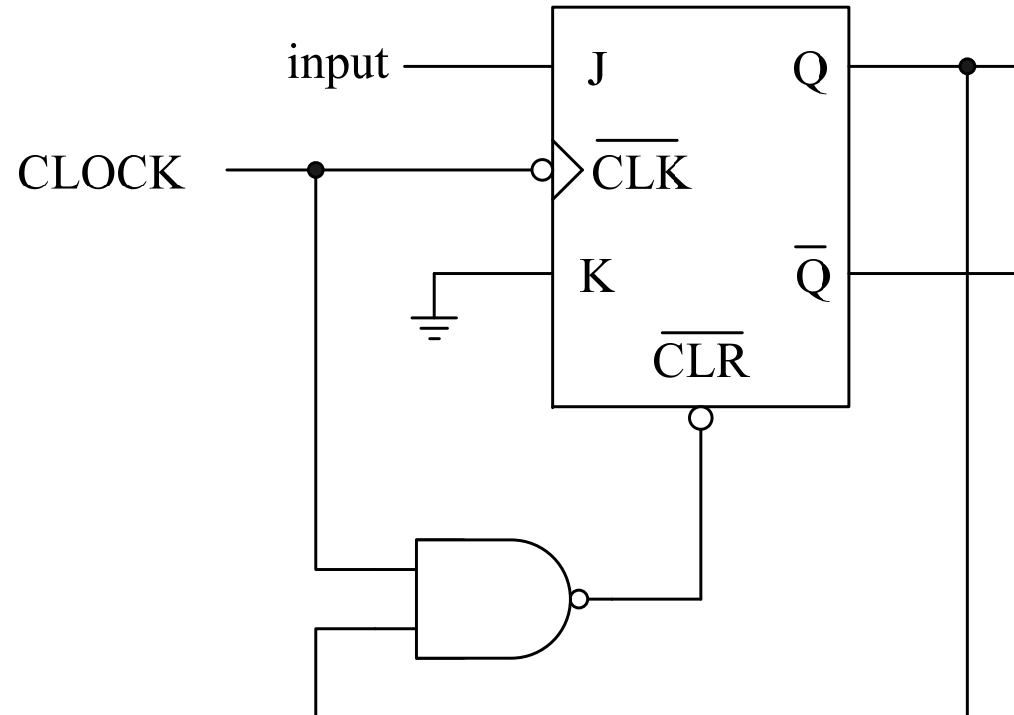

Solution Exercise

Sketch the output waveform for the circuit. Q is initially 0.

