

SKEE1223: Digital Electronics

14 – Programmable Logic Devices

Dr Michael Tan Loong Peng
PhD (Cambridge)
Senior Lecturer
Faculty of Electrical Engineering
Universiti Teknologi Malaysia

Lecture 14: Combinational Circuits

Programmable Logic Devices


- Programmable Logic Devices
- PN Diode Operation
 - ❖ AND Logic Arrays
 - ❖ OR Logic Arrays
 - ❖ Two-level AND-OR Arrays
- Programmable Logic Array (PLA)
- Realising Logic Functions with PLAs



Lecture 14

Programmable Logic Devices

 - Read-Only Memory (ROM)
- Programmable Read-Only Memory (PROM)
- Realising Logic Functions with PROMs
- Programmable Array Logic (PAL)
- Realising Logic Functions with PALs






Programmable Logic Devices

- **Programmable Logic Devices** (PLDs) are IC chips with internal logic gates connected by electronic fuses.
- These fuses can be 'blown' (by programming) to obtain different circuit configurations.
- Semi-customized chips that give high packing density at reasonable cost.
- Three classes of PLDs are :
 - ❖ Programmable Logic Array (PLA)
 - ❖ Programmable Read Only Memory (PROM)
 - ❖ Programmable Array Logic (PAL)




Programmable Logic Devices

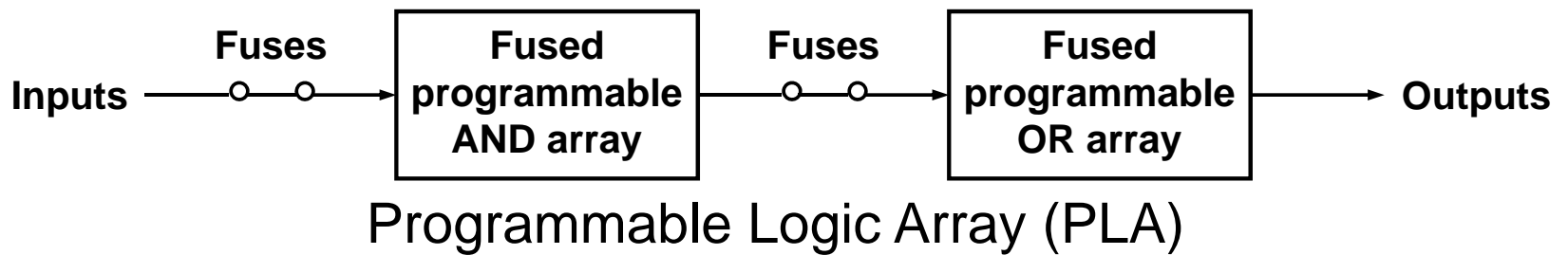 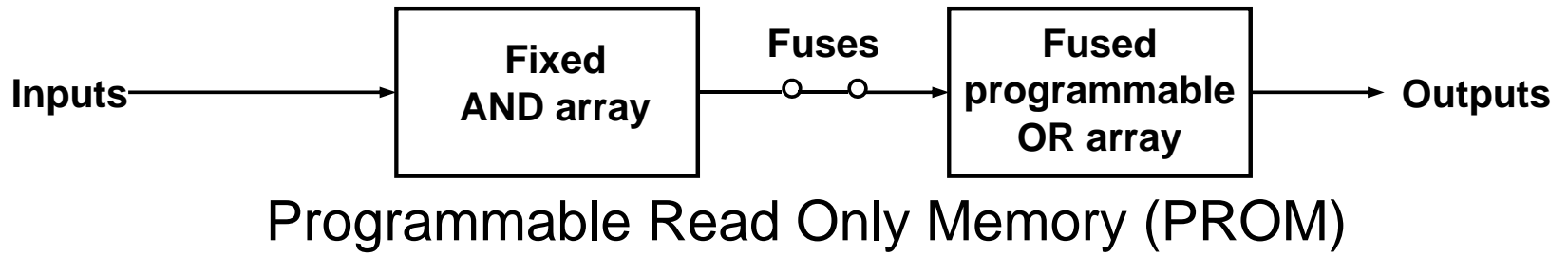


Programmable Logic Devices

 - “Programming” an array – blowing the fuses.



(a) Unprogrammed

 


(b) Programmed

 Example of a basic AND array





Programmable Logic Devices







- PLDs use diodes. A *PN diode* is an electronic device formed by creating a junction of two types of semiconductor materials, *p* type and *n* type.
 - ❖ *Forward-biased*: When *p* side (anode) is more positive than *n* side (cathode), it behaves as a closed switch.
 - ❖ *Reverse-biased*: When cathode is more positive than anode, it behaves as an open circuit.



PN junction diode and schematic symbol.

  

PN Diode Operation

      

PN diode operation for digital applications.

(a) With pull-up resistor.


(b) Reverse-biased: diode open; B pulled up to 1.

(c) Forward-biased: diode shorted, forcing B to 0.





(d) With pull-down resistor.

(e) Reverse-biased: diode open; B pulled down to 0.

 (f) Forward-biased: diode shorted, forcing B to 1.



AND Logic Arrays

    


AND function realised with a diode array.

(a) Basic configuration.




(c) One diode shorted, forcing f to 0.

(b) All diodes open; f pulled up to 1.

 (d) Multiple diodes shorted, forcing f to 0.



OR Logic Arrays

   

OR function realised with a diode array.


- (a) Basic configuration.
- (b) All diodes open; f pulled up to 0.
- (c) One diode shorted, forcing f to 1.



Two-level AND-OR Arrays

- AND and OR circuits can be interconnected to realise any arbitrary switching function.

Example: $f(a,b,c)=a.b.c'+b'.c$

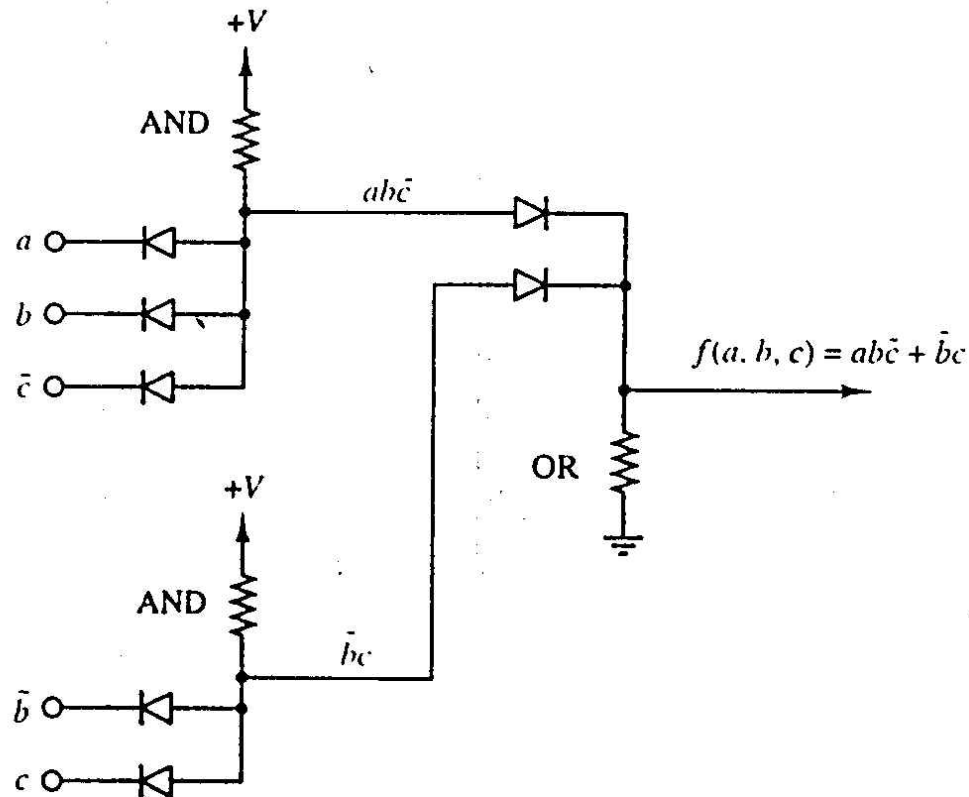

Programmable Logic Array (PLA)

- Combination of a programmable AND array followed by a programmable OR array.
- Example: Design a PLA to realise the following three logic functions and show the internal connections.

$$f_1(A,B,C,D,E) = A'.B'.D' + B'.C.D' + A'.B.C.D.E'$$

$$f_2(A,B,C,D,E) = A'.B.E + B'.C.D'.E$$

$$f_3(A,B,C,D,E) = A'.B'.D' + B'.C'.D'.E + A'.B.C.D$$




Realising Logic Functions with PLAs

$$f_1(A,B,C,D,E) = A'.B'.D' + B'.C.D' + A'.B.C.D.E'$$


$$f_2(A,B,C,D,E) = A'.B.E + B'.C.D'.E$$
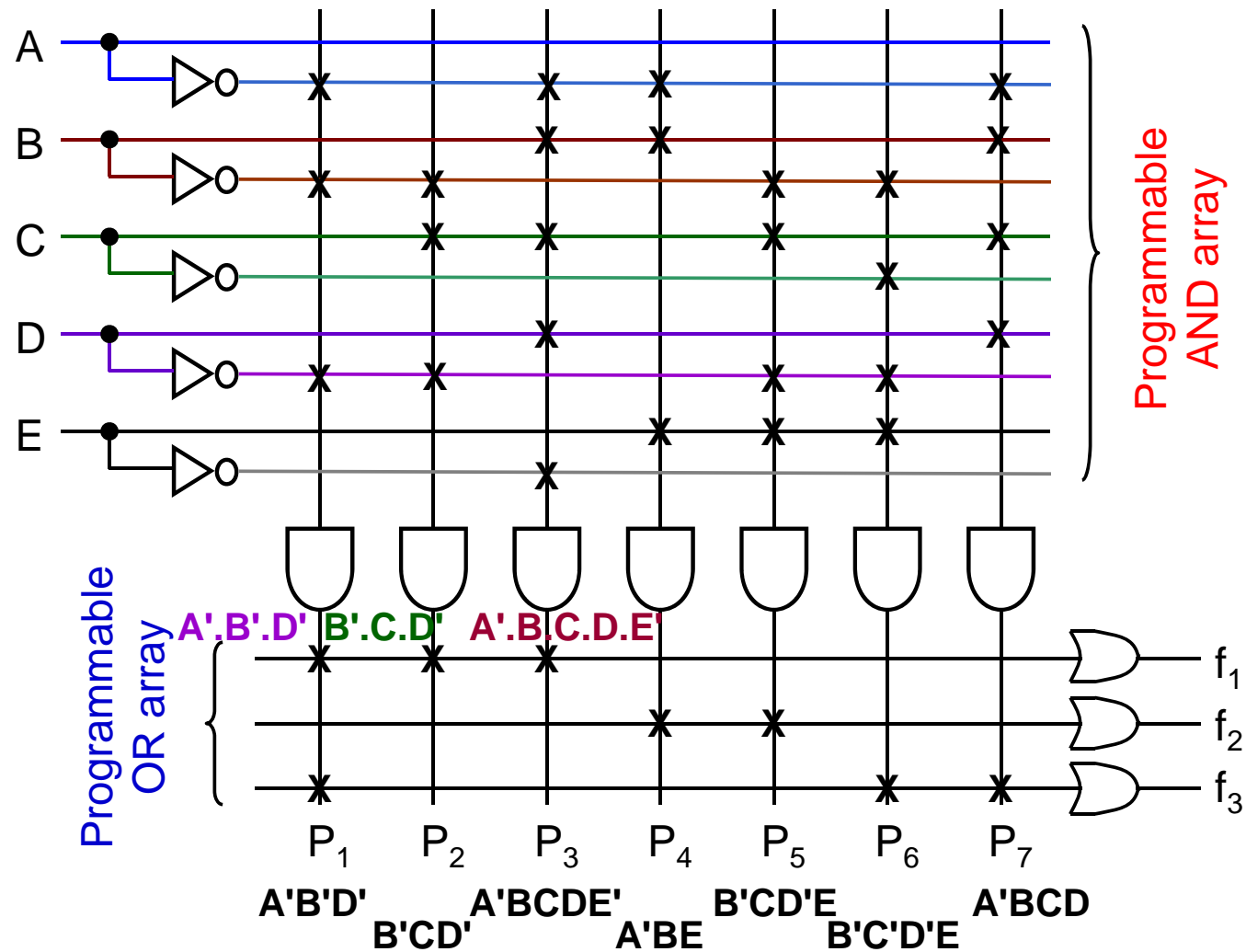
$$f_3(A,B,C,D,E) = A'.B'.D' + B'.C'.D'.E + A'.B.C.D$$



Read-Only Memory (ROM)

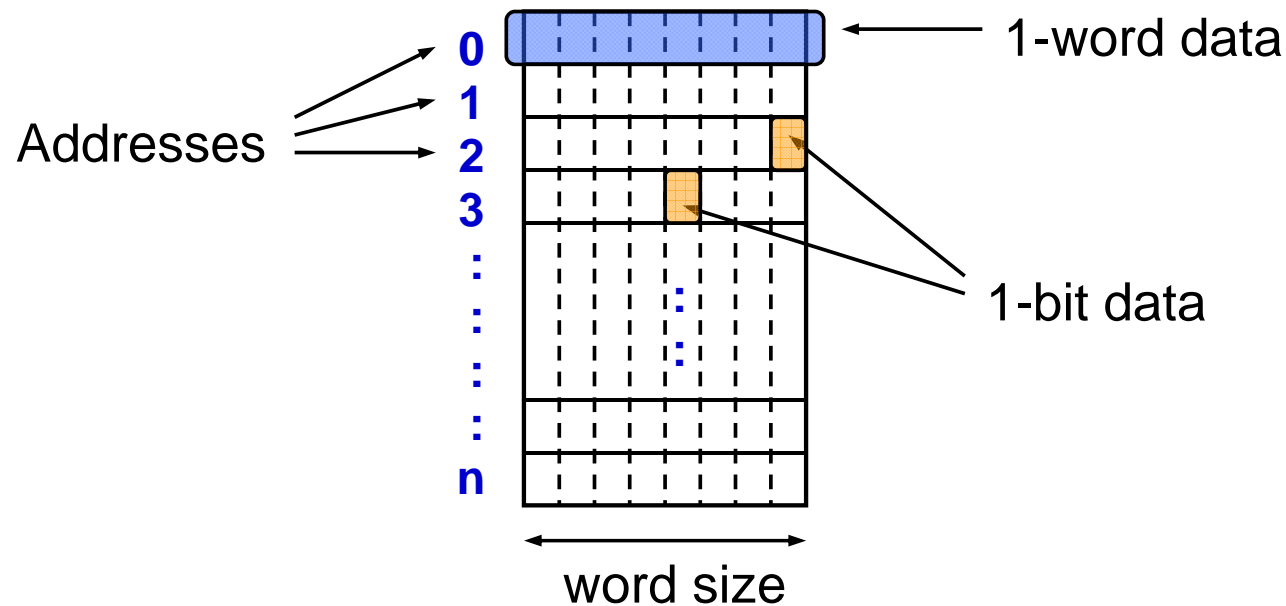- A semi-conductor memory is a device where data can be stored and retrieved.
- Logically, this memory device can be regarded as a table of memory cells (data).



Read-Only Memory (ROM)

- A **Read-Only Memory** (ROM) is a memory device where data are read from, but not written to.
- Writing is done at time of customisation, or, by special programming devices (programmable ROM).
- Any Boolean expression can be implemented using ROM. Procedure: Obtain a truth table, treat the inputs as addresses and outputs as data.
- Advantage: Boolean functions directly implemented.
- Disadvantages: Don't care conditions not used, and limited input variables (e.g. 10 inputs – 1K, 16 inputs – 64K, 20 inputs – 1M).



Read-Only Memory (ROM)

- Different types of ROM devices available:

- ❖ ROM: Read-Only Memory

Data written into memory by mask programming during manufacturing time. Expensive start-up cost but economical for high volume. Cannot be erased after data are programmed in.

- ❖ PROM: Programmable ROM

Semi-custom chip. Fuses can be broken by special hardware programmer unit. Cost-effective for low volumes. Cannot be erased after programming.



Read-Only Memory (ROM)

- ❖ **EPROM: Erasable PROM**

Similar to PROM except that data can be completely erased by exposure to ultra-violet light.

- ❖ **EEPROM: Electrically Erasable PROM**

A PROM where data can be selectively erased by hardware programmer unit, rather than by ultra-violet light. Useful for remote devices which can be re-programmed from a distance.




Programmable Read-Only Memory (PROM)


- Devices with fixed AND array (which is a decoder) and programmable OR array.
- The AND array (decoder) generates all 2^n possible minterm products of its n inputs (often referred to as n -to- 2^n decoder).
- n input lines, m output lines.
- Bit combination of input variables – **address**.
- Bit combination of output lines – **word** (each word contains m bits).




Programmable Read-Only Memory (PROM)

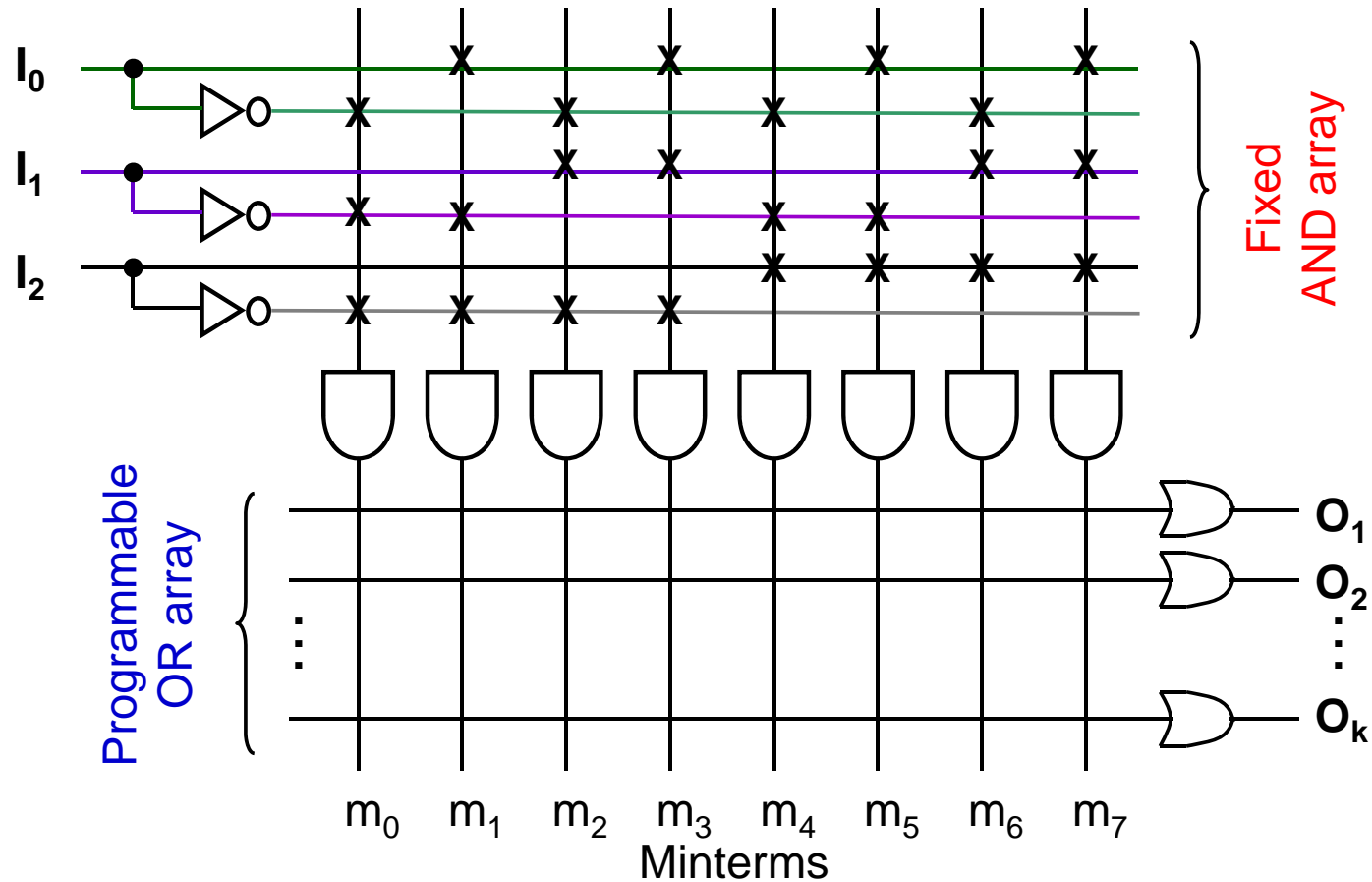

 Programmable read-only memory (PROM) can realize K functions $f(I_2, I_1, I_0)$.



Programmable Read-Only Memory (PROM)

 


$2^n \times m$ ROM

$\Rightarrow 2^n$ words, each word m bits


$\Rightarrow 2^n \times m$ bits



Programmable Read-Only Memory (PROM)

 

Logic construction of a 32 x 4 ROM.

 

Realising Logic Functions with PROMs

- Example (8 x 3 ROM):

$$f_1(A,B,C) = A.B + B'.C$$

$$f_2(A,B,C) = (A+B'+C).(A'+B)$$

$$f_3(A,B,C) = A + B.C$$

- First, we convert each function to canonical SOP form.



$$\begin{aligned} f_1(A,B,C) &= A.B + B'.C = A.B.C' + A.B.C + A'.B'.C + A.B'.C \\ &= \Sigma m(1,5,6,7) \end{aligned}$$

$$\begin{aligned} f_2(A,B,C) &= (A+B'+C).(A'+B) \\ &= (A+B'+B).(A'+B+C').(A'+B+C) \\ &= \Pi M(2,4,5) = \Sigma m(0,1,3,6,7) \end{aligned}$$



$$\begin{aligned} f_3(A,B,C) &= A + B.C = A.B'.C' + A.B'.C + A.B.C' + A.B.C + A'.B.C \\ &= \Sigma m(3,4,5,6,7) \end{aligned}$$



Realising Logic Functions with PROMs

  

Realising Logic Functions with PROMs

 
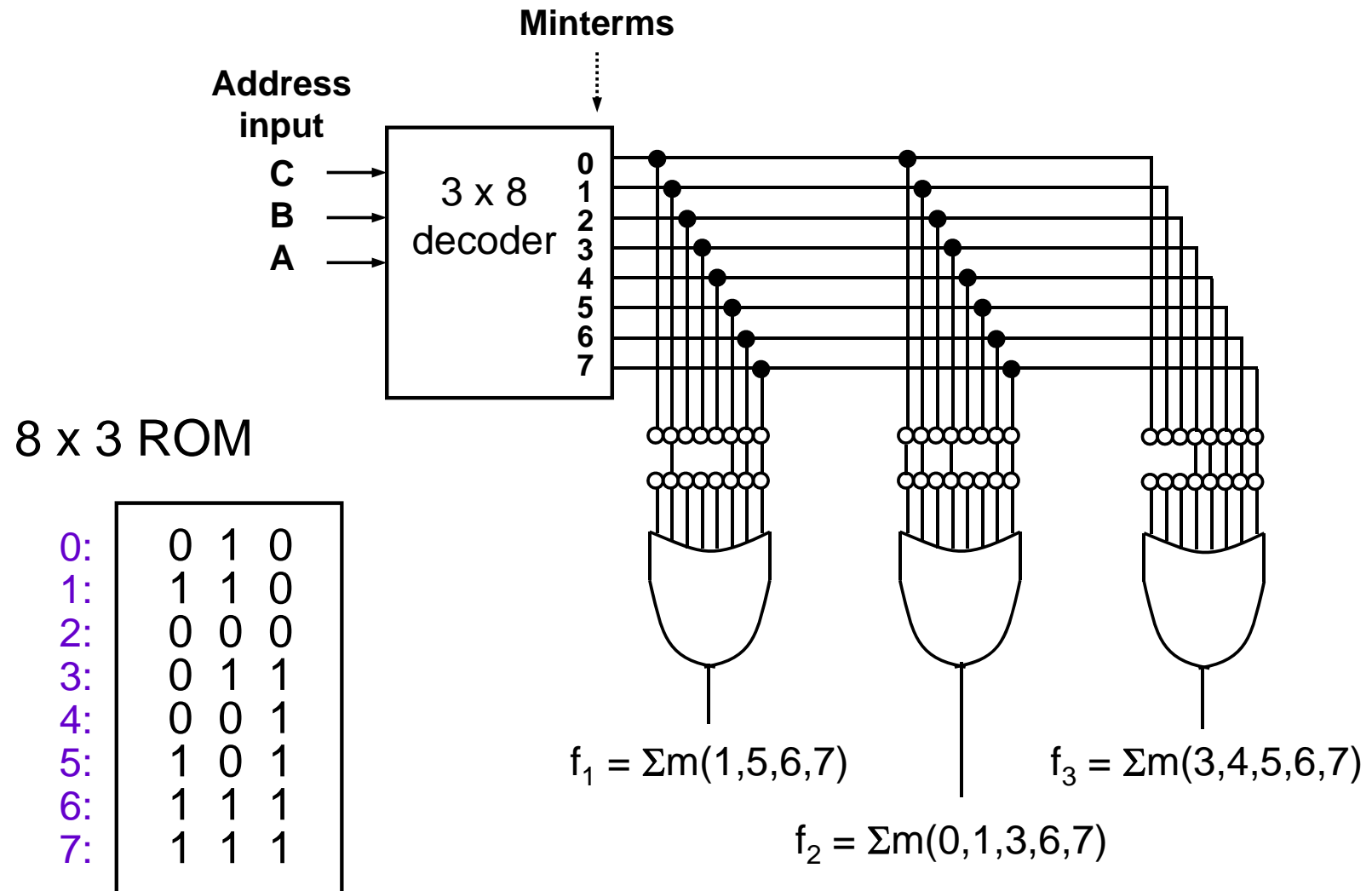


Programmable Array Logic (PAL)

- Introduced in late 1970s by Monolithic Memories Inc. as lower cost replacement for logic gates, PROMs, and PLAs.
- PAL has programmable AND array and fixed OR array.
- Less general than PLA but easier to manufacture and design.
- Product terms belong to different OR gates, cannot be shared.



Programmable Array Logic (PAL)

 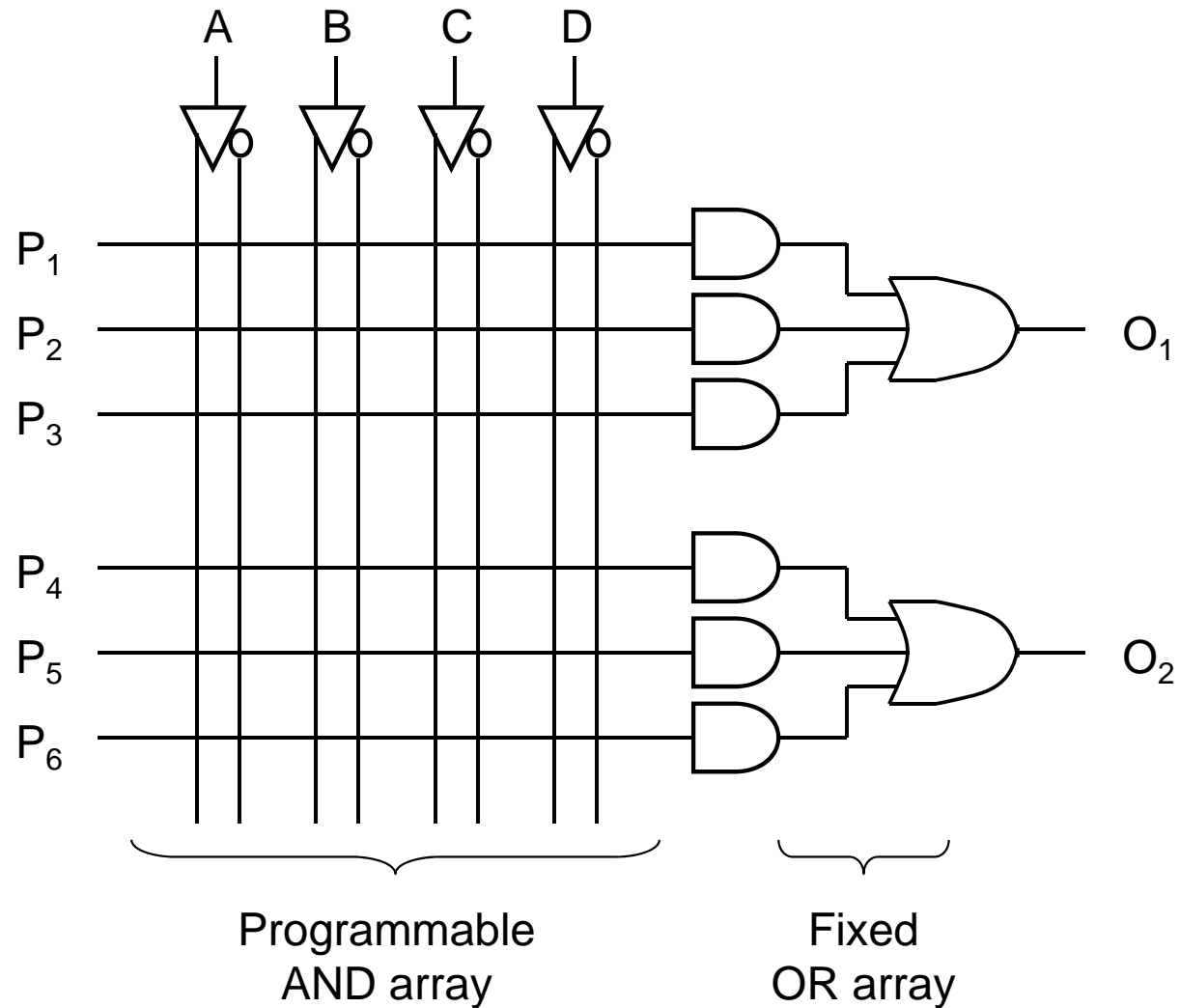

Realising Logic Functions with PALs

- Procedure is to obtain minimal SOP expressions.
- Example:

$$f_{\alpha}(A,B,C,D) = A'.B'.D' + B'.C.D' + A'.B.C.D$$

$$f_{\beta}(A,B,C,D) = A'.B + B'.C.D'$$

$$f_{\chi}(A,B,C,D) = A'.B'.D' + B'.C'.D' + A'.B.C.D$$




Realising Logic Functions with PALs

$$f_{\alpha}(A,B,C,D) = A'.B'.D' + B'.C.D' + A'.B.C.D$$

$$f_{\beta}(A,B,C,D) = A'.B + B'.C.D'$$

$$f_{\chi}(A,B,C,D) = A'.B'.D' + B'.C'.D' + A'.B.C.D$$

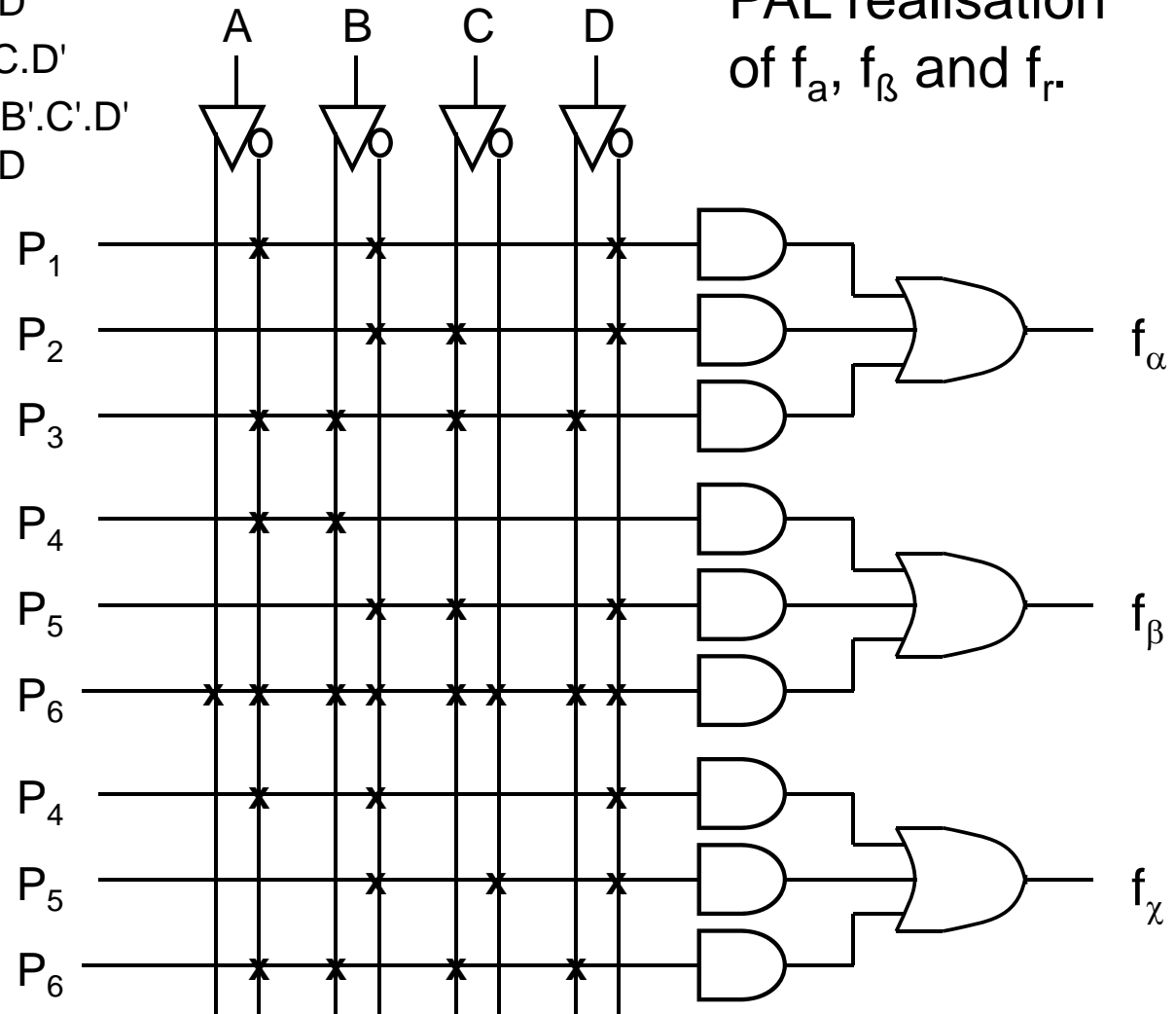PAL realisation of f_{α} , f_{β} and f_{χ}



End of segment

