

SKEE1223: Digital Electronics

5 – Logic Gates and Boolean Algebra



Dr Michael Tan Loong Peng
PhD (Cambridge)
Senior Lecturer
Faculty of Electrical Engineering
Universiti Teknologi Malaysia

Logic Gates and Boolean Algebra

- Logic Gates
 - Inverter, OR, AND, Buffer, NOR, NAND, XOR, XNOR
- Boolean Theorem
 - Commutative, Associative, Distributive Laws
 - Basic Rules
- DeMorgan's Theorem
- Universal Gates
 - NAND and NOR
- Canonical/Standard Forms of Logic
 - Sum of Product (SOP)
 - Product of Sum (POS)
 - Minterm and Maxterm

Standard Forms of Boolean Expressions

- Boolean expressions

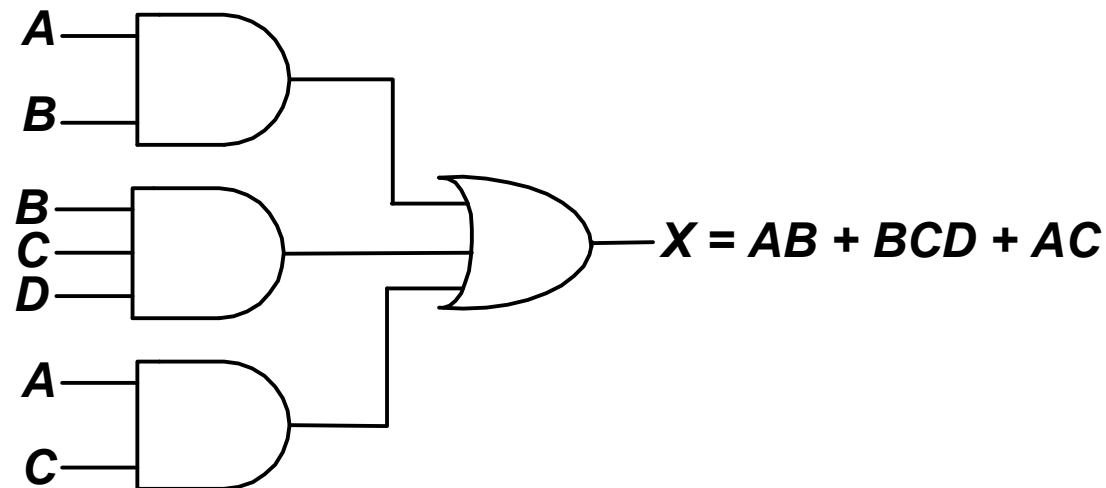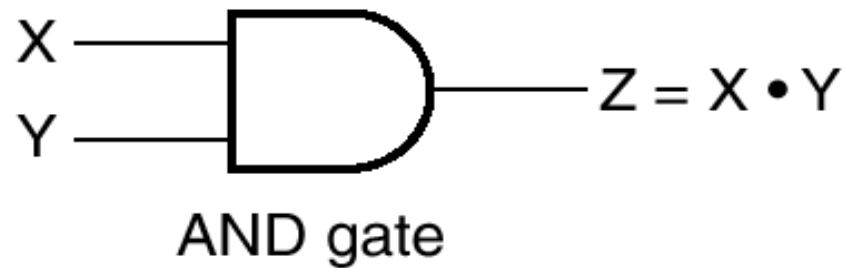


Standard forms of Boolean Expressions

- Two standard forms
 - Sum-of-products (SOP) form
 - Product-of-sums (POS) form
- Standardization
 - Evaluation, simplification and implementation of boolean expressions become more systematic, easy.

Sum-of-Products (SOP)

- Product term—a term that consists of the product of literals
- Sum-of-products—sum of two or more product terms

Example 1: $A\bar{B}C + BC + AC$

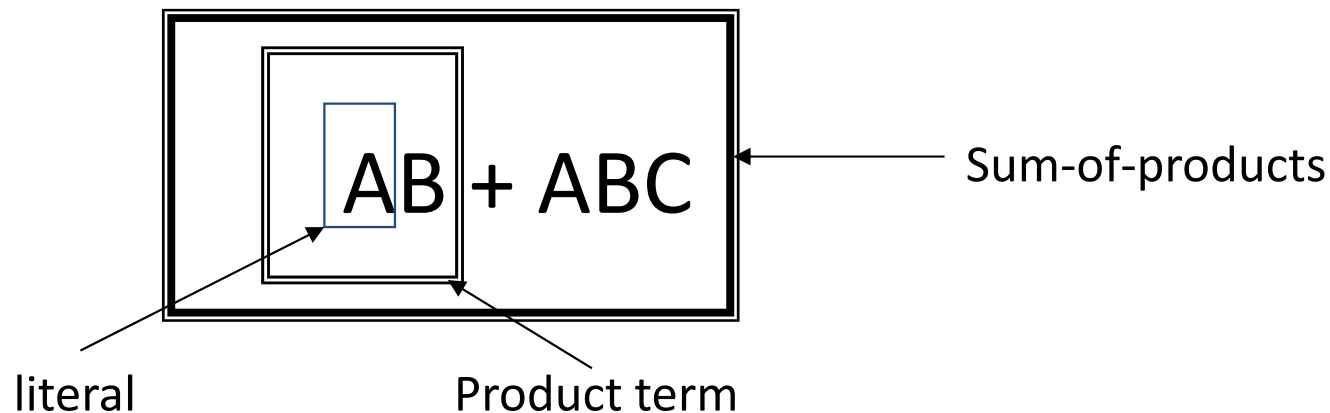

Sum of Product (SOP)

- Boolean expressions are expressed as the sum of product, example:

$$ABC + CDE + \overline{BC}D$$

minterm

literal

- Each variable or their complements is called *literals*
- Each product term is called *minterm*

Sum-of-Products (SOP)


- $A+BC$
- $\bar{A}\bar{B}+C\bar{D}$
- $\bar{A}\bar{B}\bar{C}+\bar{B}\bar{D}$
- $ABC+BD$

Domain of a SOP expression

- $\overline{A}B + A\overline{B}C$
 - Domain: A, B, C
- $ABC + CDE + \overline{B}C\overline{D}$
 - Domain: A, B, C, D, E
- $X + Y + XYZ$

AND/OR Implementation of an SOP expression

- $X = AB + BCD + AC$

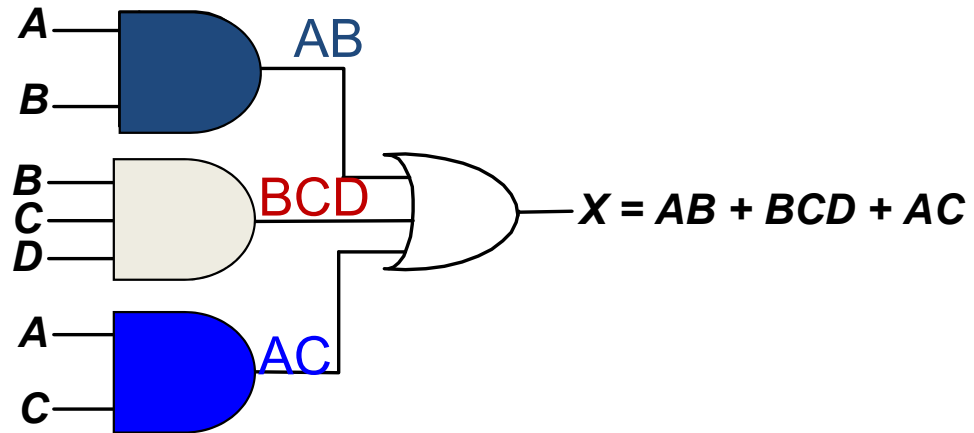

- $Y = A + BD + BC + CD$

Conversion of a general expressions to SOP form

- $A(B+CD) = AB + ACD$
- $(A+C)(AB+AC)=?$
- $AB + B(CD+EF)=?$

- $\overline{(A+B)}+C$

Canonical/Standard SOP Form

- SOP expressions
 - $\bar{A}BC+ABD+ABC\bar{D}$
 - Domain ?
- Standard SOP expression—an **expression** where **all** the **variables** in the **domain** appear in **each** of its **product term**.
- Examples: $\bar{A}\bar{B}\bar{C}+\bar{A}BC+\bar{A}BC$
 $\bar{X}YZ+XY\bar{Z}$

SOP (cont.)

- In SOP, a single overbar cannot extend over more than one variable, example:

$$AB + \overline{ABC} \leftarrow \text{Not SOP because } \overline{BC}$$

- *Standard SOP* forms must contain all of the variables in the domain of the expression for each product term, example:

$$\overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}} + \overline{A}\overline{B}\overline{C} + ABC$$

SOP (cont.)

- In the following SOP form,

$$\overline{A}BC + \overline{A}\overline{B} + AB\overline{C}D$$

- How many minterms are there? $\Rightarrow 3$
- How many literals in the second product term? $\Rightarrow 2$
- Is it in a standard SOP form? \Rightarrow No
- How do we convert the boolean expression to standard SOP form?

Conversion to Canonical/Standard SOP

Example: $A+B$

- **Step 1: Multiply each non-standard term with 1.**

$$A + B = A \bullet 1 + B \bullet 1$$

- **Step 2: Replace 1 with sum of the missing variable and its complement**

$$A + B = A(B + \bar{B}) + B(A + \bar{A})$$

- **Ans:**

$$\begin{aligned} A + B &= AB + A\bar{B} + AB + \bar{A}B \\ &= AB + A\bar{B} + \bar{A}B \end{aligned}$$

SOP (cont.)

- To convert SOP to its standard form, we use the boolean rules

$$A + \bar{A} = 1$$

$$A(B + C) = AB + AC$$

- We have

$$\bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + AB\bar{C}D$$

- The first product term is missing the variable D, and the second product term is missing C and D

SOP (cont.)

$$\overline{A}BC + \overline{A}\overline{B} + ABC\overline{D}$$

Apply $D + \overline{D} = 1$ and $C + \overline{C} = 1$

$$= \overline{A}BC(D + \overline{D}) + \overline{A}\overline{B}(C + \overline{C})(D + \overline{D}) + ABC\overline{D}$$

Apply the distributive law

$$= \overline{A}BCD + \overline{A}BC\overline{D} + (\overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C})(D + \overline{D}) + ABC\overline{D}$$

$$= \overline{A}BCD + \overline{A}BC\overline{D} + \overline{A}\overline{B}CD + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} +$$

$$\overline{A}\overline{B}\overline{C}\overline{D} + ABC\overline{D} \longleftarrow \text{Standard SOP form}$$

Exercise

a. $\overline{A}BC + A\overline{B} + \overline{A}BC\overline{D}$

b. $\overline{W}XY + \overline{W}Y\overline{Z} + WX\overline{Y}$

Product-of-Sums (POS)

- Sum term—a term that consists of the sum of literals
- Product-of-sums—multiplication of two or more sum terms.
- Example 1: $(A + B)(\overline{A + B + C})$


- Example 2: Sum term?

$$\overline{A} + \overline{B} + \overline{C} \quad \boxed{\checkmark}$$

$$\overline{A + B + C} \quad \boxed{\times}$$

Product-of-Sums (POS)

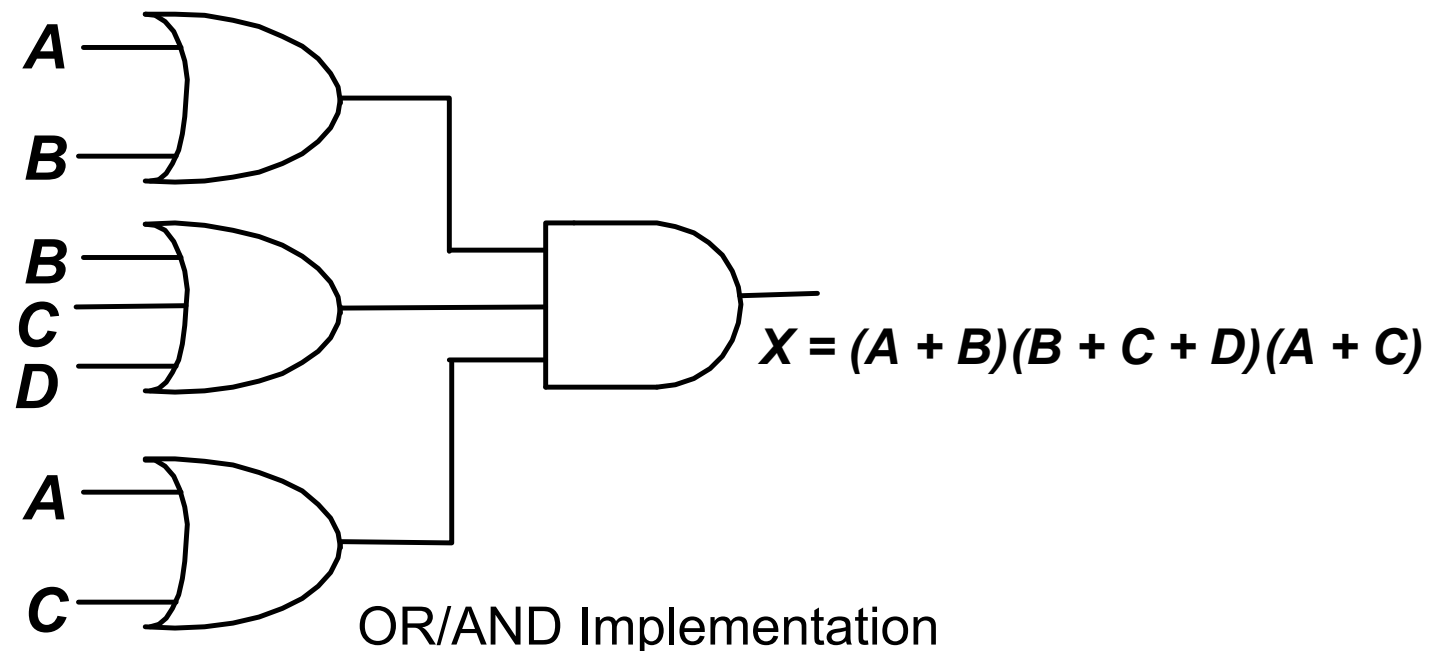- Implementation of the POS expression
- **(A + B)** **(B + C + D)** **(A + C)**



Product of Sum (POS)

- Boolean expressions are expressed as the product of sum, example:

$$(\bar{A} + B)(A + \bar{B} + C)$$

maxterm

literal

Domain of a POS expression

- $(A+B+C)(C+D+E)(B+C+D)$
 - Domain: A, B, C, D, E
- $(A+B)(A+B+C)(C+D)$
 - Domain: A, B, C, D
- $(U+T)(M+F+K)(T+E)(M)$
 - Domain:

POS (cont.)

- In POS, a single overbar cannot extend over more than one variable, example:

$$(\overline{A + B})(A + \overline{B + C}) \leftarrow \text{Not SOP because } \overline{B + C}$$

- *Standard POS* forms must contain all of the variables in the domain of the expression for each sum term, example:

$$(A + B + C)(A + B + \overline{C})(A + \overline{B} + C)$$

Canonical/Standard POS Expression

- An expression where all of the variables in the domain appear in each of its sum term.
- $(A+B+D)(A+B+C)$ is not a standard POS expression.
- Examples:
 - $(X+Y+Z)(X+Y+\overline{Z})$
 - $(\overline{U}+T+\overline{M})(U+\overline{T}+M)$

POS (cont.)

- In the following POS form,

$$(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

- Is it in a standard POS form? \Rightarrow No
- How do we convert the boolean expression to standard POS form?

Conversion to Canonical/Standard POS

Example: $(W+X+Y)(X+Y+Z)$

- **Step 1: Add 0 to each nonstandard product term.**

$$(W+X+Y+0)(X+Y+Z+0)$$

- **Step 2: Replace 0 by a product of the missing variable and its complement.**

$$(W+X+Y+Z\bar{Z})(X+Y+Z+W\bar{W})$$

- **Step 3: Apply rule 12: $A+BC=(A+B)(A+C)$**

$$(W+X+Y+Z)(W+X+Y+\bar{Z})(X+Y+Z+W)(X+Y+Z+\bar{W})$$

POS (cont.)

- To convert POS to its standard form, we use the boolean rules

$$A \cdot \bar{A} = 0$$

$$A + BC = (A + B)(A + C)$$

- We have

$$(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

- The first sum term is missing the variable D, and the second sum term is missing A

POS (cont.)

$$(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

Apply $D.\bar{D} = 0$ and $A.\bar{A} = 0$ to first and second terms

$$(A + \bar{B} + C + D.\bar{D})(A.\bar{A} + \bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

Expand first and second terms

$$(A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D})(A + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + C + \bar{D})$$

$$(A + \bar{B} + \bar{C} + D)$$

← Standard POS form

Exercise

a. $(\bar{A} + B + C)(A + \bar{B})(B + C)$

b. $(\bar{P} + Q)(\bar{P} + \bar{R} + S)$

Truth Table

- A common way of representing a logical operation of a circuit.
- If n is number of inputs, combinations in a truth table equals 2^n .
 - e.g. inputs is A,B,C, there will be $2^3=8$ combinations

| A | B | C | Output |
|---|---|---|--------|
| 0 | 0 | 0 | |
| 0 | 0 | 1 | |
| 0 | 1 | 0 | |
| 0 | 1 | 1 | |
| 1 | 0 | 0 | |
| 1 | 0 | 1 | |
| 1 | 1 | 0 | |
| 1 | 1 | 1 | |

SOP to Truth Tables

- Develop a truth table for the SOP expression

$$\bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$

- Domain = A, B, C : combinations = $2^3 = 8$
- What binary value makes the product term = 1?

| | |
|-------------------|-------------|
| $\bar{A}\bar{B}C$ | |
| 0 0 1 | = 1 1 1 = 1 |
| $A\bar{B}\bar{C}$ | |
| 1 0 0 | = 1 1 1 = 1 |
| ABC | |
| 1 1 1 | = 1 1 1 = 1 |

| INPUTS | | | OUTPUT | PRODUCT TERM |
|--------|---|---|--------|-------------------|
| A | B | C | X | |
| 0 | 0 | 0 | 0 | |
| 0 | 0 | 1 | 1 | $\bar{A}\bar{B}C$ |
| 0 | 1 | 0 | 0 | |
| 0 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 1 | $A\bar{B}\bar{C}$ |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |
| 1 | 1 | 1 | 1 | ABC |

- Fill the truth table

POS to Truth Tables

- Develop a truth table for the POS expression

$$(A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

- Domain = A, B, C. combinations = $2^3 = 8$
- What binary value makes the sum term = 0?

| | |
|-----------|-------------------|
| (A+B+C) | 0 0 0 = 0 |
| (A+B'+C) | 0 1 0 = 0 0 0 = 0 |
| (A+B'+C') | 0 1 1 = 0 0 0 = 0 |
| (A'+B+C') | 1 0 1 = 0 0 0 = 0 |
| (A'+B'+C) | 1 1 0 = 0 0 0 = 0 |

| INPUTS | | | OUTPUT | PRODUCT TERM |
|--------|---|---|--------|-------------------------------|
| A | B | C | X | |
| 0 | 0 | 0 | 0 | (A + B + C) |
| 0 | 0 | 1 | 1 | |
| 0 | 1 | 0 | 0 | (A + \bar{B} + C) |
| 0 | 1 | 1 | 0 | (A + \bar{B} + \bar{C}) |
| 1 | 0 | 0 | 1 | |
| 1 | 0 | 1 | 0 | (\bar{A} + B + \bar{C}) |
| 1 | 1 | 0 | 0 | (\bar{A} + \bar{B} + C) |
| 1 | 1 | 1 | 1 | |

- Fill the truth table

Boolean Expressions and Truth Tables

- **Step 1:** determine domain and combinations of binary values → input
- **Step 2:** convert expression to Standard SOP/POS.
- **Step 3:** find the binary values that make the product
 - Equal to 1 for SOP, e.g $ABC = 111$
 - Equal to 0 for POS, e.g $(A+B+C) = 000$
- **Step 4:** fill the remaining blanks with inverse values

Homework

- Make a truth table for the following functions:

a. $F = AB + A\bar{C}$

b. $F = (A + C)(B + \bar{C})$

Truth Table to SOP Form

- Can write SOP form of equation directly from truth table.

| A | B | C | F |
|---|---|---|-----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 ← A'BC |
| 1 | 0 | 0 | 1 ← AB'C' |
| 1 | 0 | 1 | 1 ← AB'C |
| 1 | 1 | 0 | 1 ← ABC' |
| 1 | 1 | 1 | 1 ← ABC |

Note that each term has ALL variables. If a product term has ALL variables present, it is a **MINTERM**.

$$F(A,B,C) = A'BC + AB'C' + AB'C + ABC' + ABC$$

Truth Table to **SOP** Form

- Can write POS form of equation directly from truth table.

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

← $A+B+C$

← $A+B+C'$

← $A+B'+C$

Note that each term has ALL variables. If a sum term has ALL variables present, it is a **MAXTERM**.

$$\mathbf{F(A,B,C) = (A+B+C) (A+B+C')(A+B'+C)}$$

Minterms and Maxterms

We saw that:

SOP

$$F(A, B, C) = \bar{A}BC + \bar{A}\bar{B}C + A\bar{B}C + \underbrace{AB\bar{C}} + ABC$$

form:

If a product term has all variables present, it is a

MINTERM.

POS

$$F(A, B, C) = (A + B + C)(\underbrace{A + B + \bar{C}})(A + \bar{B} + C)$$

form:

If a sum term has all variables present, it is a

MAXTERM.

All Boolean functions can be written in terms of either Minterms or Maxterms.

Using Minterms, Maxterms

A boolean function can be written in terms of Minterm or Maxterm notation as a shorthand method of specifying the function.

$$\begin{aligned}F(A,B,C) &= A'BC + AB'C' + AB'C + ABC' + ABC' + ABC \\ &= m_3 + m_4 + m_5 + m_6 + m_7 \\ &= \Sigma m(3,4,5,6,7)\end{aligned}$$

$$\begin{aligned}F(A,B,C) &= (A+B+C) (A+B+C')(A+B'+C) \\ &= M_0 M_1 M_2 \\ &= \Pi M(0,1,2)\end{aligned}$$

Minterms correspond to '1's of F, Maxterms correspond to '0's of F in truth table.

Minterms / Maxterms to Truth Table

Minterms correspond to '1's in Truth table

$$\begin{aligned}
 F(A,B,C) &= \Sigma m(1,2,6) \\
 &= m_1 + m_2 + m_6 \\
 &= A'B'C + A'BC' + ABC'
 \end{aligned}$$

| | A | B | C | F |
|---------|---|---|---|---|
| M_0 → | 0 | 0 | 0 | 0 |
| m_1 → | 0 | 0 | 1 | 1 |
| m_2 → | 0 | 1 | 0 | 1 |
| M_3 → | 0 | 1 | 1 | 0 |
| M_4 → | 1 | 0 | 0 | 0 |
| M_5 → | 1 | 0 | 1 | 0 |
| m_6 → | 1 | 1 | 0 | 1 |
| M_7 → | 1 | 1 | 1 | 0 |

Maxterms correspond to '0's in Truth table.

$$\begin{aligned}
 F(A,B,C) &= \Pi M(0,3,4,5,7) \\
 &= M_0 + M_3 + M_4 + M_5 + M_7 \\
 &= (A+B+C) (A+B'+C') (A'+B+C) (A'+B+C') (A'+B'+C')
 \end{aligned}$$

Minterms / Maxterms to Truth Table

Each line in a truth table represents both a Minterm and a Maxterm.

SOP

POS

| Row No. | A B C | Minterms | Maxterms |
|---------|-------|----------------|------------------|
| 0 | 0 0 0 | $A'B'C' = m_0$ | $A+B+C = M_0$ |
| 1 | 0 0 1 | $A'B'C = m_1$ | $A+B+C' = M_1$ |
| 2 | 0 1 0 | $A'BC' = m_2$ | $A+B'+C = M_2$ |
| 3 | 0 1 1 | $A'BC = m_3$ | $A+B'+C' = M_3$ |
| 4 | 1 0 0 | $AB'C' = m_4$ | $A'+B+C = M_4$ |
| 5 | 1 0 1 | $AB'C = m_5$ | $A'+B+C' = M_5$ |
| 6 | 1 1 0 | $ABC' = m_6$ | $A'+B'+C = M_6$ |
| 7 | 1 1 1 | $ABC = m_7$ | $A'+B'+C' = M_7$ |

Minterm and Maxterm

- Minterm: Product terms in SOP
- Maxterm: Sum terms in POS
- Standard forms of SOP and POS can be derived from truth tables

| A | B | C | Z |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

$$A + B + C$$

$$\overline{A}BC$$

$$A + \overline{B} + C$$

$$A + \overline{B} + \overline{C}$$

$$\overline{A} + B + C$$

$$\overline{A}BC$$

$$A\overline{B}C$$

$$ABC$$

For SOP form,

$$Z = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$

$$= \sum m(1,5,6,7)$$

For POS form,

$$Z = (A + B + C)(A + \overline{B} + C)$$


$$(A + \overline{B} + \overline{C})(\overline{A} + B + C)$$

$$= \prod M(0,2,3,4)$$

Minterm and Maxterm

- How to design minterms – AND-OR logic
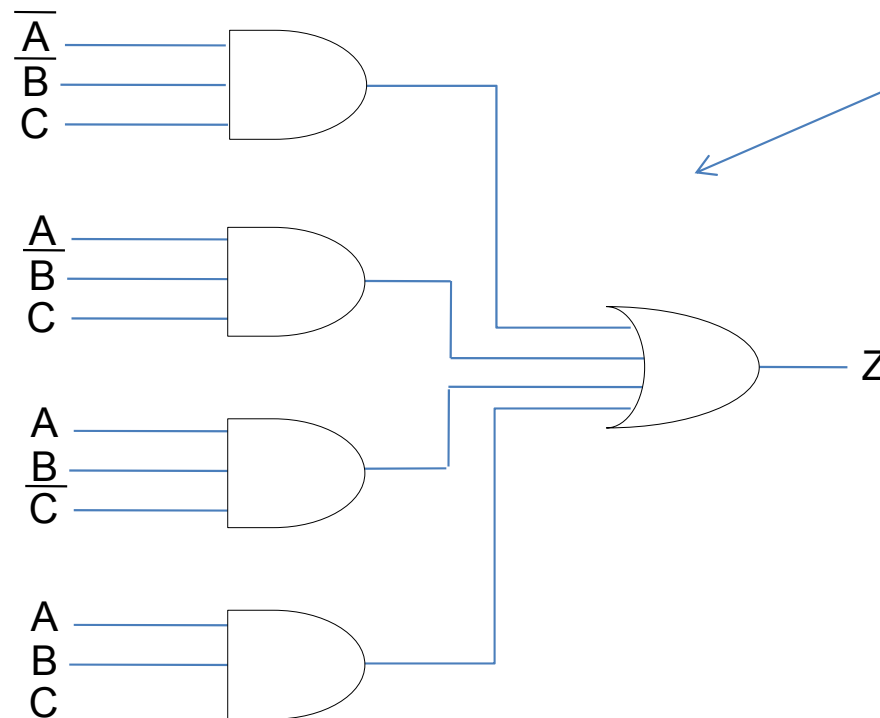
$$Z = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$




Also known as
2 level logic

Minterm and Maxterm

- How to design minterms – NAND-NAND Logic
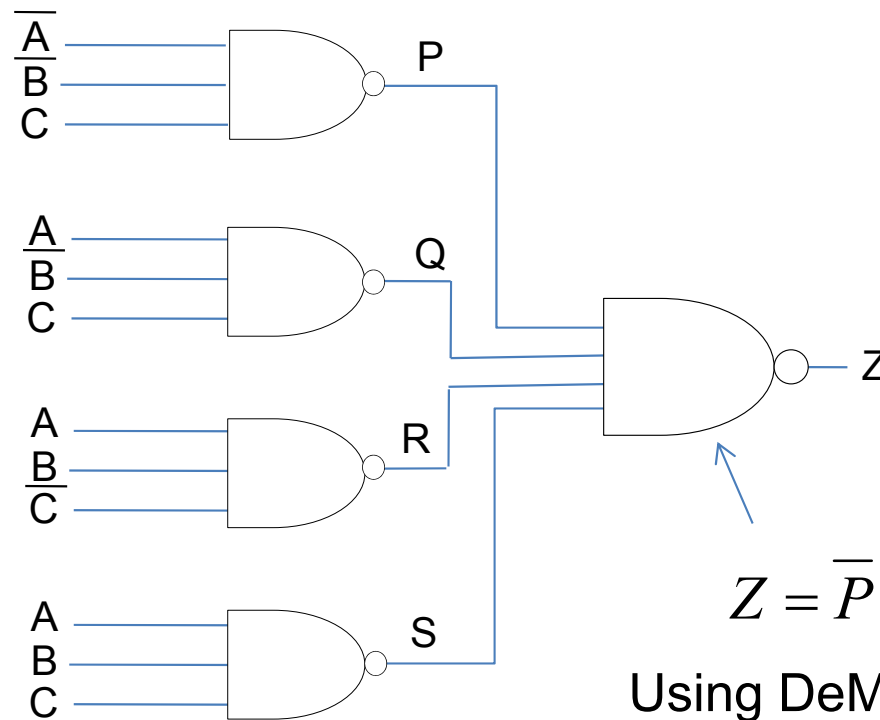
$$Z = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$



$$Z = \overline{P} + \overline{Q} + \overline{R} + \overline{S}$$


Using DeMorgan's Theorem

$$Z = \overline{P \cdot Q \cdot R \cdot S}$$

Minterm and Maxterm

- How to design maxterms – OR-AND Logic

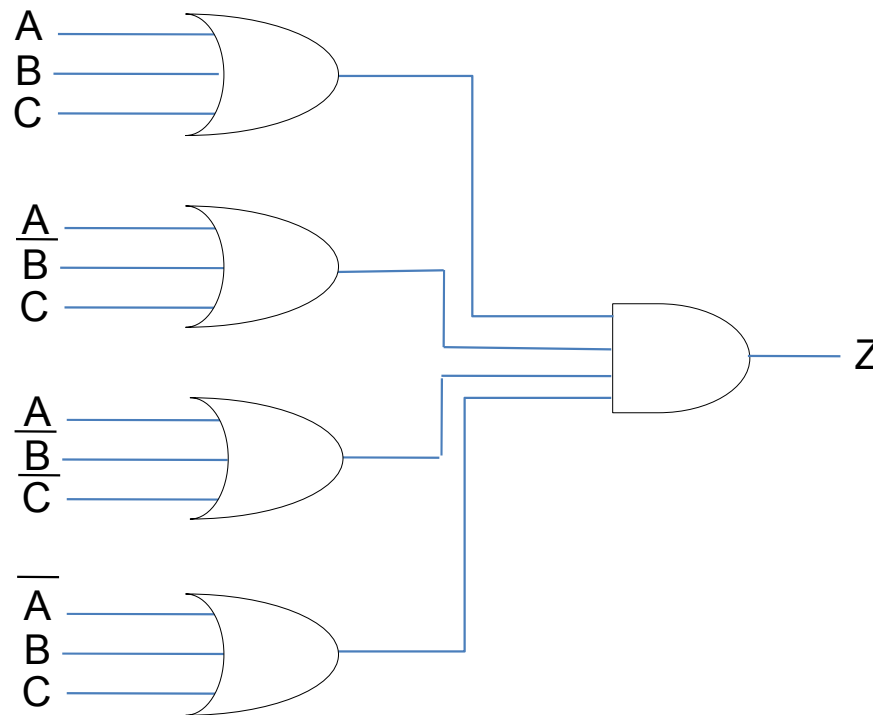
$$Z = (A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + C)$$



Minterm and Maxterm

- How to design maxterms – NOR-NOR Logic
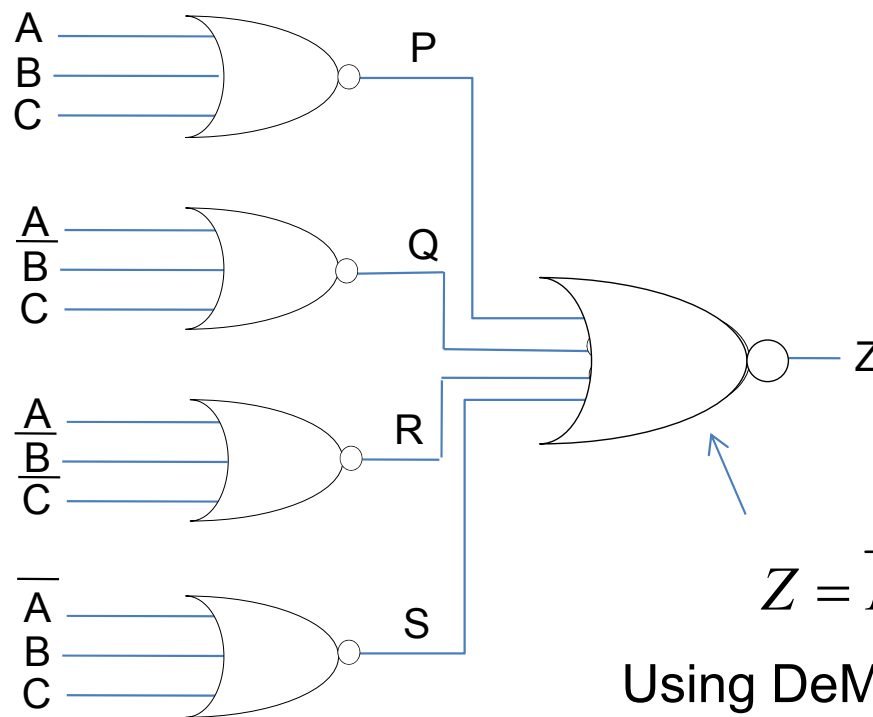
$$Z = (A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + C)$$



$$Z = \bar{P} \cdot \bar{Q} \cdot \bar{R} \cdot \bar{S}$$

Using DeMorgan's Theorem

$$Z = \overline{P + Q + R + S}$$

Minterm and Maxterm

- Can the minterm and maxterm logic be optimized?
 - Yes, using Boolean algebra – explore yourself
 - Yes, using Karnaugh maps – next lecture

Conversion of Circuits


Example :
$$F(A, B, C) = A.\bar{B} + B.C + \bar{A}.\bar{C}$$

This SOP function can be implemented using:

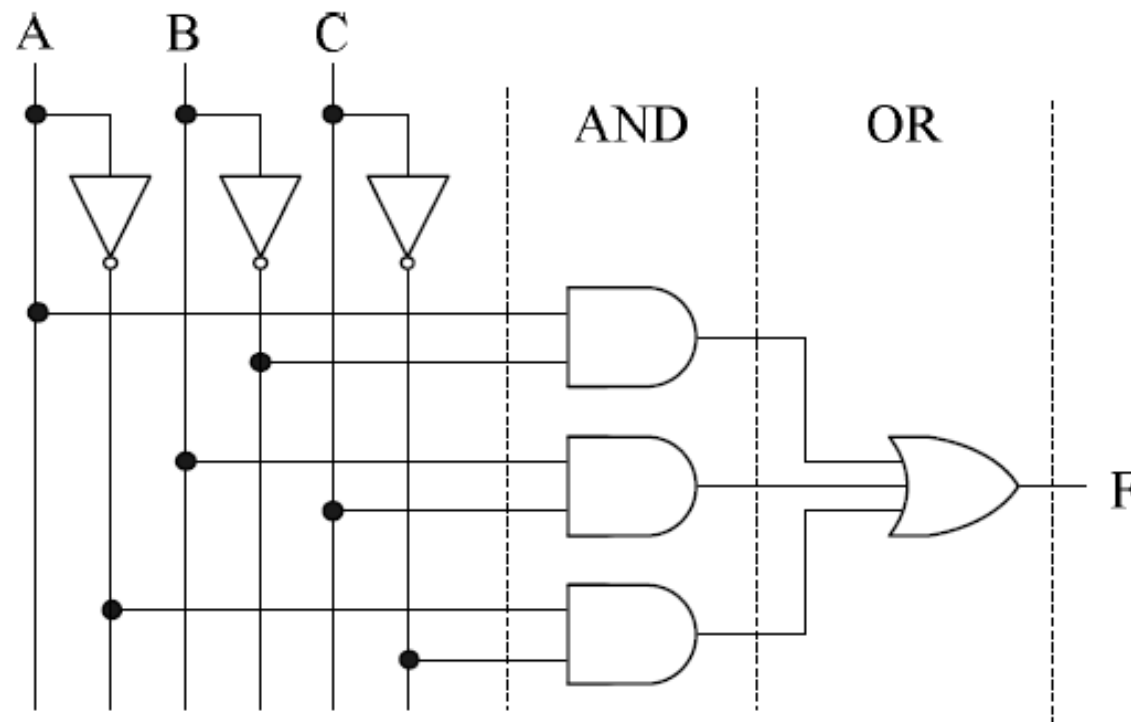- i. AND-OR circuit
- ii. NAND-NAND circuit

Conversion of Circuits

$$F(A, B, C) = A.\bar{B} + B.C + \bar{A}.\bar{C}$$




AND-OR circuit

Conversion of Circuits

$$F(A,B,C) = A\bar{B} + B.C + \bar{A}\bar{C} = \overline{\overline{A\bar{B} + B.C + \bar{A}\bar{C}}}$$
$$= \overline{(\overline{A\bar{B}})(\overline{B.C})(\overline{\bar{A}\bar{C}})}$$

Use DeMorgan's Theorem

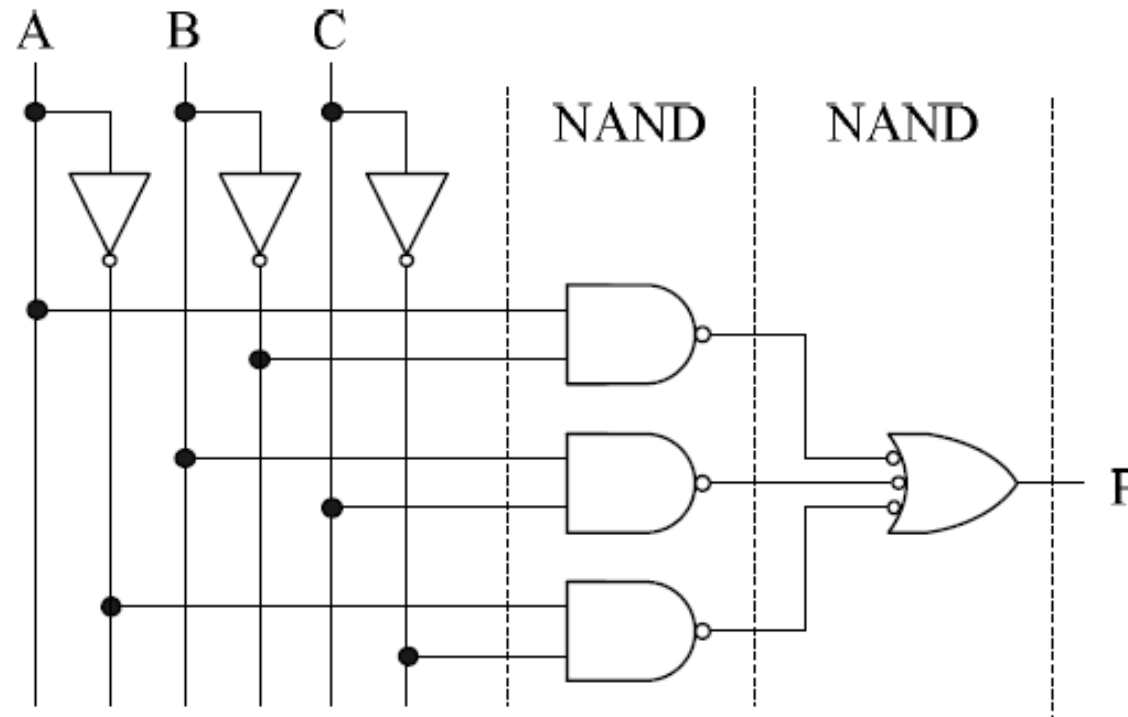

NAND-NAND circuit

Conversion of Circuits


Example: $F(A, B, C) = (\overline{A} + \overline{B} + C).(A + B + \overline{C})$

This POS function can be implemented using:

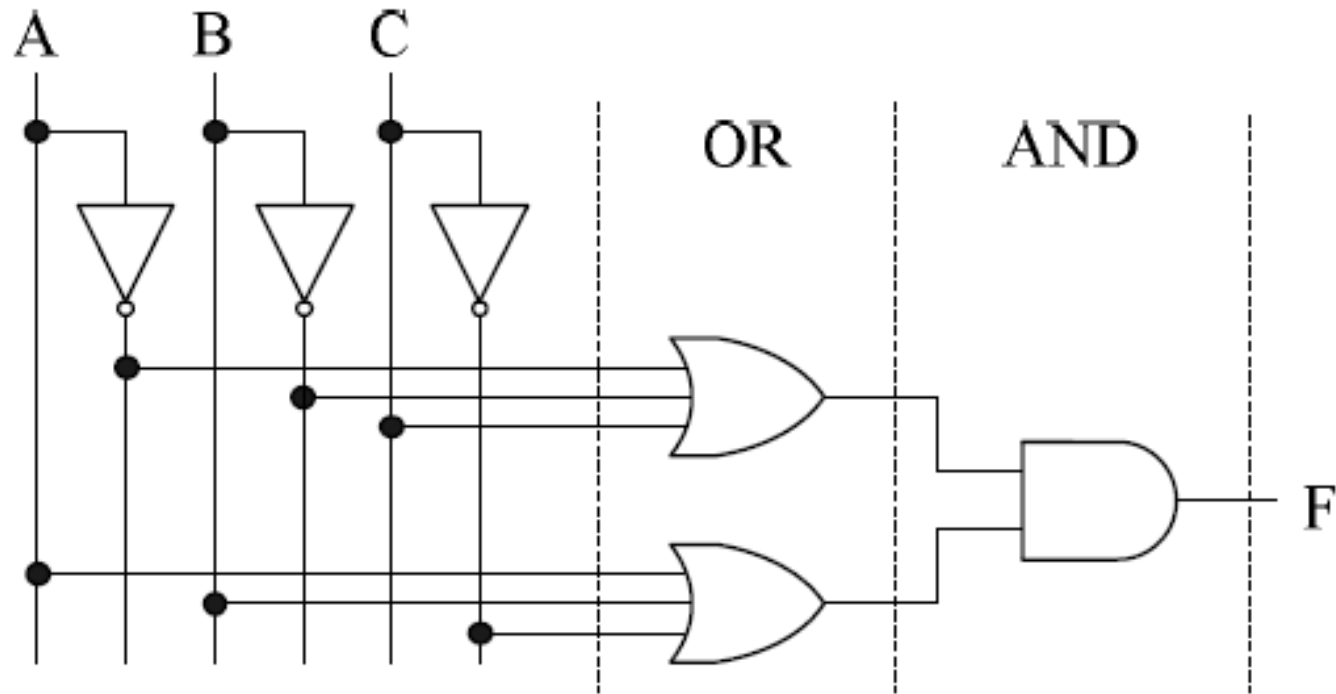- i. OR-AND circuit
- ii. NOR-NOR circuit

Conversion of Circuits


$$F(A, B, C) = (\bar{A} + \bar{B} + C) \cdot (A + B + \bar{C})$$



OR-AND circuit

Conversion of Circuits

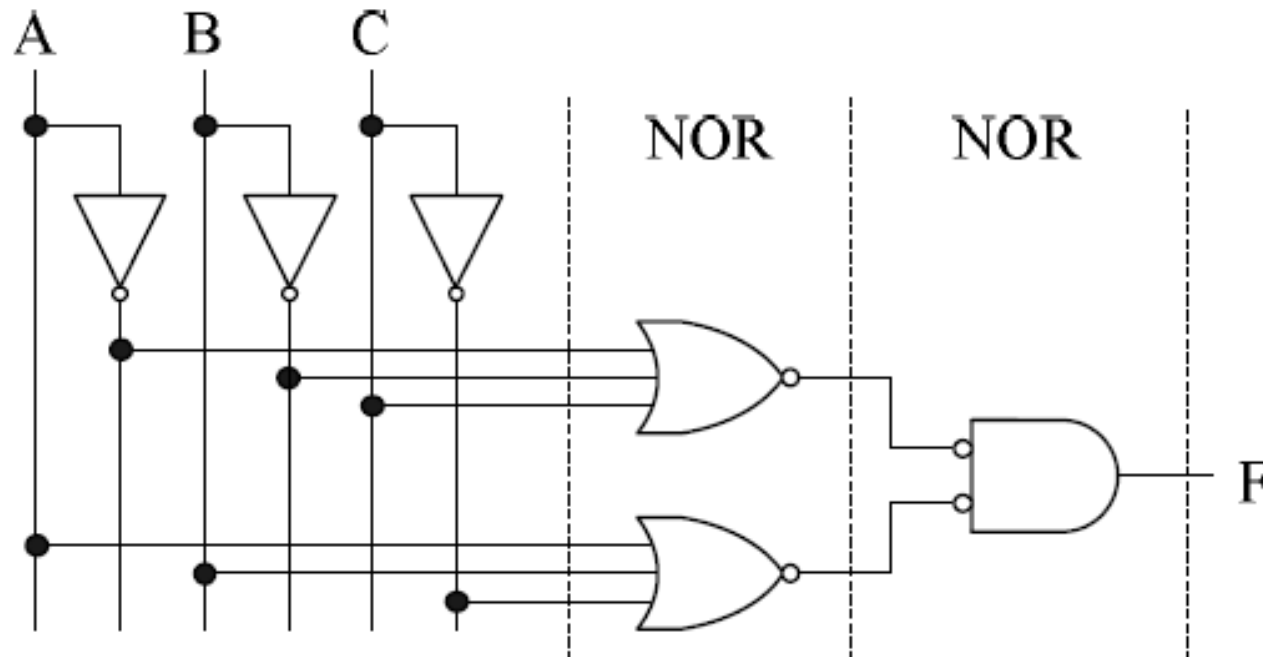
$$F(A,B,C) = (\bar{A} + \bar{B} + C) \cdot (A + B + \bar{C}) = \overline{\overline{(\bar{A} + \bar{B} + C)} \cdot \overline{(A + B + \bar{C})}}$$
$$= \overline{\overline{(\bar{A} + \bar{B} + C)} + \overline{(A + B + \bar{C})}}$$



NOR-NOR circuit

Conversion of Circuits
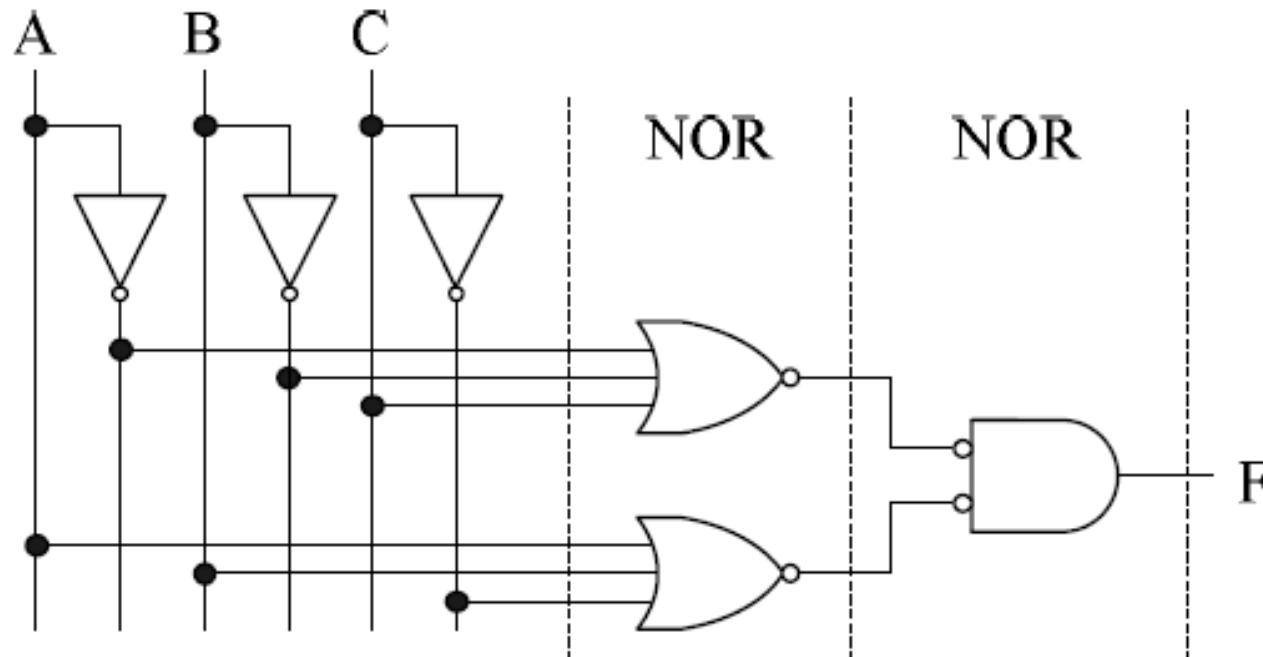
$$F(A,B,C) = (\bar{A} + \bar{B} + C) \cdot (A + B + \bar{C}) = \overline{\overline{(\bar{A} + \bar{B} + C)} \cdot \overline{(A + B + \bar{C})}}$$
$$= \overline{\overline{(\bar{A} + \bar{B} + C)} + \overline{(A + B + \bar{C})}}$$



NOR-NOR circuit

Conversion of Circuits


Example :
$$F(A, B, C) = A.\bar{B} + B.C + \bar{A}.\bar{C}$$

This SOP function can be implemented using:

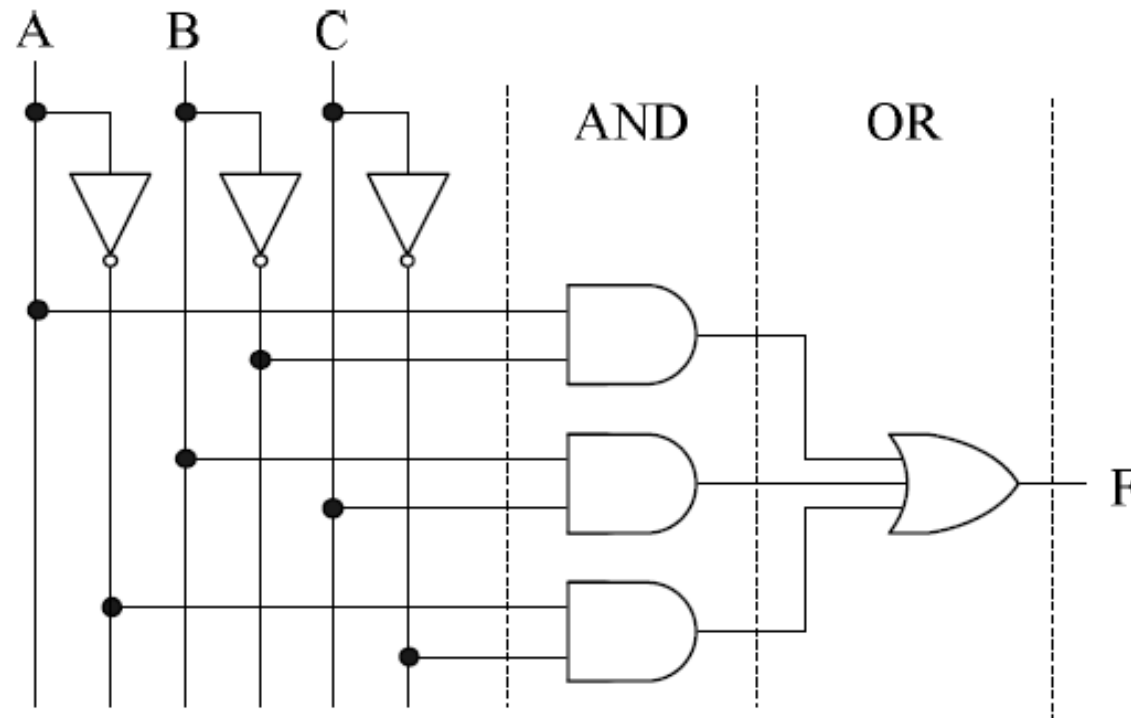- i. AND-OR circuit
- ii. NAND-NAND circuit

Conversion of Circuits

$$F(A, B, C) = A.\bar{B} + B.C + \bar{A}.C$$




AND-OR circuit

Conversion of Circuits

$$F(A,B,C) = A.\bar{B} + B.C + \bar{A}.\bar{C} = \overline{\overline{A.\bar{B} + B.C + \bar{A}.\bar{C}}}$$
$$= \overline{(\overline{A.\bar{B}}).\overline{(B.C)}.\overline{(\bar{A}.\bar{C})}}$$

Use DeMorgan's Theorem

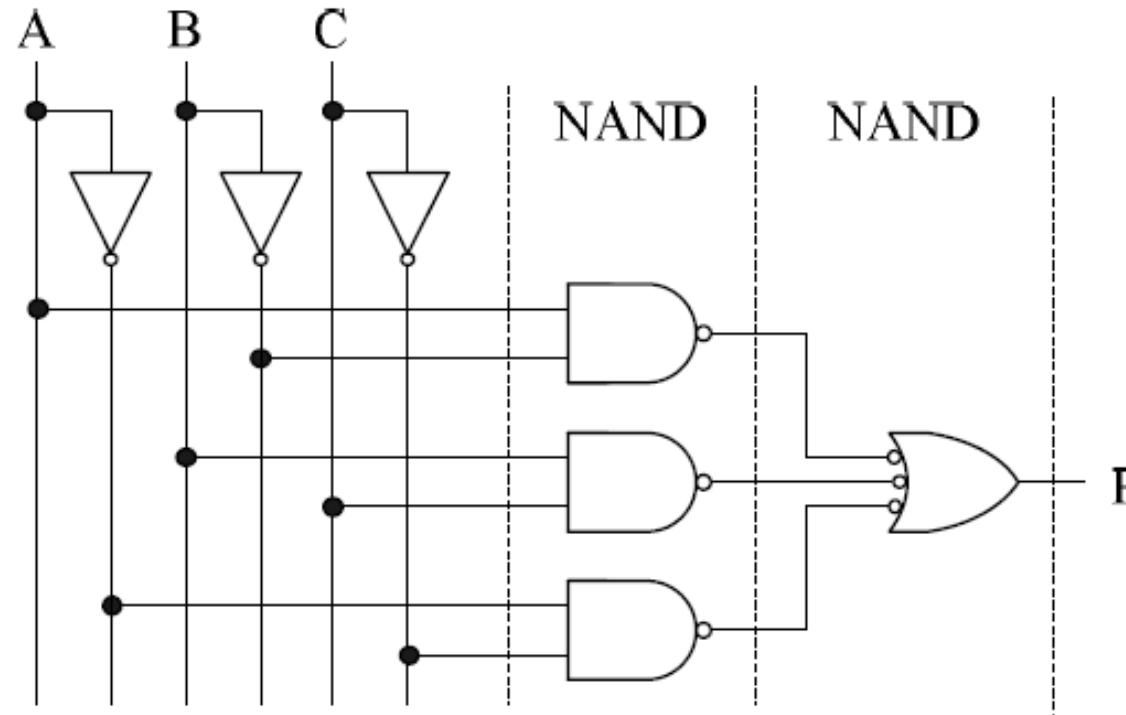

NAND-NAND circuit

Conversion of Circuits


Example: $F(A, B, C) = (\bar{A} + \bar{B} + C).(A + B + \bar{C})$

This POS function can be implemented using:

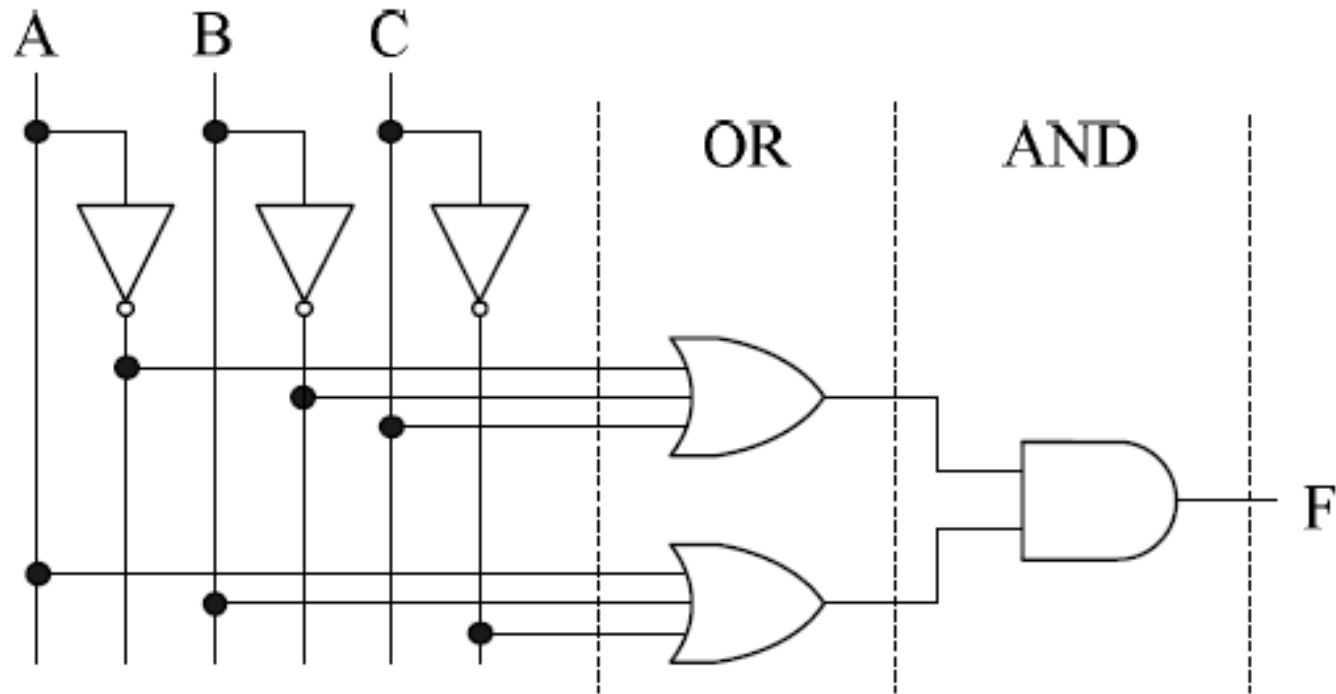- i. OR-AND circuit
- ii. NOR-NOR circuit

Conversion of Circuits


$$F(A, B, C) = (\bar{A} + \bar{B} + C).(A + B + \bar{C})$$



OR-AND circuit

Conversion of Circuits
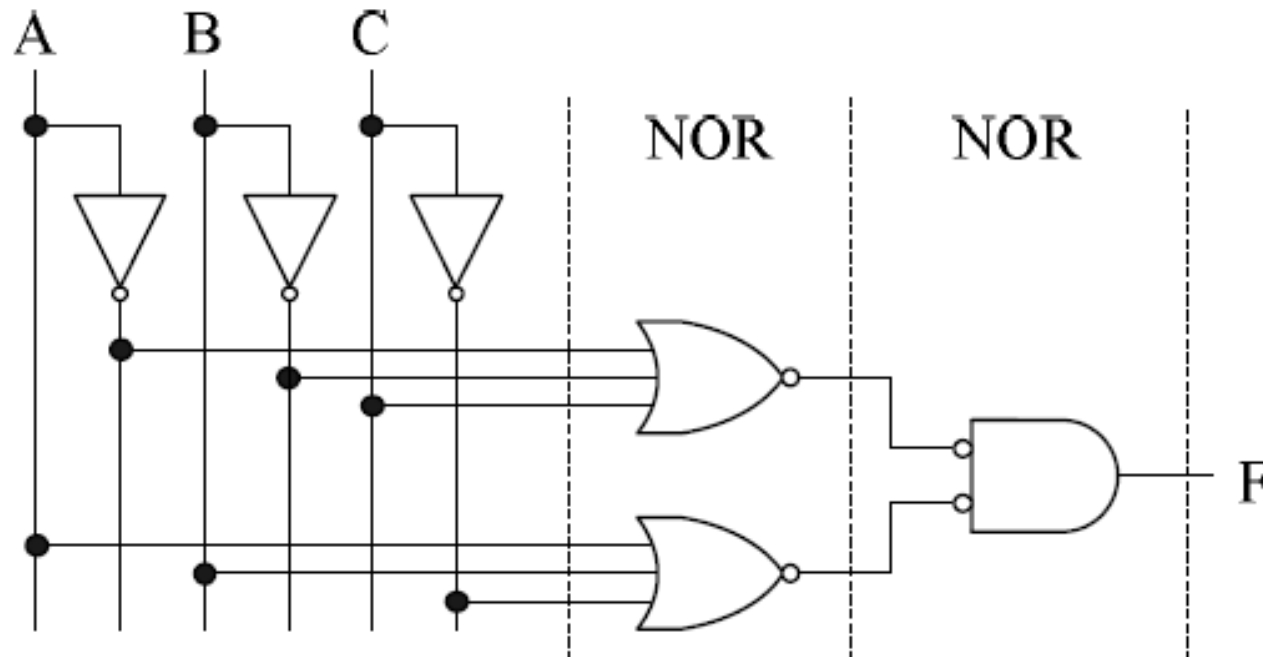
$$F(A,B,C) = (\bar{A} + \bar{B} + C) \cdot (A + B + \bar{C}) = \overline{\overline{(\bar{A} + \bar{B} + C)} \cdot \overline{(A + B + \bar{C})}}$$
$$= \overline{\overline{(\bar{A} + \bar{B} + C)} + \overline{(A + B + \bar{C})}}$$



NOR-NOR circuit