

SKEE1223: Digital Electronics

9 – Medium Scale Integrated (MSI) Circuits


Dr Michael Tan Loong Peng
PhD (Cambridge)
Senior Lecturer
Faculty of Electrical Engineering
Universiti Teknologi Malaysia

MSI Circuits

- Multiplexers (Mux)
 - 2x1, 4x1, and 8x1 muxes
 - 74x151, 74x153, 74x157 devices
- Demultiplexers (Demux), Decoders, and Encoders
 - 74x138 and 74x139 decoders
 - Encoder, priority encoder and the 75x147 devices
 - BCD to 7-segment decoder and the 74x247 devices
 - Logic functions using muxes and decoders
- Adders and Comparators
 - Half, full and ripple carry adders
 - The 74x83 devices
 - Comparator and the 74x85 devices


Demultiplexer

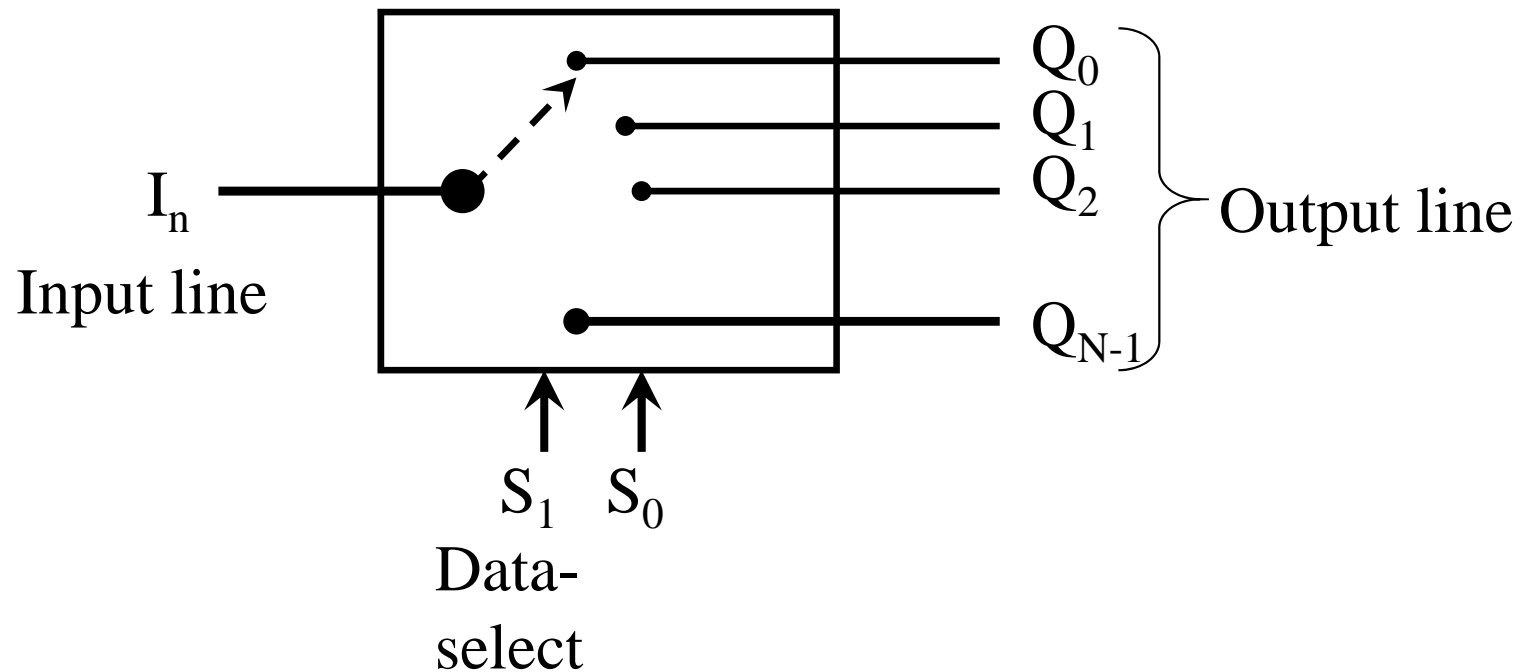- ◆ Demultiplexer (DEMUX) function is opposite to the MUX.
- ◆ It allows the single input line data to be routed to any output line.




Demultiplexer

 - ◆ DEMUX has only one input line (I_n) and several output lines ($Q_0, Q_1, Q_2, \dots, Q_{N-1}$).
- ◆ Data-select input (S_1 and S_0) is used to select which output line should be switched from the input line.



Demultiplexer

- ◆ 2-output Demultiplexer (1-2 DEMUX)

 


S	Q_1	Q_0
0	0	I_n
1	I_n	0

$$Q_0 = \bar{S} \cdot I_n$$

$$Q_1 = S \cdot I_n$$

Demultiplexer


- ◆ 4-output Demultiplexer (1-4 DEMUX)

 

$S_1 S_0 I_n$	Q_3	Q_2	Q_1	Q_0
0 0 0	0	0	0	0
0 0 1	0	0	0	1
0 1 0	0	0	0	0
0 1 1	0	0	1	0
1 0 0	0	0	0	0
1 0 1	0	1	0	0
1 1 0	0	0	0	0
1 1 1	1	0	0	0

Demultiplexer

 - ◆ 4-output Demultiplexer (1-4 DEMUX)-in simplified truth table



$S_1 S_0$	Q_3	Q_2	Q_1	Q_0
0 0	0	0	0	I_n
0 1	0	0	I_n	0
1 0	0	I_n	0	0
1 1	I_n	0	0	0

$$Q_0 = \bar{S}_1 \bar{S}_0 I_n$$


$$Q_2 = S_1 \bar{S}_0 I_n$$

$$Q_1 = \bar{S}_1 S_0 I_n$$


$$Q_3 = S_1 S_0 I_n$$

Demultiplexer

 - ◆ Design 8-output Demultiplexer (1-to-8 DEMUX)



 - ◆ Design 16-output Demultiplexer (1-to-16 DEMUX)




Demultiplexer

- ◆ Use 1-2 DEMUX to implement 1-4 DEMUX.
- ◆ Use 1-2 DEMUX to implement 1-8 DEMUX.
- ◆ Use 1-2 DEMUX to implement 1-16 DEMUX.
- ◆ Use 1-2 DEMUX and 1-4 DEMUX to implement 1-8 DEMUX.
- ◆ Use 1-4 DEMUX to implement 1-16 DEMUX.

Demultiplexer

 
- ◆ Use 74138 Decoder to Implement 1-8 DEMUX



- ◆ Use 74138 Decoder and NOT gate to Implement 1-16 DEMUX

Solution Demultiplexer

 - ◆ Use 74138 Decoder to Implement 1-8 DEMUX



Decoder

- ◆ Circuit that accepts a set of input (in binary number/code) and execute the output or a set of outputs corresponding to that particular input.
- ◆ For example, the 3-line-to-8-line '1-of-8' Decoder. For 1-of-8 Decoder only one output is activated at one time, corresponding to the input code. This decoder has an active-HIGH input and output.



Decoder


- ◆ Truth table for 1-of-8 Decoder

A	B	C	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
0	0	0	1							
0	0	1		1						
0	1	0			1					
0	1	1				1				
1	0	0					1			
1	0	1						1		
1	1	0							1	
1	1	1								1

- ◆ $Y0 = \bar{A}\bar{B}\bar{C}$
- ◆ $Y1 = \bar{A}\bar{B}C$

Decoder

- ◆ 1-of-8 Decoder logic circuit

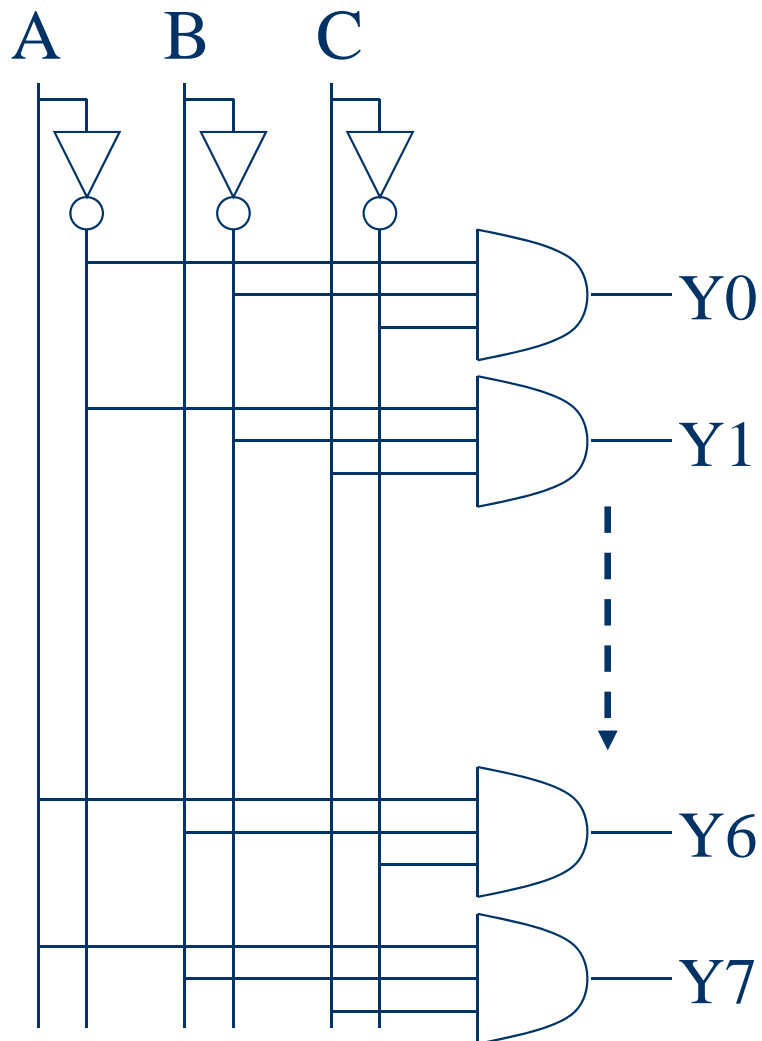


Decoder

- ◆ The 74138 Decoder (1-of-8 Decoder)
- ◆ Enable the input pin.
- ◆ Active low Enable, active low output

Dual 2-to-4 Decoder

Connection Diagram

 

Pin Description

Pin Names	Description
A_0, A_1	Address Inputs
\bar{E}	Enable Inputs
$\bar{O}_0-\bar{O}_3$	Outputs

Truth Table

Inputs			Outputs			
\bar{E}	A_0	A_1	\bar{O}_0	\bar{O}_1	\bar{O}_2	\bar{O}_3
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	H	L	H	L	H	H
L	L	H	H	H	L	H
L	H	H	H	H	H	L

H = HIGH Voltage Level


L = LOW Voltage Level

X = Immaterial

Decoders

◆ 2x4 Decoder

Active high output decoder

 

Function:

$$O_3 O_2 O_1 O_0 = 0001 \text{ when } A_1 A_0 = 00 \longrightarrow O0 = \overline{A1} \cdot \overline{A0}$$


$$O_3 O_2 O_1 O_0 = 0010 \text{ when } A_1 A_0 = 01 \longrightarrow O1 = \overline{A1} \cdot A0$$

$$O_3 O_2 O_1 O_0 = 0100 \text{ when } A_1 A_0 = 10 \longrightarrow O2 = A1 \cdot \overline{A0}$$

$$O_3 O_2 O_1 O_0 = 1000 \text{ when } A_1 A_0 = 11 \longrightarrow O3 = A1 \cdot A0$$

Decoders (cont.)

 - ◆ Decoders are typically designed as active low



Bubble at output denotes active low output

Function:

$$O_3 O_2 O_1 O_0 = 1110 \text{ when } A_1 A_0 = 00 \longrightarrow O_0 = \overline{\overline{A_1 \cdot A_0}}$$


$$O_3 O_2 O_1 O_0 = 1101 \text{ when } A_1 A_0 = 01 \longrightarrow O_1 = \overline{A_1 \cdot A_0}$$

$$O_3 O_2 O_1 O_0 = 1011 \text{ when } A_1 A_0 = 10 \longrightarrow O_2 = A_1 \cdot \overline{A_0}$$

$$O_3 O_2 O_1 O_0 = 0111 \text{ when } A_1 A_0 = 11 \longrightarrow O_3 = \overline{A_1 \cdot A_0}$$

Decoders (cont.)

◆ 2x4 Decoder with active low enable

 

Function:

If ($E = 1$),

$$O_3 O_2 O_1 O_0 = 1111, A_1 A_0 = xx$$

If ($E = 0$),

$$O_3 O_2 O_1 O_0 = 1110 \text{ when } A_1 A_0 = 00$$

$$O_3 O_2 O_1 O_0 = 1101 \text{ when } A_1 A_0 = 01$$

$$O_3 O_2 O_1 O_0 = 1011 \text{ when } A_1 A_0 = 10$$

$$O_3 O_2 O_1 O_0 = 0111 \text{ when } A_1 A_0 = 11$$

Can you draw the logic circuit?

$$O_0 = \overline{\overline{E} \cdot \overline{A_1} \cdot \overline{A_0}}$$


$$O_1 = \overline{\overline{E} \cdot \overline{A_1} \cdot A_0}$$

$$O_2 = \overline{\overline{E} \cdot A_1 \cdot \overline{A_0}}$$

$$O_3 = \overline{\overline{E} \cdot A_1 \cdot A_0}$$

Decoders (cont.)

◆ 3x8 Decoder

 

Function:

$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1111\ 1110$ when $A_2 A_1 A_0 = 000$

$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1111\ 1101$ when $A_2 A_1 A_0 = 001$

$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1111\ 1011$ when $A_2 A_1 A_0 = 010$

$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1111\ 0111$ when $A_2 A_1 A_0 = 011$

$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1110\ 1111$ when $A_2 A_1 A_0 = 100$

$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1101\ 1111$ when $A_2 A_1 A_0 = 101$

$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1011\ 1111$ when $A_2 A_1 A_0 = 110$


$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 0111\ 1111$ when $A_2 A_1 A_0 = 111$

How does the logic circuit look like?

- Can we use K-Map?

Decoders (cont.)

- ◆ 74138 Single 3x8 Decoder

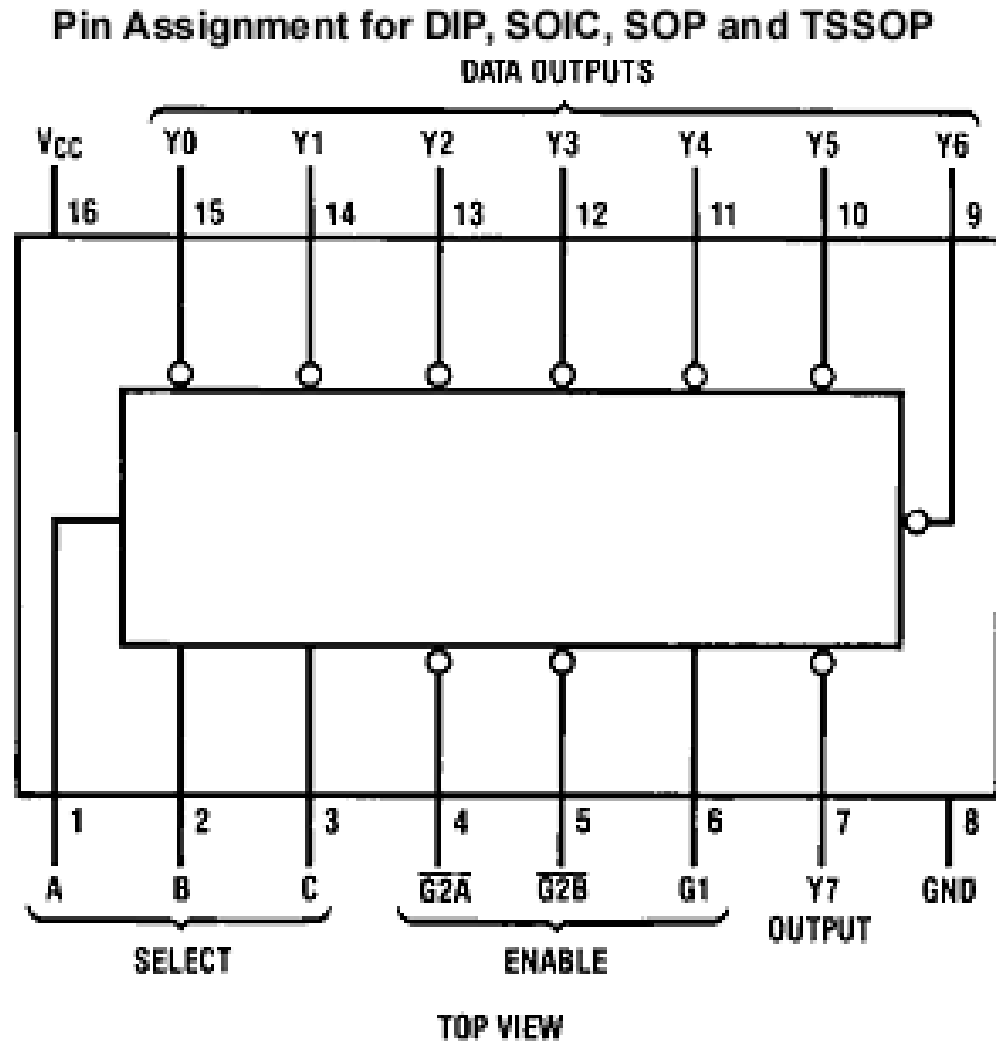

Contains one active low 3x8 decoder with three enable inputs (G2A, G2B, G1)

Decoders (cont.)

◆ 74138 Single 3x8 Decoder (cont.)

Truth Table

Inputs			Outputs									
Enable		Select			Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
G1	$\overline{G2}$ (Note 1)	C	B	A								
X	H	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	H	H	H	H	H	L	H	H	H	H
H	L	H	L	L	H	H	H	H	L	H	H	H
H	L	H	H	L	H	H	H	H	H	L	H	H
H	L	H	H	H	H	H	H	H	H	H	H	L


H = HIGH Level, L = LOW Level, X = don't care

Note 1: $\overline{G2} = G2A + G2B$

Output is enabled only when $G1 = 1$, $\overline{G2A} = 0$, $\overline{G2B} = 0$

Decoder

- ◆ 74138 Decoder chip

 

Decoder

- 74138 Decoder

Enabled I/P			Input			Output							
\overline{E}_1	\overline{E}	E_3	A	B	C	\overline{Y}_0	\overline{Y}_1	\overline{Y}_2	\overline{Y}_3	\overline{Y}_4	\overline{Y}_5	\overline{Y}_6	\overline{Y}_7
1	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	0	X	X	X	1	1	1	1	1	1	1	1
0	0	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	0	1	1	1
0	0	1	1	0	1	1	1	1	1	1	0	1	1
0	0	1	1	1	0	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	1	1	1	1	0

Decoders (cont.)

- ◆ 74x139 Dual 2x4 Decoder

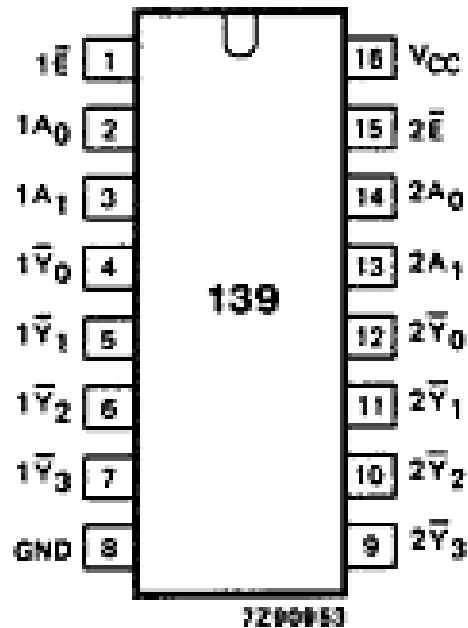


Fig.1 Pin configuration.

 


Fig.2 Logic symbol.

Contains two 2x4 decoder with separate enable

Decoders (cont.)

◆ 74x139 Dual 2x4 decoder (cont.)

FUNCTION TABLE

INPUTS			OUTPUTS			
\overline{nE}	nA_0	nA_1	$\overline{nY_0}$	$\overline{nY_1}$	$\overline{nY_2}$	$\overline{nY_3}$
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	H	L	H	L	H	H
L	L	H	H	H	L	H
L	H	H	H	H	H	L



Notes

1. H = HIGH voltage level
L = LOW voltage level
X = don't care

Output depends on inputs A with $\overline{nE} = 0$

Decoders (cont.)

  - ◆ How to design 1x8 demux using the 74138?





Want to make this
Functions as a
1x8 demux

Decoders (In General)

DM74LS138 • DM74LS139

Connection Diagrams

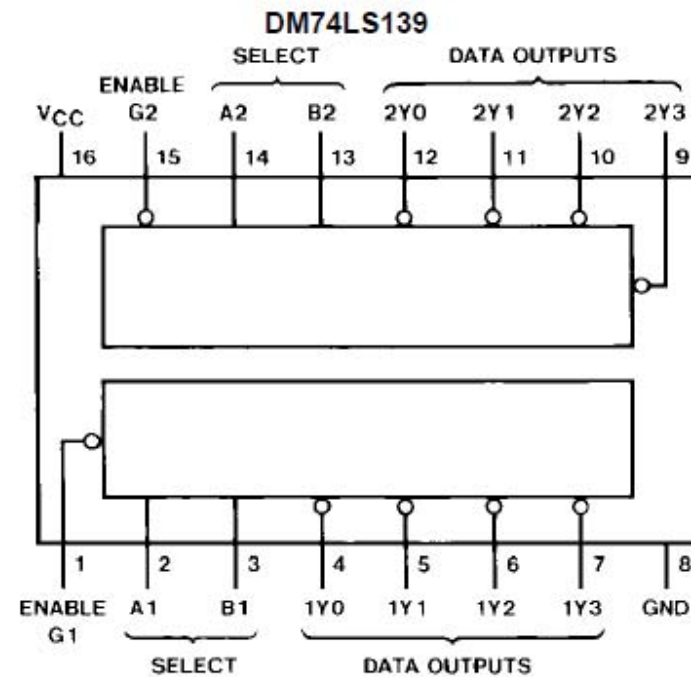 

Decoders (LS138 & LS139)

Function Tables

DM74LS138

Inputs					Outputs							
Enable		Select										
G1	G2 (Note 1)	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
X	H	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	H	H	H	H	H	L	H	H	H	H
H	L	H	L	L	H	H	H	H	L	H	H	H
H	L	H	L	H	H	H	H	H	H	L	H	H
H	L	H	H	L	H	H	H	H	H	H	L	H
H	L	H	H	H	H	H	H	H	H	H	H	L

DM74LS139

Inputs			Outputs			
Enable	Select					
G	B	A	Y0	Y1	Y2	Y3
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	L	H	H	L	H	H
L	H	L	H	H	L	H
L	H	H	H	H	H	L

H = HIGH Level


L = LOW Level

X = Don't Care

Note 1: $G2 = G2A + G2B$


Decoder

- ◆ BCD to 7-Segment Decoder

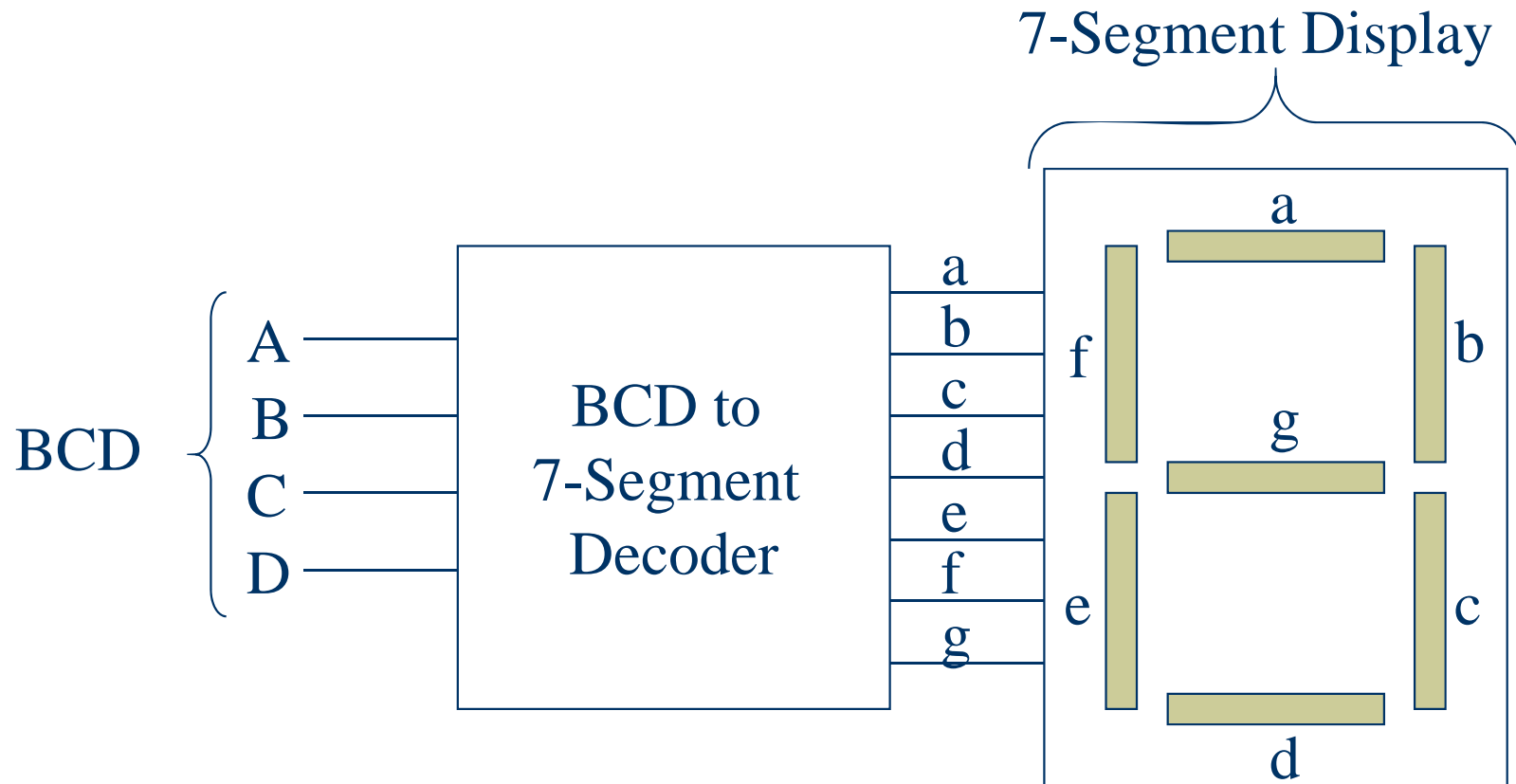

Decoder

- ◆ 7-Segment Display

 

- ◆ Common Anode :

- Output of decoder must be active low to light up.

- ◆ Common Cathode :

- Output of decoder must be active high to light up.



BCD to seven segments decoders- drivers 7447A (74LS47) and 7448 (74LS48)

- The BCD to 7 Segments Decoder is used exclusively for the drive the display of decimal digits; therefore it is usually called Decoder Driver.


BCD to seven segments decoders- drivers 7447A (74LS47) and 7448 (74LS48)

- BCD to 7 Segments Decoders are the TTL the 74(LS)47 which drives the common anode displays and the 74(LS)48 which drives the common cathode displays.


Anode and Cathode

  

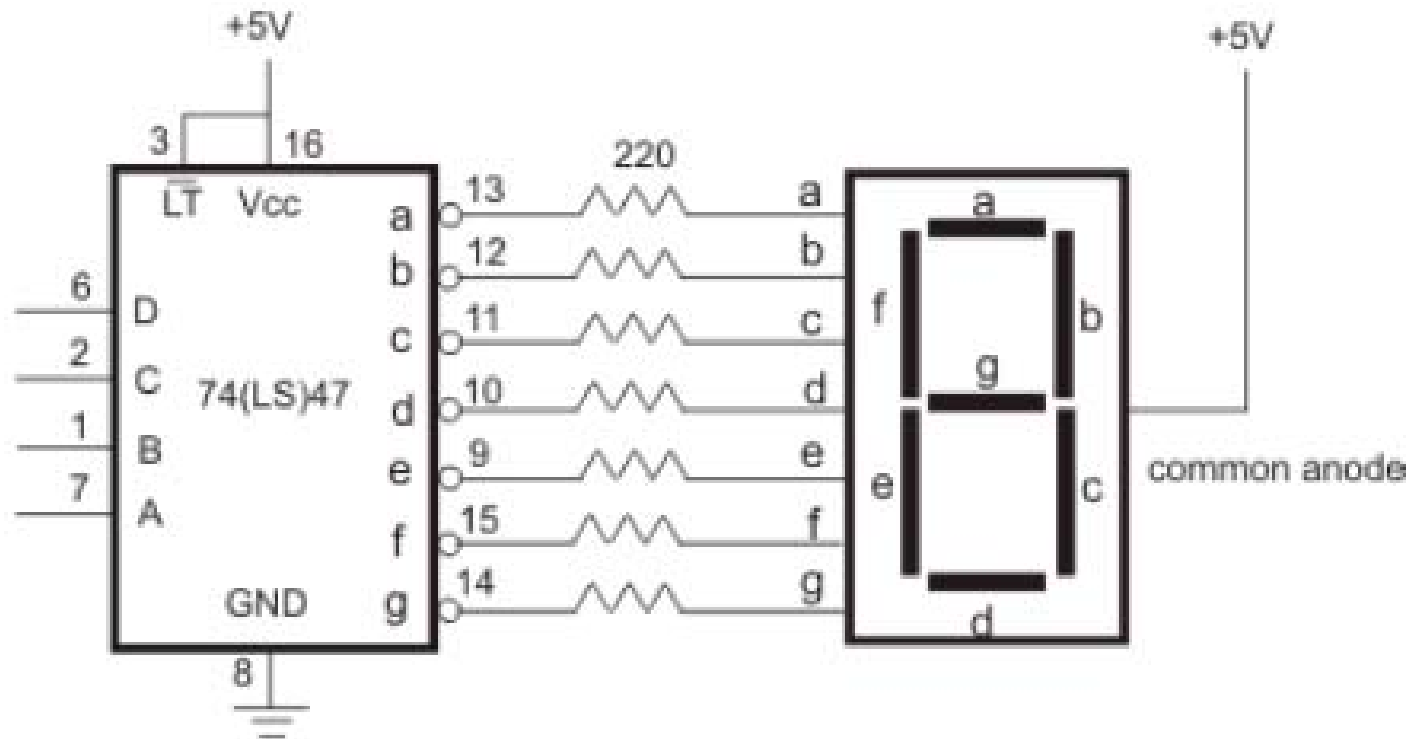BCD to seven segments decoders- drivers 7447A (74LS47)



 
BCD to seven segments decoders- drivers 7448 (74LS48)




BCD to 7 Segment Decoder

- 7447 BCD to 7 Segment Decoder

Connection Diagram

 

Logic Symbol

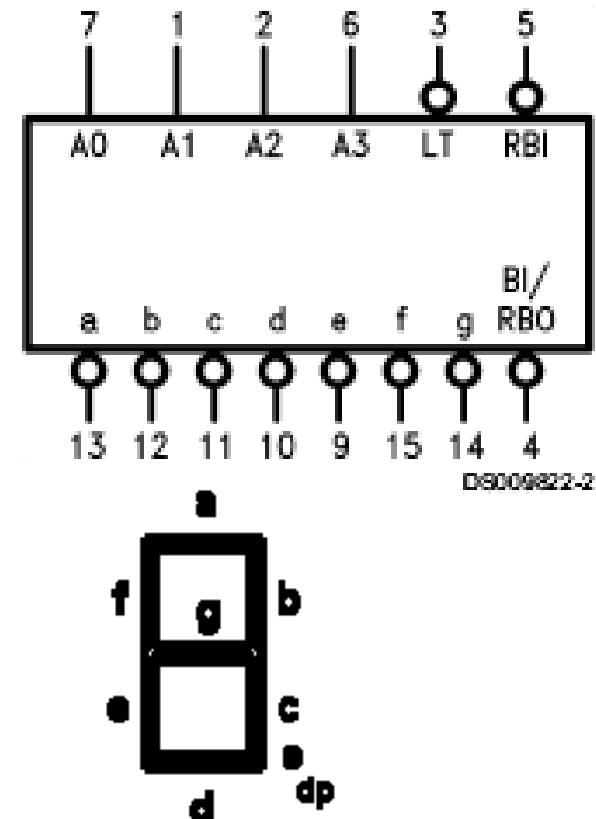


Converts 4-bit BCD (A3, A2, A1, A0) to 7-segment LED (a,b,c,d,e,f,g)


BCD to 7 Segment Decoder (cont.)

- What is the output of 7447 if input is 0110?

Logic Symbol

 

V_{cc} = Pin 16
GND = Pin 8

 

a	b	c	d	e	f	g
0	1	0	0	0	0	0

Exercise 1

- ◆ Show how the outputs of the truth table below can be implemented using:
 - 3 to 8 (1-of-8) active high decoder
 - 2 to 4 (1-of-4) active high decoder

E'	A	B	C	O0	O1	O2	O3	O4	O5	O6	O7
0	0	0	0	1	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0	0
0	1	0	0	0	0	0	0	1	0	0	0
0	1	0	1	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	0	0	0	1	0
0	1	1	1	0	0	0	0	0	0	0	1

Solution Exercise 1

- 3 to 8 (1-of-8) active high decoder
 - Answer : label a 3 to 8 decoder correctly
- 2 to 4 (1-of-4) active high decoder
 - Answer : Cascade two 2-to-4 decoders, assume both decoders have active low enable bit E' (E -bar). The first decoder's enable bit connected to A and the second decoder's enable bit connected to A -bar. The two inputs of each decoder is connected to B and C, with B as MSB. Eight outputs can be obtained, with output O0-O3 from first decoder, and O4-O7 from second decoder.

Exercise 2

- ◆ Implement the output of the truth table using a 3 to 8 (or 1-of-8) decoder with :

- active high output
- active low output

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

→ O_0 or $\overline{O_0}$

→ O_1 or $\overline{O_1}$

→ O_2 or $\overline{O_2}$

→ O_3 or $\overline{O_3}$

→ O_4 or $\overline{O_4}$

→ O_5 or $\overline{O_5}$



→ O_6 or $\overline{O_6}$

→ O_7 or $\overline{O_7}$



Solution Exercise 2

- ◆ Implement the output of the truth table using a 3 to 8 (or 1-of-8) decoder with :

- active high output

  


- active low output

 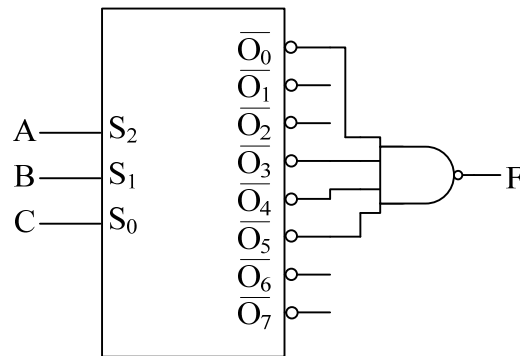

Encoder

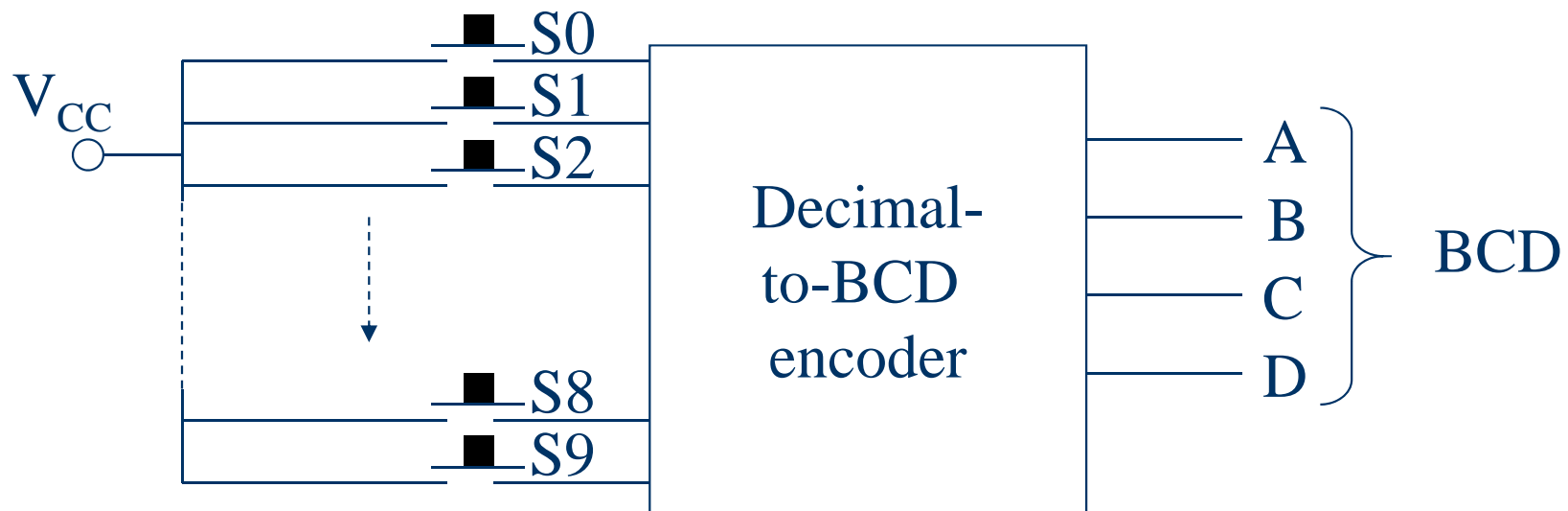- ◆ An encoder accepts an active level on ONE of its inputs, and converts it to a coded output.
- ◆ For example, the Decimal to BCD encoder as shown in figure below. This encoder has 10 inputs and 4-bit output. Input and output are ACTIVE HIGH (normal state is LOW).



Encoder

- ◆ Truth table for Decimal-to-BCD encoder

S0	S1	S2	S3	S4	S5	S6	S7	S8	S9	A	B	C	D
1										0	0	0	0
	1									0	0	0	1
		1								0	0	1	0
			1							0	0	1	1
				1						0	1	0	0
					1					0	1	0	1
						1				0	1	1	0
							1			0	1	1	1
								1		1	0	0	0
									1	1	0	0	1

Encoder

- ◆ Obtain the Boolean expression for each output, and draw the logic circuit

$$A = S8 + S9$$

$$B = S4 + S5 + S6 + S7$$

$$C = S2 + S3 + S6 + S7$$


$$D = S1 + S3 + S5 + S7 + S9$$

A has one OR gate with 2 inputs

B has one OR gate with 4 inputs

C has one OR gate with 4 inputs



D has one OR gate with 5 inputs

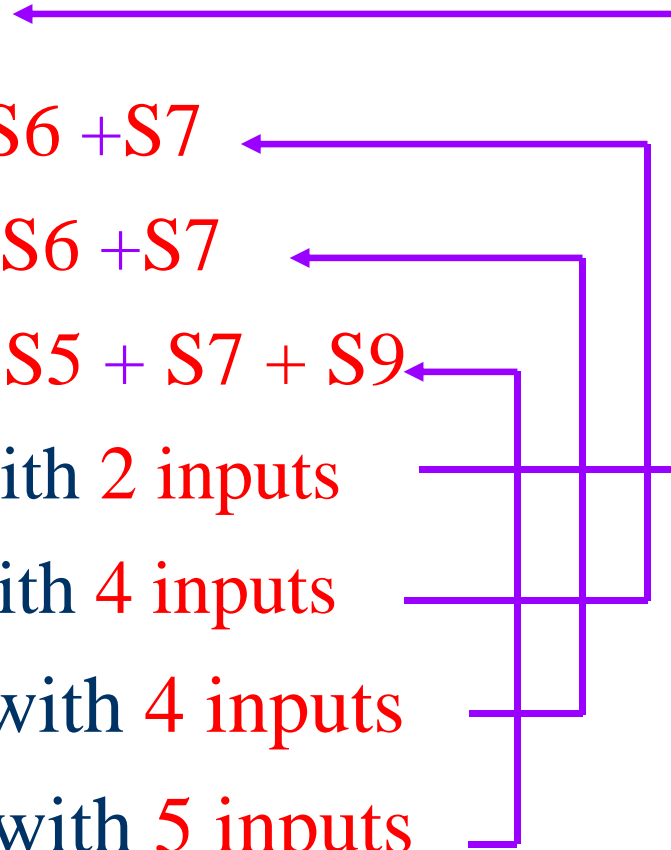


Encoder

- ◆ The 74HC147 Decimal-to-BCD **Priority Encoder**.
- ◆ Active-LOW input, active-LOW output
- ◆ HPRI /BCD means highest value input has priority.
- ◆ Example: If both key 3 and 6 are pressed, the BCD output will be 0110 (representing the decimal 6, which has higher value).

+V

  

74HC147

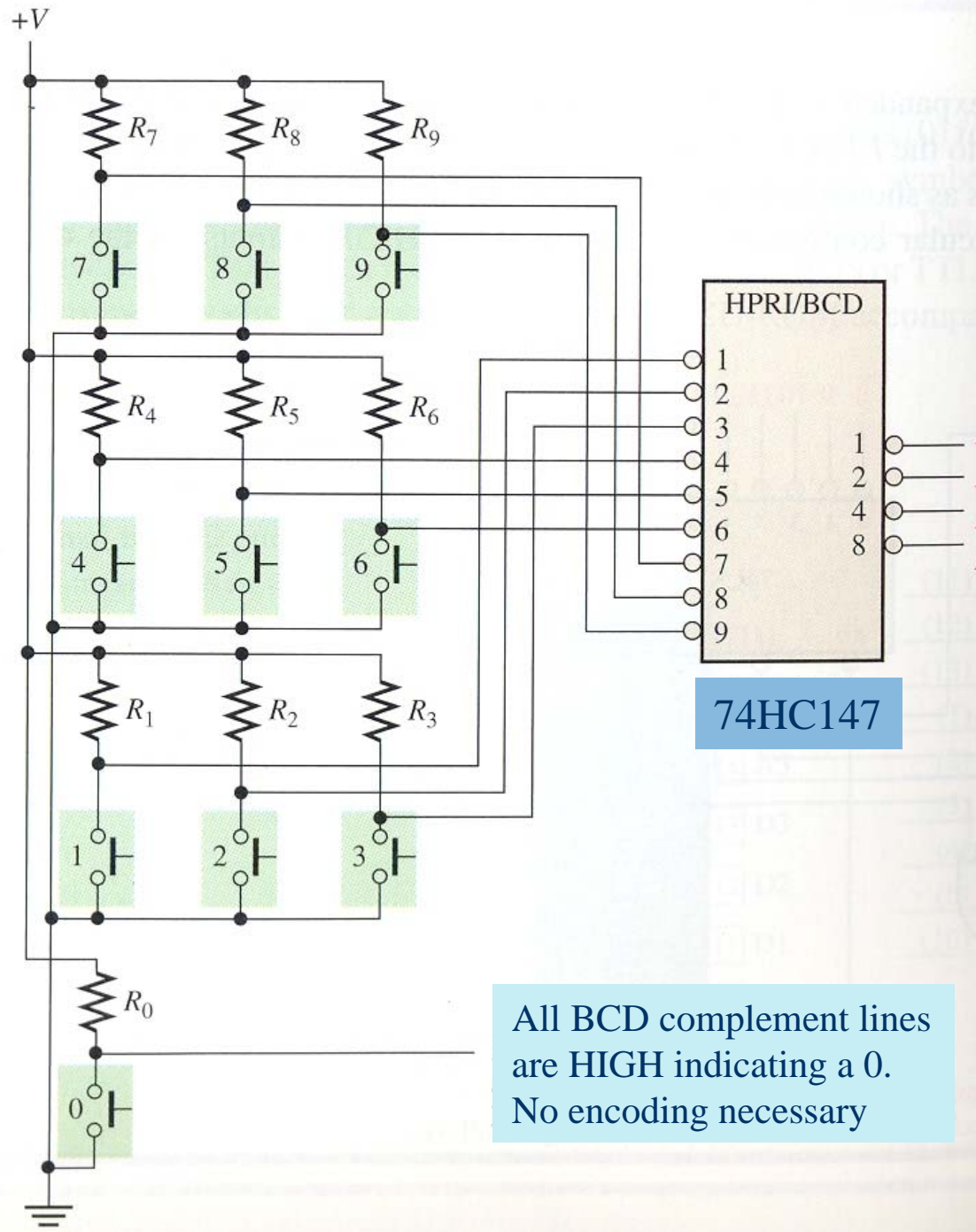

All BCD complement lines are HIGH indicating a 0. No encoding necessary

Encoder

- ◆ Design a 3 inputs and 2 outputs **LOWEST-PRIORITY ENCODER**? (**active HIGH** input and output)
- ◆ Ex: if all S_1 , S_2 , and S_3 is activated then S_1 will be considered.
- ◆ If $S_1 = 1$, $Y_1 Y_0 = 01$; if $S_2 = 1$, $Y_1 Y_0 = 10$; if $S_3 = 1$, $Y_1 Y_0 = 11$;
no inp active, $Y_1 Y_0 = 00$



$S_3 S_2 S_1$	$Y_1 Y_0$
000	00
001	01
010	10
011	01
100	11
101	01
110	10
111	01

Encoder

- ◆ The truth table for
 - **lowest priority** encoder
 - active high input
 - active high output

can be simplified

S_3 S_2 S_1	Y_1 Y_0
0 0 0	00
X X 1	01
X 1 0	10
1 0 0	11

Encoder

- ◆ Design a 3 inputs and 2 outputs HIGHEST-PRIORITY ENCODER? (**active LOW** input and output)
- ◆ Eg, if all A, B, and C is activated then A will be considered.
- ◆ If A=0, $Y_1Y_0=00$; if B=0, $Y_1Y_0=01$; if C=0, $Y_1Y_0=10$;
no inp active, $Y_1Y_0=11$



ABC	Y_1Y_0
000	00
001	00
010	00
011	00
100	01
101	01
110	10
111	11

Encoder

- ◆ The truth table for
 - highest priority encoder
 - **active low** input
 - active low output

can be simplified to:


$S_3 S_2 S_1$	$Y_1 Y_0$
0 X X	00
1 0 X	01
1 1 0	10
1 1 1	11

5.5 Encoders

- Priority Encoders

The solution is to assign priority to the input lines, so that when multiple inputs are asserted, the encoding device produces the number of the highest-priority input. Such a device is called a priority encoder.

- The 74x148 Priority Encoders

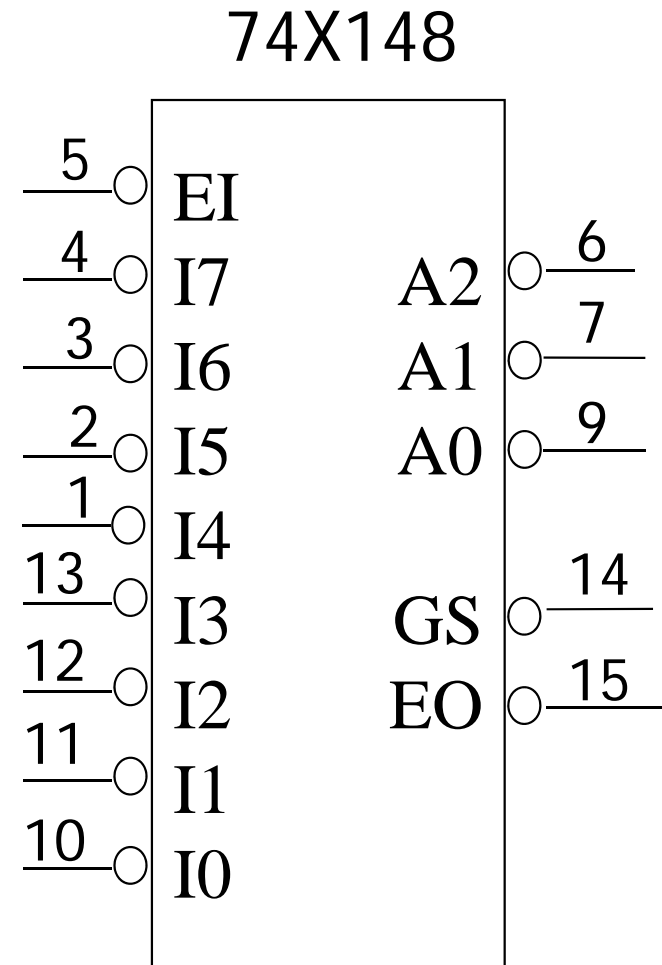

Return

Back

Next

5.5 Encoders

- Input data $\overline{I_0}-\overline{I_7}$
- Enable input \overline{EI}
- Output \overline{GS} is asserted when the device is enabled and one or more of the request are asserted.
- Output \overline{EO} is asserted if \overline{EI} is assert but no request input is asserted, it designed to be connected to the \overline{EI} input of another '148 that handles lower-priority requests.

Return


Back

Next

Encoders

- Performs reverse decoder function

4x2 Encoder

 

Function:

$$A_1A_0 = 00 \text{ when } D_3D_2D_1D_0 = 1110$$

$$A_1A_0 = 01 \text{ when } D_3D_2D_1D_0 = 1101$$

$$A_1A_0 = 10 \text{ when } D_3D_2D_1D_0 = 1011$$

$$A_1A_0 = 11 \text{ when } D_3D_2D_1D_0 = 0111$$

Which implies,

$$A_1 = D_3\overline{D_2}\overline{D_1}D_0 + \overline{D_3}D_2D_1D_0$$


$$A_0 = D_3D_2\overline{D_1}D_0 + \overline{D_3}D_2D_1D_0$$

What happens if more than 1 input is '0' ($D_0 = 0$ and $D_1 = 0$)?

- We need a priority encoder

Encoders (cont.)

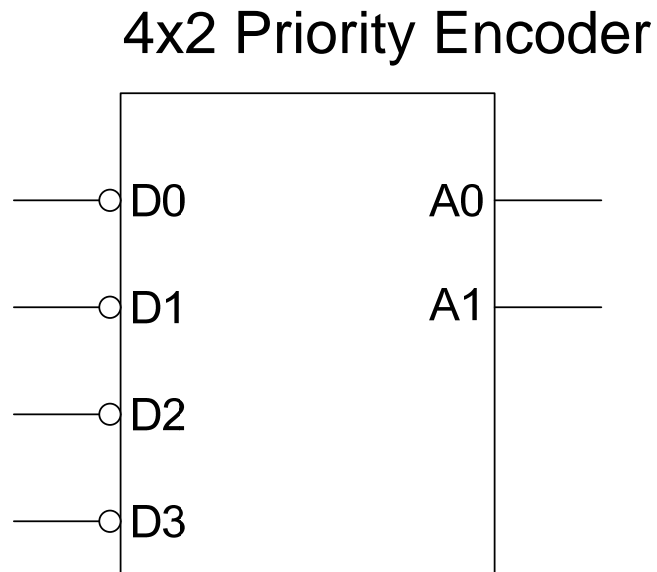- Priority Encoder: Output depends on the largest active input



Function:

$A_1A_0 = 00$ when $D_3D_2D_1D_0 = 1110$

$A_1A_0 = 01$ when $D_3D_2D_1D_0 = 110x$

$A_1A_0 = 10$ when $D_3D_2D_1D_0 = 10xx$

$A_1A_0 = 11$ when $D_3D_2D_1D_0 = 0xxx$

Can you derive the truth table of the priority encoder?

What happens if more than 1 input is '0' ($D_0 = 0$ and $D_1 = 0$)?


- output $A_1A_0 = 01$

Logic function using Mux


- Any logic function (AND, OR, decoder, encoder, etc) can be realized using mux. All we need is a truth table
- This is the concept widely being used today in FPGA (Field Programmable Gate Array), where any logic functions can be rapidly implemented using Mux

Logic function using Mux (cont.)

- 2-input AND gate using 4x1 Mux

 

X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

 


Logic function using Mux (cont.)

- Implement the following using Mux


$$F(A, B, C) = \sum m(0,1,4,7)$$

C	B	A	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

Logic function using Decoder

 
- Similar to Mux, any logic function can be realized using decoders
- 2-input AND gate using 2x4 decoder



AND gate

X	Y	Z = X · Y
0	0	0
0	1	0
1	0	0
1	1	1

2x4 Decoder

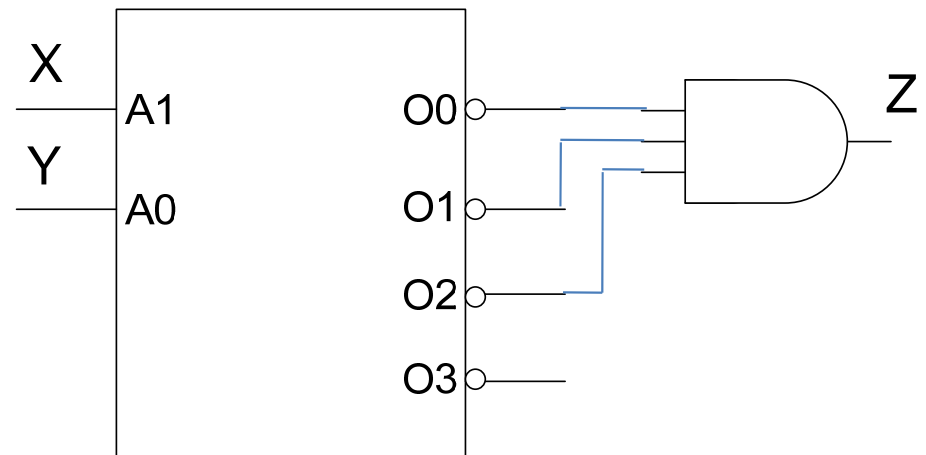

Logic function using Decoder (cont.)

- Implement the following using 74138

$$F(A, B, C) = \prod M(2, 3, 5, 6)$$

C B A	F
0 0 0	1
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	0
1 1 0	0
1 1 1	1

