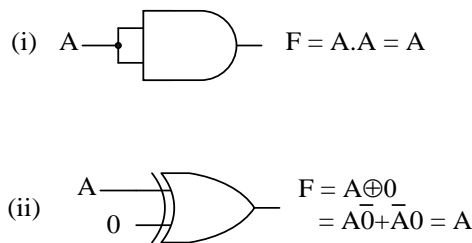



Solution to Exercise for Test 1

1. 1. resolution 2. data 3. acceleration 4. digitized 5. reconverted
2. (i) digital (ii) convert digital to analogue signals (iii) audio amplifier
3. (i) 8 bits (ii) 4 bytes (iii) 2 nibbles
4. (a) 1001 (b) A00 (c) 0001 0000 0000
5.  $1x8^2+6x8+7 = 4X^2+3X+4, 4X^2+3X-115 = 0, (4X+23)(X-5) = 0, \therefore X = 5.$
6. (a)  $10110_G = 11011_2 = 27_{10} = 0010\ 0111_{BCD}$   
(b)  $5742_8 = 101111100010_2 = BE_{16}$
7. (i)  $11101_2 = 29_{10}, 29/20 = 1$  remainder 9,  $1/20 = 0$  remainder 1,  $\therefore 11101_2 = 19_{20}.$   
(ii)  $2BJ_{20} = 2x20^2+11x20+19 = 1039_{10}.$
8.  $43_8 = 35_{10}, 00110111_{BCD} = 37_{10}, 24_{16} = 36_{10}, 00100010_2 = 34_{10}, 0201_4 = 33_{10},$   
In ascending order :  $0201_4, 00100010_2, 43_8, 24_{16}, 00110111_{BCD}$
9. All false

10.




11.

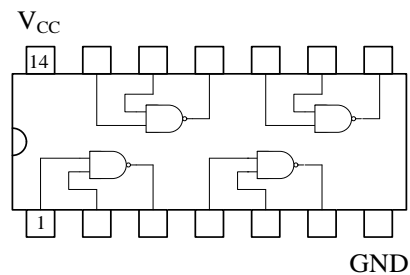

12. Correct statements are (i) and (ii).


13. (a)  $F = \overline{\overline{A + A + B + B + A + B}} = (A + \bar{A}.B)(B + \bar{A}.B) = (A + \bar{B}).(B + \bar{A}) = A.B + \bar{A}.B$
- (b)  $F = \overline{(A + B).(\bar{A}.B)} = \overline{(A + B)} + A.B = \bar{A}.B + A.B$  Both are X-NOR gates.

14.

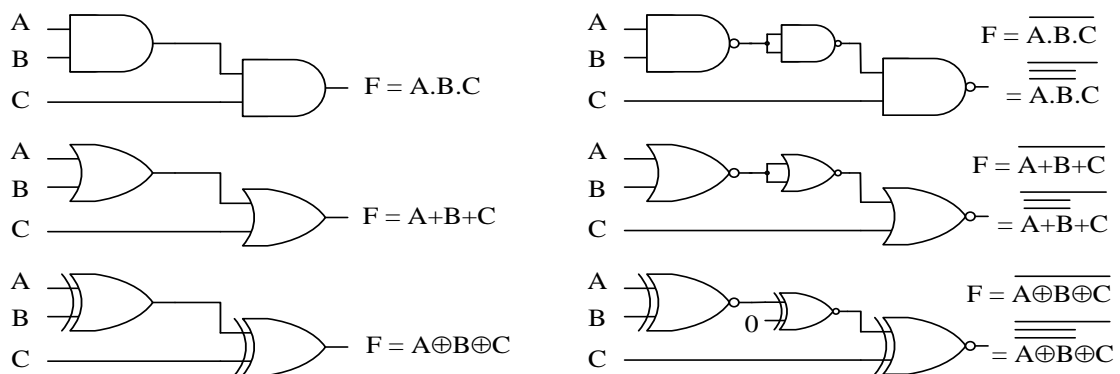


AND, OR and X-OR gates can be cascaded, while NAND, NOR and X-NOR gates can't be cascaded directly - requires additional inverter.

15.

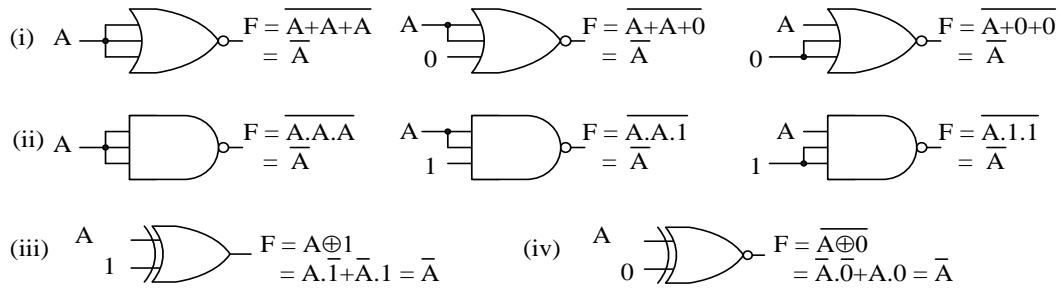


16. (a)

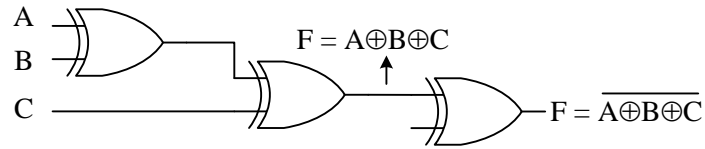


(b)

$$F = A + B.C = \overline{\overline{A + B.C}} = \overline{\overline{A}. \overline{B.C}} = \overline{\overline{A}. \overline{B}. \overline{C}}$$
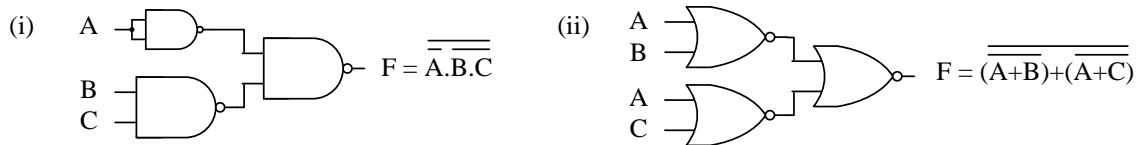
$$= (A + B).(A + C) = \overline{\overline{A + B}. \overline{A + C}} = \overline{\overline{A + B} + \overline{A + C}}$$



17.

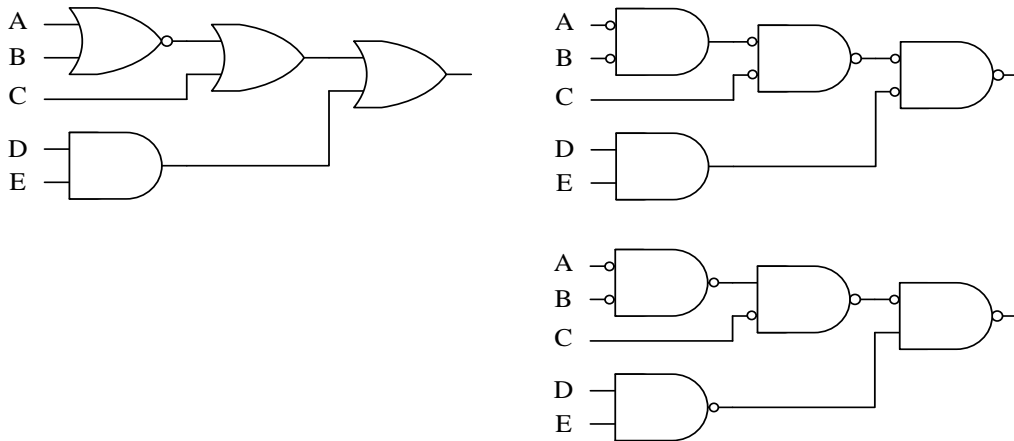


18.  $A \oplus B = \overline{\overline{A}. \overline{B}} + \overline{\overline{A}. B} = \overline{\overline{A}. \overline{B}} = A + B$

19. (a)  $(UTM) + (UITM) = UTM(1+I) = UTM$  True
- (b)  $AB + BA = ABBA, ABBA = AB$  True
- (c)  $KL(\overline{KL} + C) = KLCC, KL\overline{KL} = 0, KLC = KLCC$  True
- (d)  $(FKE) \oplus (FKE) = (UTM) \oplus (UTM), A \oplus A = 0$  True

20.

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0
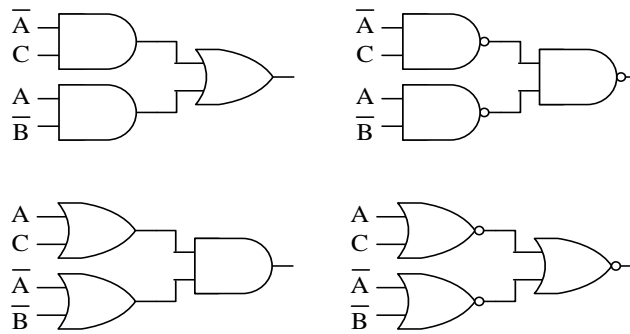
$$\begin{aligned}
 F(A,B,C) &= \sum m(1, 3, 4, 5) = \bar{A}\bar{B}.C + \bar{A}.B.C + A.\bar{B}.\bar{C} + A.B.\bar{C} = \bar{A}.C + A.\bar{B} \\
 &= \prod M(0, 2, 6, 7) = (A+B+C)(A+\bar{B}+C)(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C}) \\
 &= (A+C+B.\bar{B})(\bar{A}+\bar{B}+C.\bar{C}) = (A+C)(\bar{A}+\bar{B})
 \end{aligned}$$



21.

$$\begin{aligned}
 F(A,B,C,D) &= \overline{A.B + \bar{B}.C.C.D} = \overline{A.B.B.C.C.D} = (\bar{A} + \bar{B})(\bar{B} + \bar{C})(\bar{C} + D) \\
 &= \bar{A}.B.\bar{C} + \bar{A}.B.D + \bar{A}.\bar{C} + \bar{A}.\bar{C}.D + \bar{B}.\bar{C} + \bar{B}.\bar{C}.D \\
 &= \bar{A}.B.D + \bar{A}.\bar{C} + \bar{B}.\bar{C}
 \end{aligned}$$

